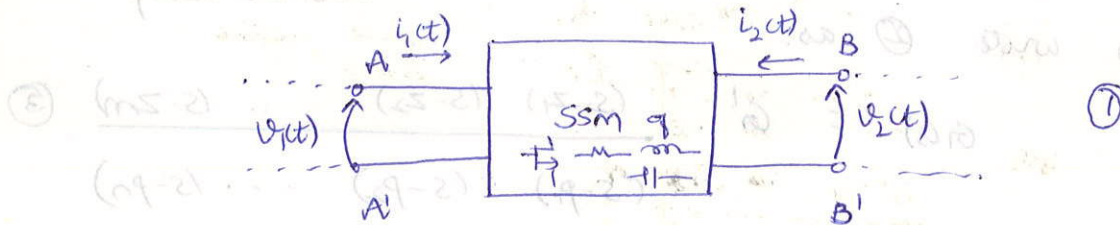


"It all boils down to amplification & matching."

Poles, Zeros & Freq Response (Molly Review)

SSM of any ckt containing transistors &

REC n/ws



$A, A' \equiv$ any two nodes of ckt.

$B, B' \equiv$ " "

Defn: Let $x(t) = 0 \quad \forall t < 0$ $x(t)$ be any real signal

Then $\mathcal{L}\{x(t)\} = \int_{-\infty}^{\infty} x(t) e^{-st} dt \equiv$ Bilateral Laplace transform
(all $x(t)$)

Let $G(s) = \frac{x(s)}{y(s)}$ where $x(t) = V_1(t), i_1(t), V_2(t)$ or $i_2(t)$
& $y(t) =$ " "

e.g. $G(s) = \frac{V_2(s)}{V_1(s)} \quad \frac{V_2(s)}{V_1(s)} \equiv$ Laplace transform of
gain from A, A' to B, B'

①.

or $G(s) = \frac{V_1(s)}{i_1(s)} \equiv$ Laplace transform of
impedance @ A, A' terminals
etc.

Fact: $G(s)$ is always rational w/ real coefficients.

(Something true but not going to prove it)

$$\text{i.e. } G(s) = \frac{a_m s^m + a_{m-1} s^{m-1} + \dots + a_1 s + a_0}{b_n s^n + b_{n-1} s^{n-1} + \dots + b_1 s + b_0}$$

where $a_k, b_k \in \mathbb{R}$ "real coeffs" $\rightarrow$ ② "rational"

Q Do $\exists$ practical sys. for which $G(s) \neq \text{rational}$
 $\downarrow$
 there exists

A Yes! eg: delay element:

$$G(s) = e^{-s\tau} \equiv \tau \text{ second delay}$$

(But $e^{-s\tau}$ is an infinite power series expansion which can be truncated hence its always fine to treat $G(s)$ as being rational)

can write ② as:

$$G(s) = G' \cdot \frac{(s-z_1)(s-z_2)\dots(s-z_m)}{(s-p_1)(s-p_2)\dots(s-p_n)} \quad \textcircled{3}$$

where $G', z_k, p_k \in \mathbb{C}$

$z_k, k=1,2,\dots,m \equiv \text{zeros of } G(s)$

$p_k, k=1,2,\dots,n \equiv \text{poles of } G(s)$

Fact

$G(s), s \in \mathbb{C}$

$G(j\omega), \omega \in \mathbb{R}$ (if it exists)

$$g(t) = \mathcal{L}^{-1}\{G(s)\}$$

"Impulse Response"

"Freq Response"

contain equivalent info about ①

(can obtain one from other interchangeably)

- Goal: Find simple way to deduce "shape" of $G(j\omega)$ from poles and zeros of $G(s)$

Claim 1: Real coefficients

$\iff \exists s_0 = \alpha + j\beta$
 is equivalent to $(\alpha, \beta \text{ are real no.s})$
 i.e. $\alpha, \beta \in \mathbb{R}$

is a pole (or zero) of $G(s)$

then $s_0^* = \alpha - j\beta$ is a pole (or zero) of $G(s)$

Proof: Exercise

Ex:

$$(s - s_0)(s - s_0^*) = s^2 - s(\underbrace{s_0 + s_0^*}_{2\text{Re}\{s_0\}}) + \underbrace{s_0 s_0^*}_{|s_0|^2}$$

$$= s^2 + s(-2\zeta\omega_0) + \omega_0^2$$

$\downarrow$ ζ (Zeta) ω_0

where $\omega_0 \equiv |s_0| \equiv$ "resonant freq"

$$\zeta = \frac{-\text{Re}\{s_0\}}{\omega_0} \equiv \text{"damping ratio"}$$

$$(Claim 1 \Rightarrow s, \omega_0 \in \mathbb{R})$$

Can group conjugate poles & zeros to get:

$$G(s) = G' \left[\prod_{\text{real zeros}} (s - z_k) \right] \left[\prod_{\text{complex zero pairs}} (s^2 + s(2\zeta_i \omega_{0i}) + \omega_{0i}^2) \right]$$

$$\star \left[\prod_{\text{real poles}} \frac{1}{(s - p_k)} \right] \left[\prod_{\text{complex pole pairs}} \frac{1}{s^2 + s(2\zeta_i \omega_{0i}) + \omega_{0i}^2} \right]$$

→ ④

Let $\omega_{zi}, i = 1, 2, \dots, N \equiv$ the set of (non-zero) real zeros

$\omega_{pi}, i = 1, 2, \dots, N' \equiv$ the set of (non-zero) real poles

Do complex
this always occur
in pairs?

$$\therefore G(s) = \underbrace{G(0)}_{\text{evaluated @ } s=0} s^{n_0} \left[\prod_{\text{real zeros}} (1 - s/\omega_{zk}) \right] \left[\prod_{\text{complex zero pairs}} \left(\frac{s^2}{\omega_{0zi}^2} + \frac{2\zeta_{zi}}{\omega_{0zi}} s + 1 \right) \right]$$

$$\star \left[\prod_{\text{real poles}} \frac{1}{(1 - s/\omega_{pk})} \right] \left[\prod_{\text{complex pole pairs}} \left(\frac{s^2}{\omega_{0pi}^2} + \frac{2\zeta_{pi}}{\omega_{0pi}} s + 1 \right) \right]$$

where $G(0) = \frac{a_0}{b_0}$

??

$n_0 = \# \text{ of } \underline{\text{real zeros}} - \# \text{ of } \underline{\text{real poles}}$

→ ⑤

Usually interested in $10 \log_{10} (|G(j\omega)|^2)$ & $\angle G(j\omega)$
 gain in dB $= \tan^{-1} \left(\frac{\text{Im} G(j\omega)}{\text{Re} G(j\omega)} \right)$

Gain (Assume $n_0=0$ for $n \geq 0$)

$$10 \log |G(j\omega)|^2 = 10 \log |G(0)|^2 \quad (6)$$

$$+ \sum_{\text{real zeros}} 10 \log (1 + \omega^2 / \omega_{zk}^2) \quad (7)$$

$$- \sum_{\text{real poles}} 10 \log (1 + \omega^2 / \omega_{pk}^2) \quad (8)$$

$$+ \sum_{\text{complex zero pairs}} 10 \log \left(\left(1 - \frac{\omega^2}{\omega_{0z1}^2} \right)^2 + 4 \frac{\zeta_{z1}^2}{\omega_{0z1}^2} \omega^2 \right) \quad (9)$$

$$- \sum_{\text{complex pole pairs}} 10 \log \left(\left(1 - \frac{\omega^2}{\omega_{0p1}^2} \right)^2 + 4 \frac{\zeta_{p1}^2}{\omega_{0p1}^2} \omega^2 \right) \quad (10)$$

Exercise: What if $n_0 \neq 0$?

$\Rightarrow$ Only 2 "types" of curves summed together



$$(7), (8) \rightarrow 0 \text{ as } \omega \rightarrow 0 \quad (\because \log 1 \rightarrow 0)$$

$$(7) \rightarrow 20 \log \omega + \text{const.} \quad (\text{as } \omega \rightarrow \infty)$$

$\downarrow$
 $(-20 \log \omega_{zk})$

$$(8) \rightarrow -20 \log \omega - \text{const.} \quad (\text{as } \omega \rightarrow \infty)$$

$\downarrow$
 $(20 \log \omega_{pk})$

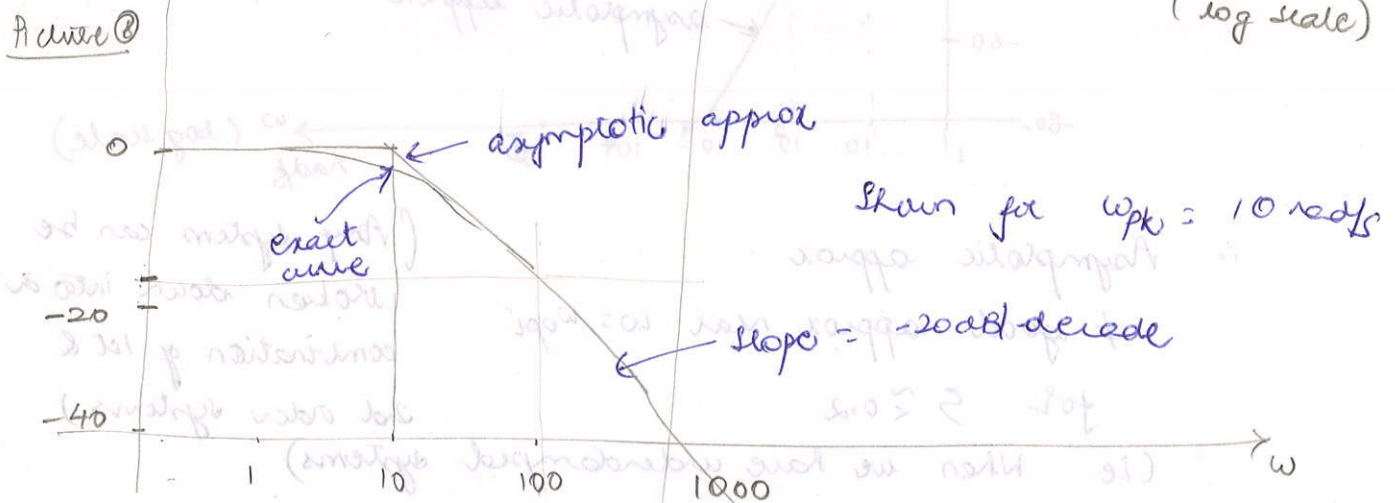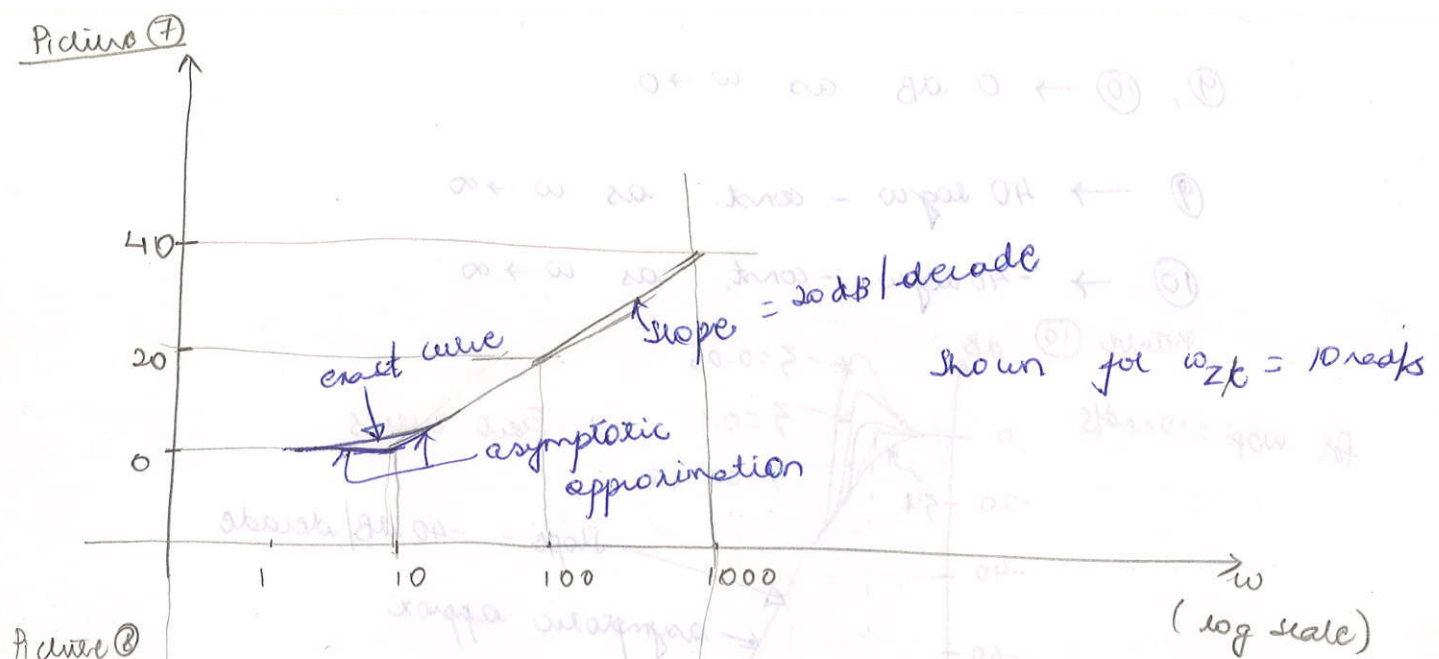

LEC #2

JAN 10'08

Recall ⑩:
$$20 \sum_{\text{complex pole pairs}} 10 \log \left[\left(1 - \frac{\omega^2}{\omega_{pi}^2} \right)^2 + 4 \frac{\zeta_{pi}^2}{\omega_{pi}^2} \omega^2 \right]$$


Claim 2: Max departure of ~~real~~ exact curve for real pole & real zeros factors from asymptotic approx. is factor of 0.707 in both ⑦ & ⑧.

Proof: Exercise

⑨, ⑩ $\rightarrow 0$ dB as $\omega \rightarrow 0$

⑨ $\rightarrow 40 \log \omega - \text{const.}$ as $\omega \rightarrow \infty$

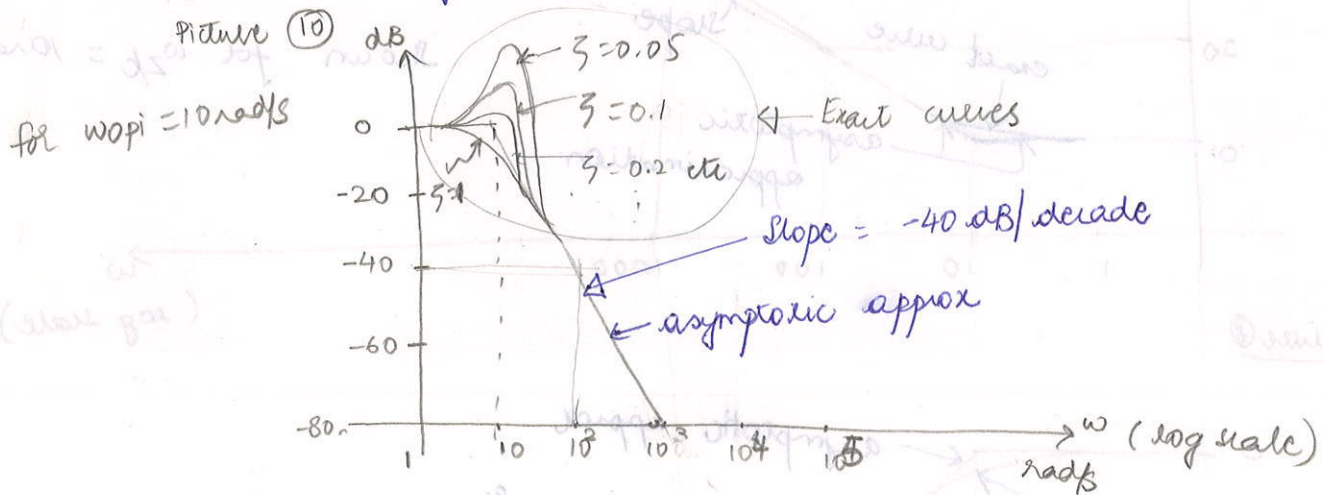⑩ $\rightarrow -40 \log \omega - \text{const.}$ as $\omega \rightarrow \infty$



$\therefore$ Asymptotic approx

$\neq$ good approx near $\omega = \omega_{0pi}$

for $\zeta \gtrsim 0.2$

(i.e. When we have underdamped systems)

(Any system can be broken down into a combination of 1st & 2nd order systems)


Poles associated w/ ⑩:

(Verify)

$$\theta = \tan^{-1} \sqrt{\frac{1}{\zeta_{pi}^2} - 1}$$

$$= \cos^{-1}(\zeta_{pi})$$

$$(\zeta_{pi} < 1)$$

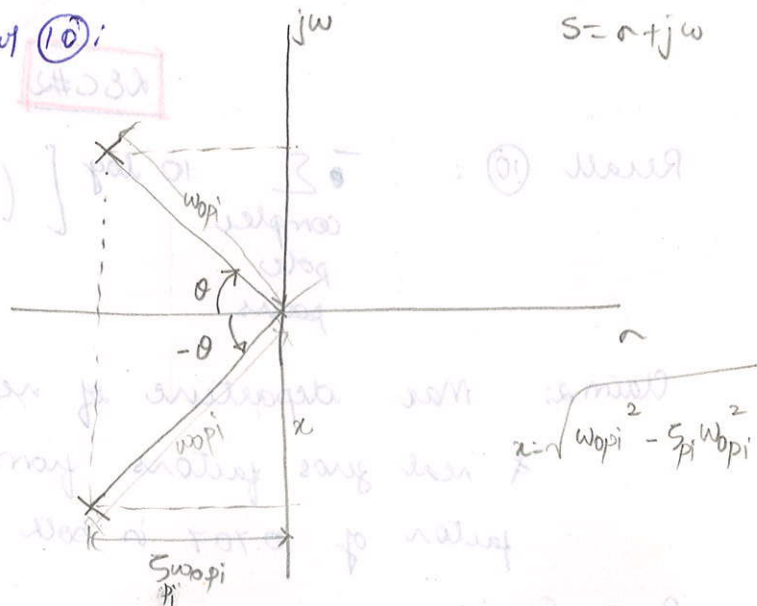

Start of new lecture (new #s for equations)

$$G(s) = \frac{a_n s^n + a_{n-1} s^{n-1} + \dots + a_1 s + a_0}{b_n s^n + b_{n-1} s^{n-1} + \dots + b_1 s + b_0} \quad (1)$$

where $a_k, b_k \in \mathbb{R}$ & $s \in \mathbb{C}$

(2) Let $\{w_{zk} : k=1, 2, \dots, N\}$ = non-zero, real zeros of (1) if any
 $\{w_{pk}, k=1, 2, \dots, N'\}$ = non-zero, real poles of (1) if any
 $\{s_{zk}, s_{zk}^* : k=1, \dots, N''\}$ = non-real conjugate zeros of (1) if any
 $\{s_{pk}, s_{pk}^* : k=1, \dots, N'''\}$ = non-real conjugate poles of (1) if any

$w_{xk} = |s_{xk}|$ ($x \equiv z \text{ or } p$) ($\equiv$ "natural freq" when $x=p$)
 (doesn't have any physical meaning for the case of zero)

$\zeta_{xk} = \frac{-\operatorname{Re}\{s_{xk}\}}{w_{xk}}$ ($x \equiv z \text{ or } p$) ($\equiv$ "damping ratio" when $x=p$)

Using (2), (1) becomes

$$(3) \quad G(s) = G(0) s^{n_0} \left[\prod_{k=1}^N (1 - s/w_{zk}) \right] \left[\prod_{k=1}^{N'} \frac{1}{1 - s/w_{pk}} \right] \left[\prod_{k=1}^{N''} \frac{1}{s^2 + 2\zeta_{zk} w_{zk} s + w_{zk}^2} \right] \left[\prod_{k=1}^{N'''} \frac{1}{s^2 + 2\zeta_{pk} w_{pk} s + w_{pk}^2} \right]$$

where $G(0) = \frac{a_0}{b_0}$, $n_0 = (\# \text{ of zero-freq zeros} - \# \text{ of zero-freq poles})$

$G(j\omega) = \underbrace{|G(j\omega)|}_{\text{magnitude}} e^{j \underbrace{\angle G(j\omega)}_{\text{phase}}}$

(mag. response indicates how I/P P.S.D. is transferred @ O/P)

(Phase response matters when for eg. we build feedback systems)

Phase response:

Exercise: Verify $\angle G(j\omega) = \sum \angle (\text{each factor in } \textcircled{3}) \big|_{s=j\omega}$

factor in ③ $\longrightarrow$ $\angle$ factor in ③ $\big|_{s=j\omega}$


$(a+j\omega)^n \quad G(\omega) = \frac{a_0}{b_0} \longrightarrow \begin{cases} 0 & \text{if } G(\omega) > 0 \\ \pi & \text{if } G(\omega) < 0 \end{cases}$


$s^N \longrightarrow \frac{\pi}{2} N$

$\frac{1}{(1 - \frac{s}{\omega_{xk}})} \longrightarrow \mp \tan^{-1} \left(\frac{\omega}{\omega_{xk}} \right) \quad x = \text{pole}$

$\left[\frac{1}{\omega_{oxk}^2} (s^2 + 2\zeta_{xk} \omega_{oxk} s + \omega_{oxk}^2) \right]^{-1} \longrightarrow \pm \tan^{-1} \left(\frac{2\zeta_{xk} \omega_{oxk} \omega}{\omega_{oxk}^2 - \omega^2} \right) \quad x = \text{pole}$

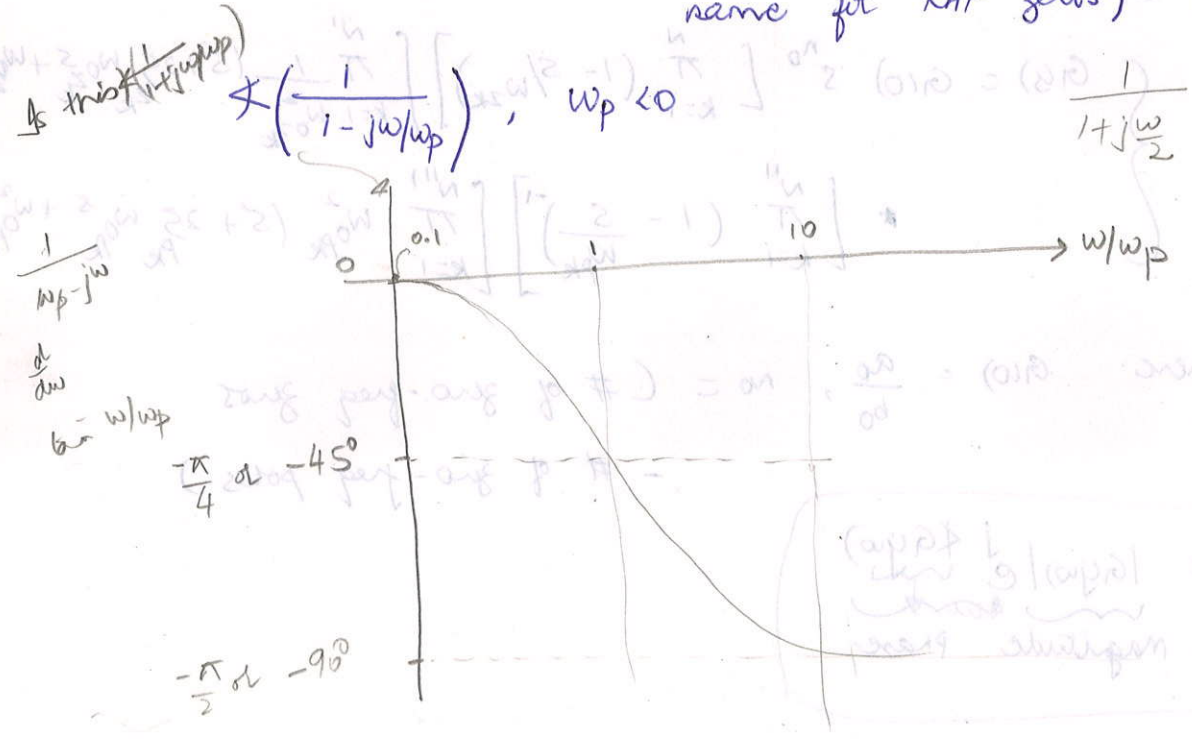Picture (For LHP poles, only sign changes for LHP zeros, name for RHP zeros)



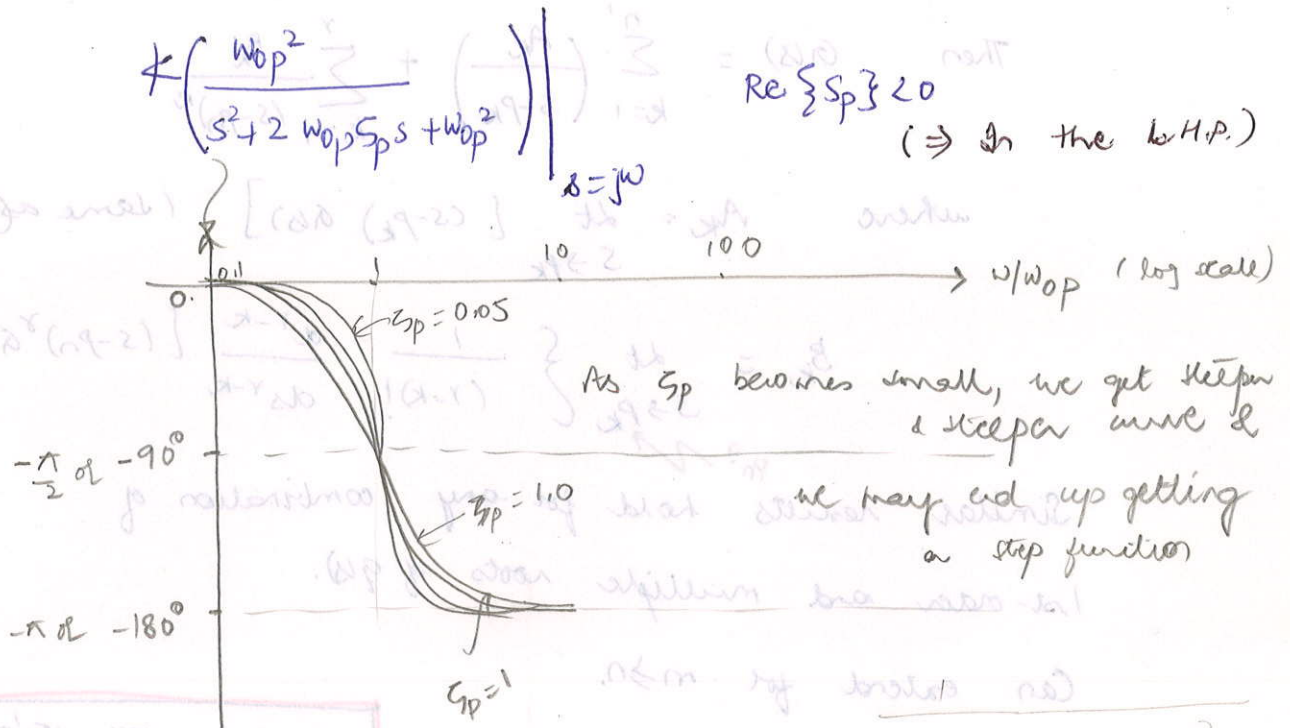

Poles, Zeros & time response

Let $p(s) = a_m s^m + a_{m-1} s^{m-1} + \dots + a_0$
 $q(s) = b_n s^n + b_{n-1} s^{n-1} + \dots + b_0$

$\Rightarrow G(s) = \frac{p(s)}{q(s)} = \frac{p(s)}{b_1 (s-p_1) (s-p_2) \dots (s-p_n)}$

Recall "Partial Fraction Expansion" (PFE)

Ex1 $m < n$ (i.e. more poles than zeros), $p_i \neq p_j$ for $i \neq j$
 $\Rightarrow$ Roots of $q(s)$ are all first order roots

Then $G(s) = \sum_{k=1}^n \frac{A_k}{(s-p_k)}$ where $A_k \in \mathbb{R}$

where $A_k = \lim_{s \rightarrow p_k} [(s-p_k) G(s)]$
 (4)

Ex2 $m < n$, $p_1, p_2, \dots, p_{n'}$ = 1st-order roots of $q(s)$
 where $n' \leq n-2$

and $p_{n'+1} = p_{n'+2} = \dots = p_n$

"multiple roots" of $q(s)$ where $r = n - n'$

Then $G(s) = \sum_{k=1}^{n'} \left(\frac{A_k}{s-p_k} \right) + \sum_{k=1}^r \frac{B_k}{(s-p_n)^k}$

where $A_k = \lim_{s \rightarrow p_k} [(s-p_k) G(s)]$ (same as ④)

$B_k = \lim_{s \rightarrow p_n} \left\{ \frac{1}{(r-k)!} \frac{d^{r-k}}{ds^{r-k}} [(s-p_n)^r G(s)] \right\}$ ⑤

Similar results hold for any combination of 1st-order and multiple roots of $q(s)$.

Can extend for $m > n$.

LEC #3 JAN 15 '08


Continuing from last time (i.e., retaining sequence of #s for eqs.)

Let $g(t) = \mathcal{L}^{-1} \{G(s)\}$

PFE $\Rightarrow g(t) =$ Weighted sum of terms of types:

$\mathcal{L}^{-1} \left\{ \frac{1}{s-p_k} \right\} = e^{p_k t} u(t)$ ⑥

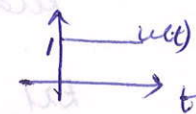$\mathcal{L}^{-1} \left\{ \frac{1}{(s-p_k)^r} \right\} = \frac{t^{r-1}}{(r-1)!} e^{p_k t} u(t)$ ⑦



Note: ⑦ = ⑥ + ⑥ + ⑥ + ⑥ + ... + ⑥

Convolution, r times

(multiplication in freq. domain = convolution in time domain)

In circuits, rarely have multiple roots of $q(s)$ (i.e. Rarely have multiple equal poles)

$\Rightarrow$ Only concerned w/ ⑥ usually

[Very often in DSP collection of analog ckts, we can have multiple identical terms]

For real non-zero poles,

$$(6) \propto \mathcal{L}^{-1} \left\{ \frac{1}{1 - s/\omega_{pk}} \right\} \quad (\omega_{pk} \text{ is real pole from last time})$$

For non-real poles, can group pairs for which ~~results~~ results in terms of form

$$\mathcal{L}^{-1} \left\{ \frac{\omega_{pk}^2}{s^2 + s(2\zeta_p \omega_{pk}) + \omega_{pk}^2} \right\}$$

(Impulse response difficult to stimulate in real world or in lab)

Step Response (is more convenient)


$$\mathcal{L}\{u(t)\} = \frac{1}{s} \quad \left[\int_{-\infty}^{\infty} e^{-st} f(t) dt = \int_0^{\infty} e^{-st} dt = \frac{e^{-st}}{-s} \right]_0^{\infty} = \frac{1}{s}$$

Response of "output" w/ "input" = $u(t) \equiv$ "step response"

$$\therefore g_{\text{step}}(t) = \mathcal{L}^{-1} \left\{ \frac{1}{s} \right\}$$

$$\mathcal{L}^{-1} \left\{ \frac{1}{s(1 - s/\omega_p)} \right\} = u(t) [1 - e^{\omega_p t}]$$


[ω_p is $-w$ for real systems]

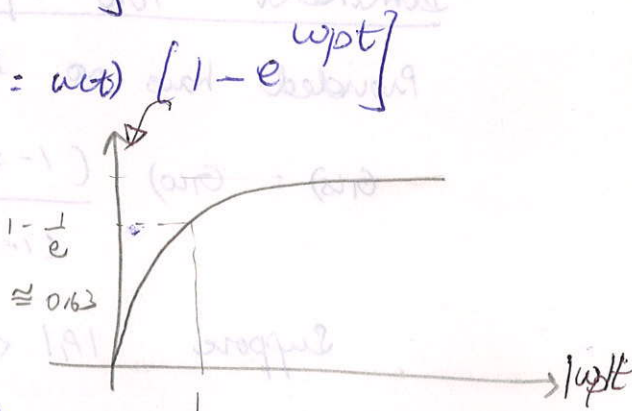

$$\mathcal{L}^{-1} \left\{ \frac{1}{s} \frac{\omega_{pk}^2}{s^2 + s(2\zeta_p \omega_{pk}) + \omega_{pk}^2} \right\}$$

$$= u(t) \left[1 \oplus \frac{1}{\sqrt{1 - \zeta_p^2}} e^{-\zeta_p \omega_{pk} t} \sin(\omega_{pk} \sqrt{1 - \zeta_p^2} t + \theta) \right]$$

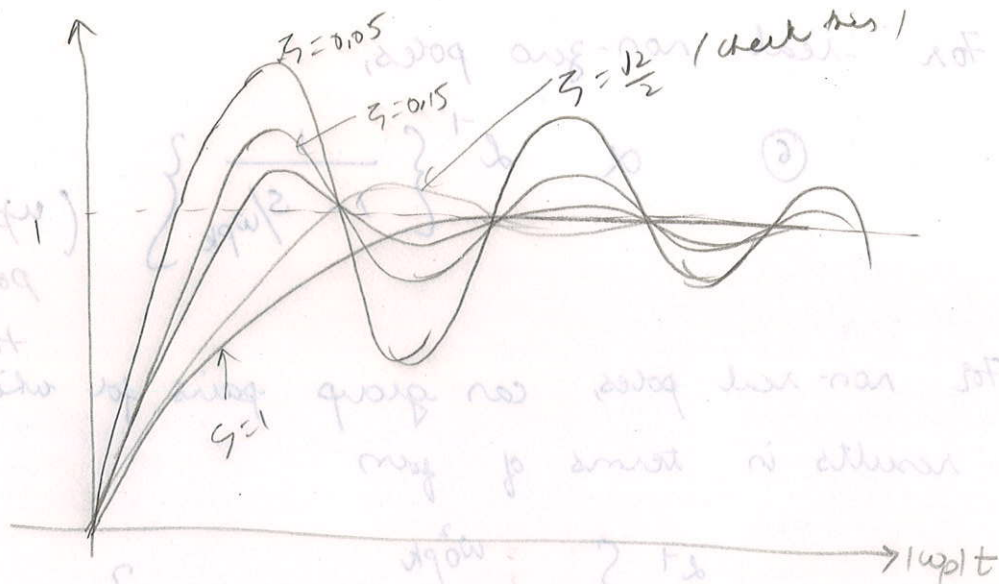where $\theta = \tan^{-1} \left(\frac{\sqrt{1 - \zeta_p^2}}{\zeta_p} \right)$



For $\zeta_p = 0$, poles on imaginary axis $\Rightarrow$ oscillation

For $\zeta_p < 0$, poles in RHP $\Rightarrow$ oscillation w/ exponentially increasing amplitude

For $0 < \zeta_p < 1$, "overshoots" but settles to 1

(Ringing is bad.)

Proven instabilities may lead to oscillation)

$$s = -\zeta_p \omega_{op} \pm \sqrt{4\zeta_p^2 \omega_{op}^2 - 4\omega_{op}^2}$$

Dominant Pole Approximation

Provided - have no DC poles or zeros =

$$G(s) = G(0) \frac{(1-s/z_1)(1-s/z_2) \dots (1-s/z_m)}{(1-s/p_1)(1-s/p_2) \dots (1-s/p_n)}$$

Suppose $|p_1| \ll |p_k|$, $2 \leq k \leq n \Rightarrow (p_1 \in \mathbb{R},$

$|p_1| \ll |p_k|$, $1 \leq k \leq m$

$\therefore$ Complex ^{poles} ~~poles~~ come in pair)

$$\text{Thus } |G(j\omega)| \approx \frac{G(0)}{\sqrt{1+\omega^2} |p_1|^2}$$

$$|G(j\omega_{-3dB})| = \frac{G(0)}{\sqrt{2}}$$

$$\Rightarrow \omega_{-3dB} = |A|$$



↳ called "3dB Bandwidth"

Reset # system

Common Source Amplifier's Freq. Response:


Aside: Course convention:

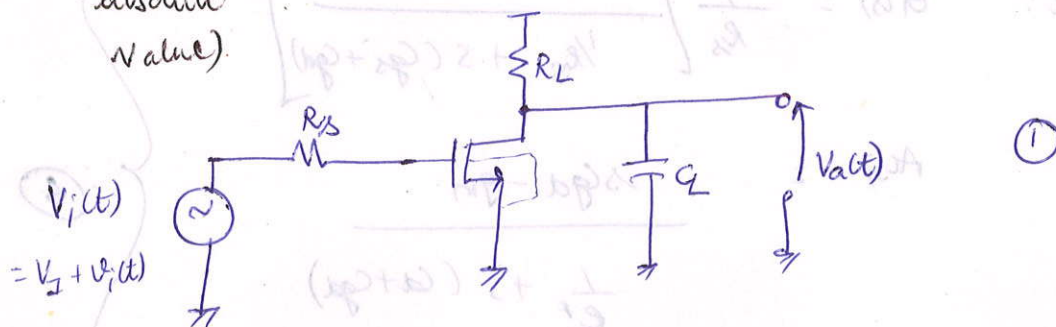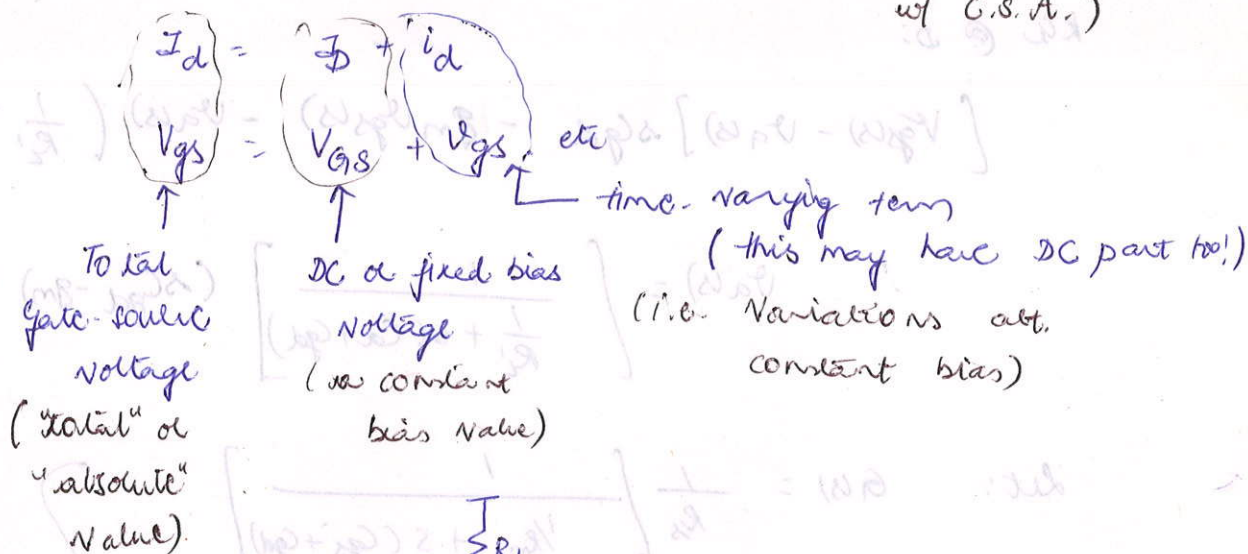(Can understand 90% of op-amps w/ C.S.A.)



(R_S & R_L from active ckt's (eg. R_L can be current source load) not actual resistors)

S.S.M.

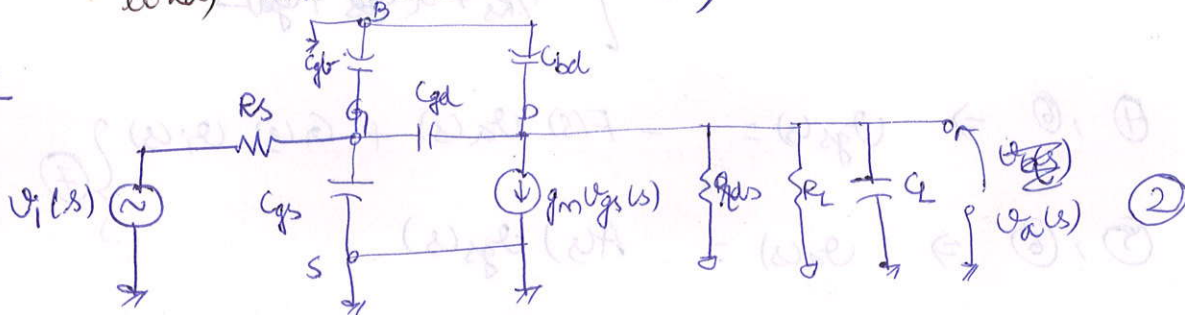

C_{gs} & C_{gd} are in ||.

Let

$$C_{gs}' = C_{gs} + C_{gs} \quad (\cong C_{gs} \text{ usually})$$

$$C_d = C_{gd} || R_L$$

$$R_L' = R_L || R_{ds}$$

eg. For $I_D = 200 \mu A$, $\mu_n = 50$, $V_{DS} = 500 k\Omega$
 $C_{gs}' = 90 fF$, $C_{gd} = 20 fF$
 $C_d = 80 fF$, $g_m = 1.7 \times 10^{-3} S$

③

Note: ② also ssm of diff. pair. Dm $\frac{1}{2}$ ckt,

KCL @ G:

$$\frac{V_i(s) - V_{gs}(s)}{R_s} - V_{gs}(s) s C_{gs}'$$

$$- [V_{gs}(s) - V_a(s)] s C_{gd} = 0$$

$$\therefore V_{gs}(s) = \left[\frac{1}{\frac{1}{R_s} + s(C_{gs}' + C_{gd})} \right] (V_a(s) s C_{gd} + V_i(s) \frac{1}{R_s}) \quad ④$$

KCL @ D:

$$[V_{gs}(s) - V_a(s)] s C_{gd} - g_m V_{gs}(s) - V_a(s) \left(\frac{1}{R_L} + s C_L \right) = 0$$

$$\therefore V_a(s) = \left[\frac{1}{\frac{1}{R_L} + s(C_L + C_{gd})} \right] (s C_{gd} - g_m) V_{gs}(s) \quad ⑤$$

$$\text{Let: } G(s) = \frac{1}{R_s} \left[\frac{1}{\frac{1}{R_s} + s(C_{gs}' + C_{gd})} \right]$$


$$A(s) = \frac{s C_{gd} - g_m}{\frac{1}{R_L} + s(C_L + C_{gd})} \quad ⑥$$

$$F(s) = -s C_{gd} \left[\frac{1}{\frac{1}{R_s} + s(C_{gs}' + C_{gd})} \right]$$

$$\textcircled{4}, \textcircled{6} \Rightarrow V_{gs}(s) = -F(s) V_a(s) + G(s) V_i(s) \quad ⑦$$

$$\textcircled{5}, \textcircled{6} \Rightarrow V_a(s) = A(s) V_{gs}(s)$$

⑦ $\Rightarrow$ "Block Diagram" of ②:

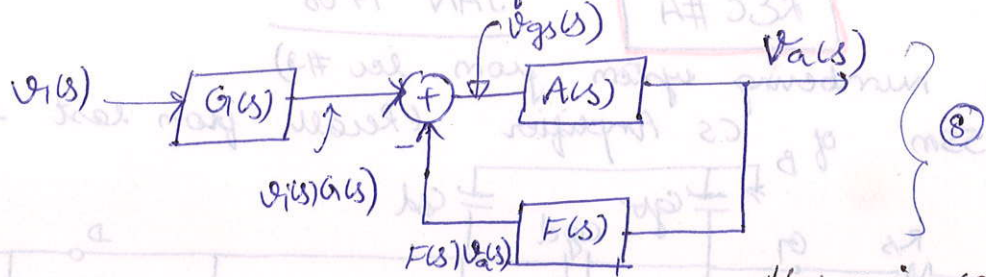

⑧ using Mason's gain Formula (SSM)

(or)

⑦ using algebra

$$\Rightarrow A_e(s) = \frac{G(s) \cdot A(s)}{1 + A(s)F(s)} \quad \text{⑨}$$

Block Diagrams

SSM of ② $\Leftrightarrow$ system of equations in 's' (eg. ④ & ⑤)

$\Rightarrow$ block diagram

(eg. ⑧)

- SSM is symbolic $\Rightarrow$ good for insight
- but components are bi-directional $\Rightarrow$ bad for insight

- Can't go directly from a S.S.M.

to gains & impedances. (need system of equations first)

- Block diagrams provide insight because components are unidirectional $\Rightarrow$ feedback paths are obvious

- Can go directly from block diagrams to gains & impedances (using Mason's gain formula)

- Helps in conceptually understanding ckt's.

- eg. Gain margin & Phase margin tools were inherently developed using block diagrams.

(Need to know how those tools were developed in order to know their limitations. eg. -ve PM.

may be stable & +ve PM may be unstable)


- Block Diagrams work well in discrete time too.

- Feedback is clearly seen in block diagrams eg. Gd which is a feedback + feedforward cap. is difficult to understand just from ckt's.

REC #4

JAN 17 08

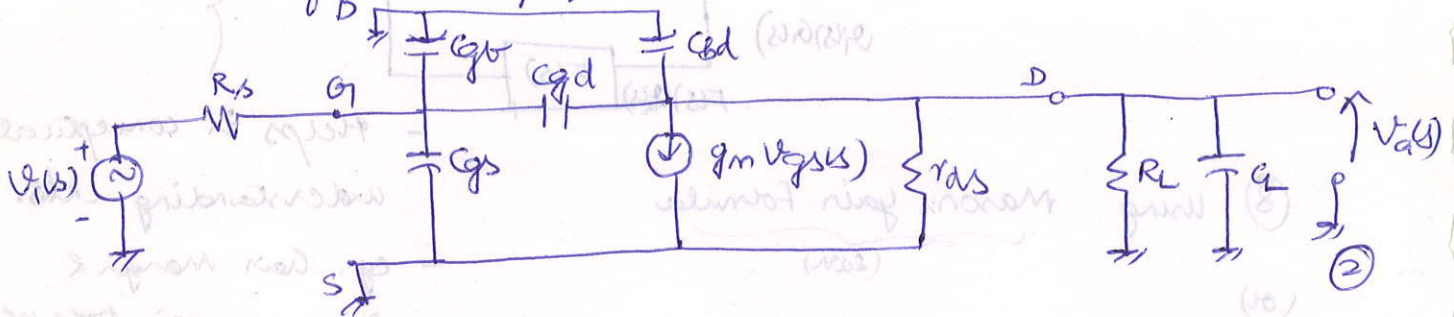
(Still numbering system from Lec #3)
SSM of B CS Amplifier (Recall from last time)



Last time found,

$$v_{gs}(s) = -F(s) v_o(s) + G(s) v_i(s) \quad (7)$$

$$v_o(s) = A(s) v_{gs}(s)$$

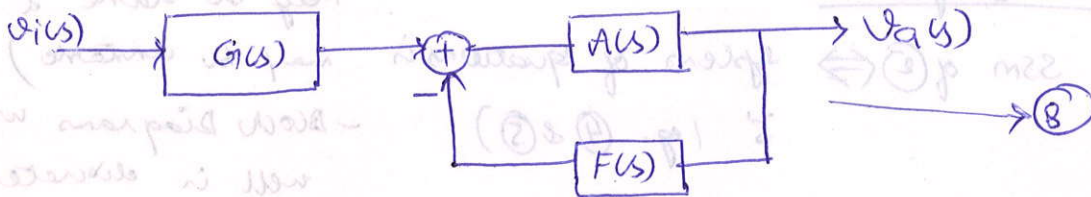

$$\frac{v_o(s)}{v_i(s)} = A_v(s) = \frac{G(s) A(s)}{1 + A(s) F(s)} \quad (8)$$

Recall: stability (for a causal system, which is usually the case in ckt. design)

$\Rightarrow$ no poles in RHP.

$\Rightarrow$ "stability" $\Leftrightarrow A(s) F(s) \neq -1$ for any s_0

wt $\text{Re}\{s_0\} \geq 0 \rightarrow$ i.e. on imaginary axis or R.H.P.

(assumes $F(s) \neq 0$ and no poles of $A(s)$ is a zero of $F(s)$)

($A(s) F(s)$ can be -1 for s in L.H.P. but not on imaginary axis or R.H.P.)

$s = -2 + j\omega$

First consider $A_{vo} = A_v(j\omega) \Big|_{\omega=0}$ "DC gain"

$$A_{vo} = \frac{G_v(j\omega) A_v(j\omega)}{1 + A_v(j\omega) F_v(j\omega)} \Big|_{\omega=0}$$

$$F_v(j\omega) \Big|_{\omega=0} = 0$$

($Z_{eqd} = 0$ @ 100 freq.)

(makes sense because $F(s)$ represents feedback through g_d)

$$\Rightarrow A_{vo} = -g_m R_L' \quad \text{--- (10)}$$

Now consider poles & zeros: let $H_v(j\omega) = \frac{A_v(j\omega)}{A_{vo}}$

$$\therefore A_v(j\omega) = A_{vo} H_v(j\omega)$$

(normalised x gain)

$$\textcircled{6} \& \textcircled{9} \Rightarrow H_v(s) = \frac{1 - s/z_1}{1 + a_1 s + a_2 s^2}$$

$$\left(\text{where } z_1 = \frac{g_m}{C_{gd}} ; a_1 = R_s [C_{gs}' + C_{gd} (1 + g_m R_L')] + R_L' (C_{gd} + C_a) \right)$$

$$a_2 = R_s R_L' [C_a C_{gs}' + C_d C_{gd} + C_{gs}' C_{gd}]$$

$$\therefore A_v(s) = A_{vo}(s) \left[\frac{1 - s/z_1}{(1 - s/p_1)(1 - s/p_2)} \right]$$

Usually, device parameters


$\Rightarrow a_1^2 > 4a_2$ for C.S. amp.

$\Rightarrow p_1 \& p_2$ are real.

c/b. C.S.A by itself
won't generally ring)

$$\left. \begin{aligned} \text{where } p_1 &= \frac{-a_1 \pm \sqrt{a_1^2 - 4a_2}}{2a_2} \\ p_2 &= \frac{-a_1 - \sqrt{a_1^2 - 4a_2}}{2a_2} \end{aligned} \right\} \textcircled{11}$$

(Always check units)

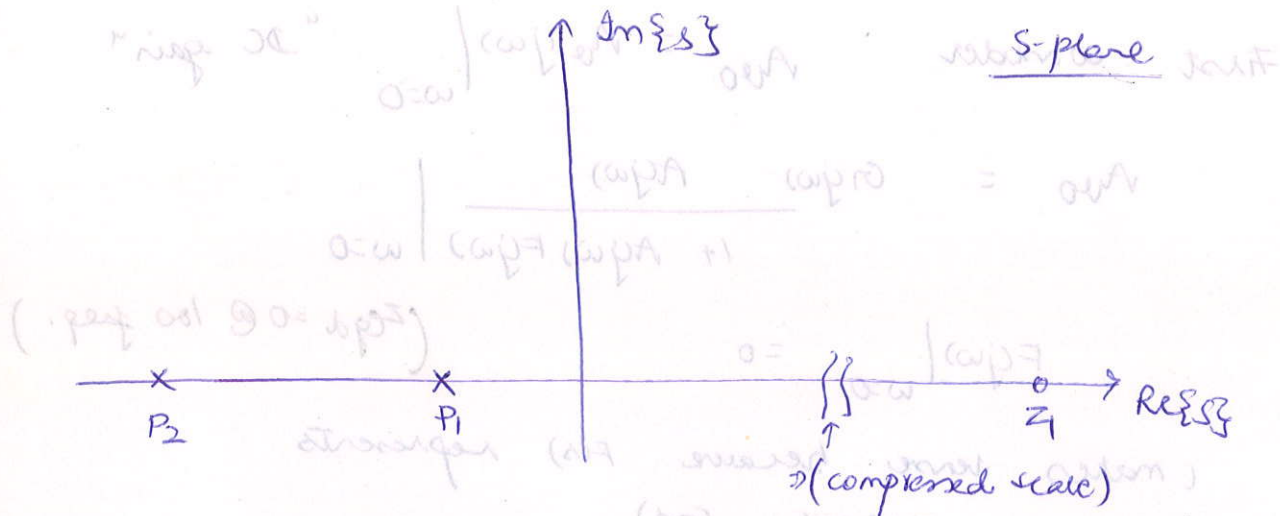

eg Using ③ (from last time) w/ $R_L = 10k\Omega$, $R_S = 5k\Omega$,

gives $A_{vo} = -15.5$, $f_{z1} = \frac{Z1}{2\pi} = 13.5 \text{ GHz}$

$f_{p1} = \frac{|P1|}{2\pi} = 56 \text{ MHz}$, $f_{p2} = \frac{|P2|}{2\pi} = 860 \text{ MHz}$.

(Easier to calculate
is rad/s, easier to

$\left. \begin{matrix} |P1| \ll |P2| \\ |P1| \ll |Z1| \end{matrix} \right\} \Rightarrow P1 = \text{dominant pole. (think is poles/s or Hz)}$

$\Rightarrow |A_{v(j\omega)}| \approx A_{vo} \left(\frac{1}{1 + j\omega/(2\pi \times 56 \text{ M})} \right)$

valid for $\omega \leq f_{p2} \cdot 2\pi$

$\Rightarrow 3\text{dB BW} = 56 \text{ MHz}$

Now consider ① w/ capacitor C_C connected between D and G.

$\Rightarrow C_C$ is parallel w/ C_{gd} is ②

$\Rightarrow$ all equations so far hold if C_{gd} is replaced

by $C = C_{gd} + C_C$.


Can show using ① and ② (exercise)

$P1 \approx - \frac{1}{(C_C + C') R_L' + (C_{gs}' + C') R_S + g_m R_S R_L' C'}$ ⑬

$\approx - \frac{1}{C_C R_L'}$ for large R_S & R_L

$$P_2 \approx \frac{-g_m C'}{C_d C_{gs}' + C' (C_d + C_{gs}')} \quad \frac{-g_m}{C_d + C_{gs}'} \quad \text{if } C_d' \gg C_d$$


$$Z_1 = \frac{g_m}{C_{gs}' C'}$$

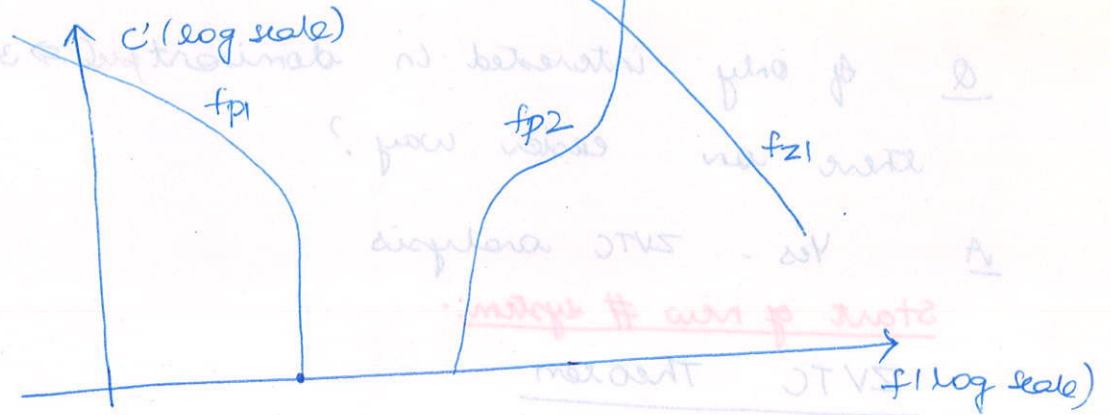

$\therefore$ Increasing C' splits poles but moves zero close to origin

Reset Number System

Zero Value Time Constant Analysis :-

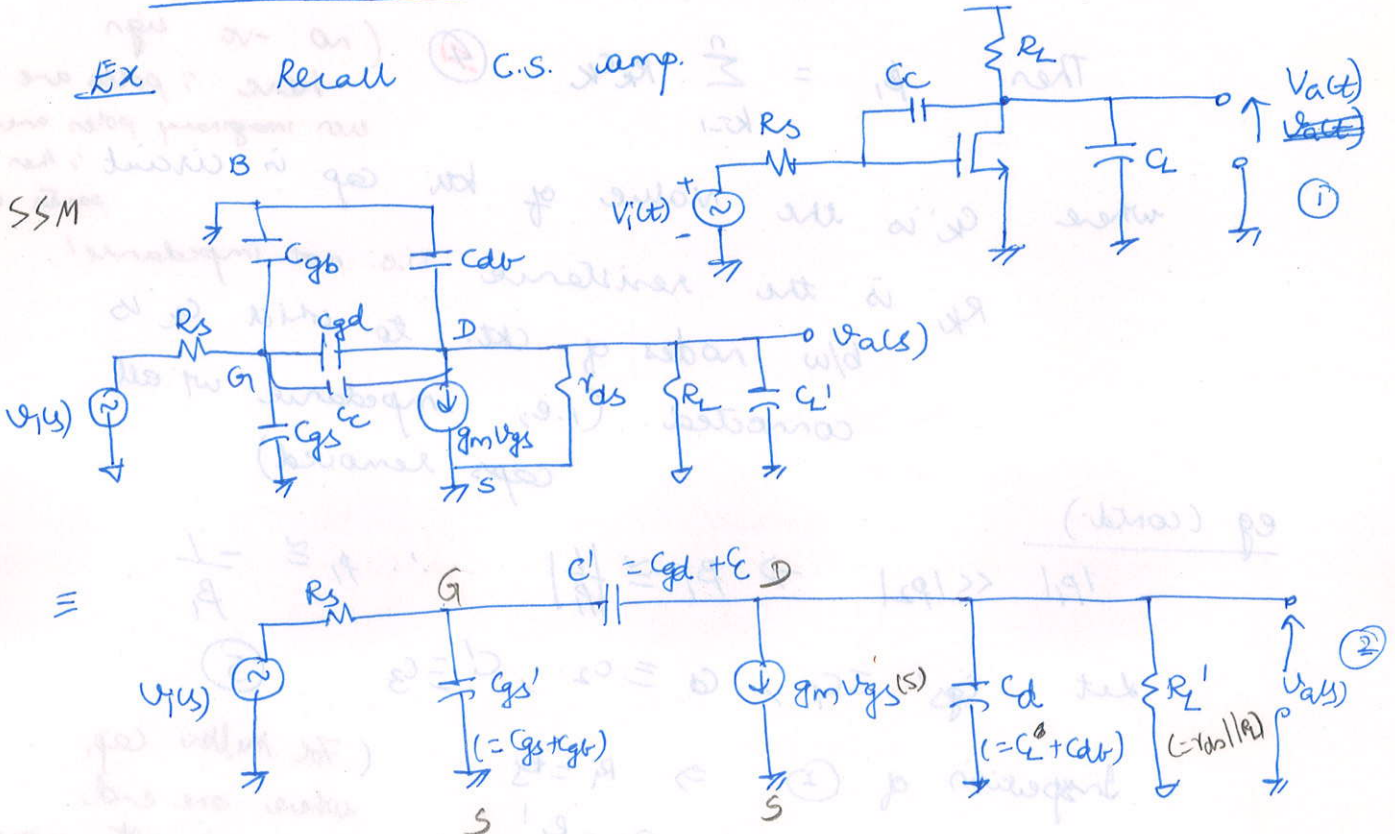

Last time, hard work $\Rightarrow p_1 \approx \frac{-1}{(C_d+C)R_L + (C_g' + C')R_S + g_m R_S R_L' C'}$

$p_1 = \text{dominant pole}$ so $3\text{dB BW} = \frac{|p_1|}{2\pi}$

③

Q If only interested in dominant pole $\Rightarrow 3\text{dB BW}$ is there an easier way?

A Yes - ZVTC analysis

Start of new # system:

ZVTC Theorem

Consider a circuit that contains only sources, resistors and capacitors (i.e. no inductors) and poles $p_1, p_2, \dots, p_n$ where $p_k \neq 0$

$$\text{Let } \beta_1 = - \sum_{k=1}^n \frac{1}{p_k}$$

$$\text{Then } \beta_1 = \sum_{k=1}^n R_k C_k \quad (4)$$

(no -ve sign here "poles are -ve" even imaginary poles are fine "then imaginary parts cancel")

where C_k is the value of k^{th} cap in circuit
 R_k is the resistance b/w nodes of ckt. to which C_k is connected (i.e., impedance w/ all caps removed) (i.e. not impedance)

eg (contd.)


$$|p_1| \ll |p_2| \Rightarrow \beta_1 \approx \left| \frac{1}{p_1} \right| \therefore p_1 \approx -\frac{1}{\beta_1}$$

$$\text{Let } C_{gs}' \equiv C_1, C_d \equiv C_2, C' \equiv C_3 \quad (5)$$

$$\text{Inspection of (2)} \Rightarrow R_1 = R_S, R_2 = R_L'$$

(For Miller cap, where one end of cap is not grounded then need to modify theorem)

To find R_3 , use:

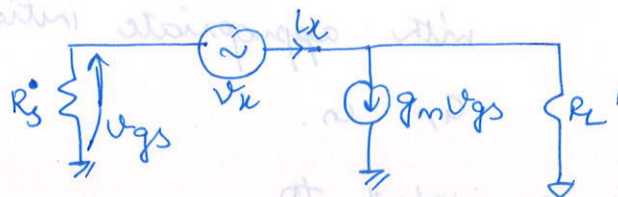

$$\Rightarrow v_{gs} = -i_x R_3$$

$$v_x = (i_x - g_m v_{gs}) R_L' - v_{gs}$$

$$\Rightarrow R_3' = R_L' + R_s + g_m R_L' R_s$$

$$(4) \Rightarrow P_1 \approx \frac{-1}{R_s C_{gs}' + R_L C_d + (R_L' + R_s + g_m R_L' R_s) C'}$$

= (3) from last time.

L&C #5

JAN 2018

ZVTC Theorem (contd.) (same # system)


PROOF:-

Have:

Impulse:

$$v_i(t) = \delta(t)$$

$$V_i(s) = 1$$

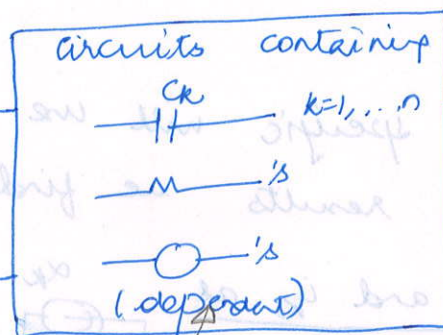


Impulse Response

$$v_a(t) = g(t)$$

$$(V_a(s) = G(s))$$

(2)

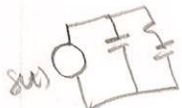


For calculating P_1 & C_1 we need to turn off independent sources

where $G(s) = A_0 \frac{p(s)}{(1-s/p_1)(1-s/p_2) \dots (1-s/p_n)}$ $\leftarrow$ some polynomial

Note: In (2), $v_i(t) = \delta(t)$ sets initial condition of each capacitor C_k $k=1, \dots, n$. After $t=0$, $v_i(t)=0$ (At least one cap will get charged)


$\Rightarrow g(t) =$ transient of (2) w/ $v_i(t) = 0$ but with appropriate initial conditions on $G, R, C, \dots$

$\therefore$ (2) is equivalent to

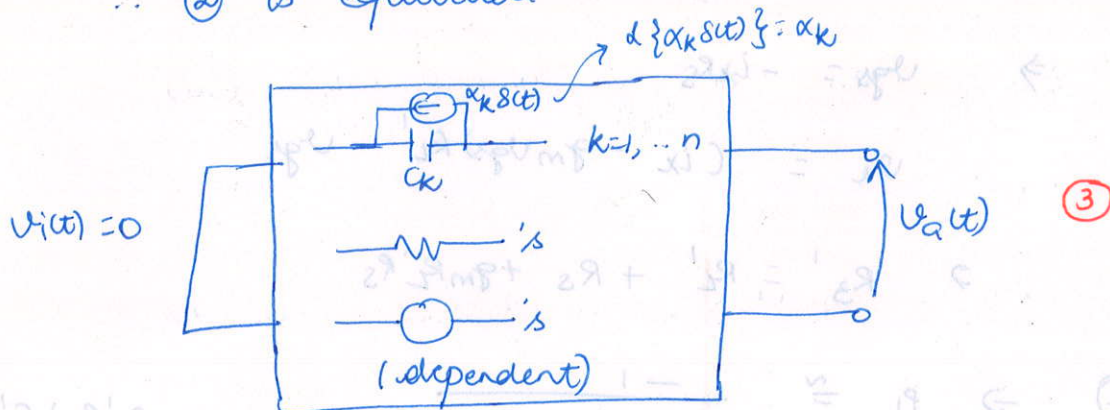

E.g. s.s.m. of G.S. amplifier (last time)

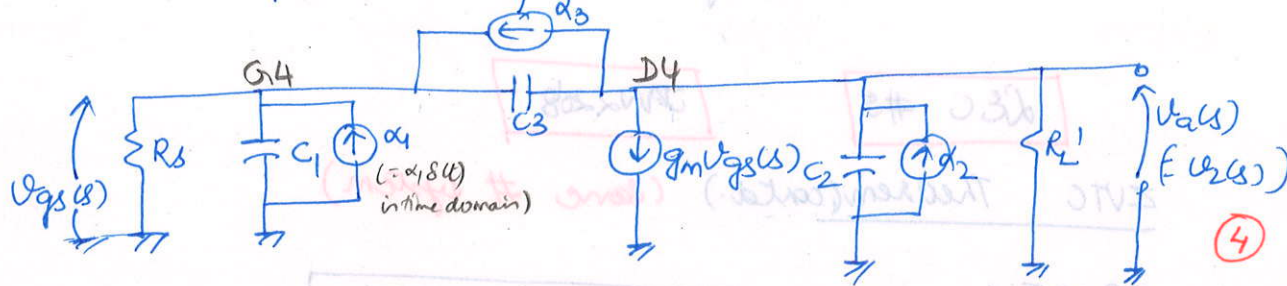
w/ $v_i(t) = s(t)$ produces time $v_o(t)$ as



NOTE:

To be specific will use (4) in place of (3) for today. But all results we find generalize to (3).

Define v_k and i_k as

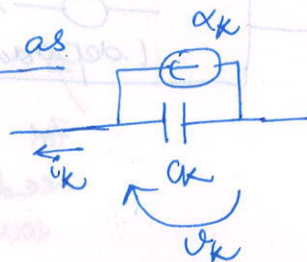

$$\therefore i_k(s) = \alpha_k - v_k(s) s C_k \quad (5)$$

KCL @ any node $\Rightarrow$ equation of the form:

$$d_1 i_1(s) + d_2 i_2(s) + d_3 i_3(s) + g_1 v_1(s) + g_2 v_2(s) + g_3 v_3(s) = 0$$

where $d_k = 1, 0, \text{ or } -1$

(corresponding to current entering, not entering/leaving & leaving a node)

and $g_k =$ some conductance

e.g. k_{11} @ gate of ④:

$$-i_1(s) - i_3(s) + \frac{1}{R_s} v_1(s) = 0 \quad \text{where is } v_1(s)?$$

have only $v_g(s)$

Can solve all the equations of this form to get:

$$i_1(s) = a_{11} v_1(s) + a_{12} v_2(s) + a_{13} v_3(s)$$

$$i_2(s) = a_{21} v_1(s) + a_{22} v_2(s) + a_{23} v_3(s)$$

$$i_3(s) = a_{31} v_1(s) + a_{32} v_2(s) + a_{33} v_3(s)$$

⑥
where
 $a_{jk} =$
some
conductance

Note: To force ⑥ to be linearly independent,

may need to add tiny resistors in series

w/ some of the caps (conceptually, not physically)

("tiny" $\Leftrightarrow$ small enough to have negligible effect on (ckt.))

In matrix notation, ⑥ is $\underline{i}(s) = \underline{A} \underline{v}(s)$

$$\underline{i}(s) = \begin{bmatrix} i_1(s) \\ i_2(s) \\ i_3(s) \end{bmatrix}_{3 \times 1}, \quad \underline{A} = \begin{bmatrix} a_{11} & a_{12} & a_{13} \\ a_{21} & a_{22} & a_{23} \\ a_{31} & a_{32} & a_{33} \end{bmatrix}_{3 \times 3}, \quad \underline{v}(s) = \begin{bmatrix} v_1(s) \\ v_2(s) \\ v_3(s) \end{bmatrix}_{3 \times 1}$$

Using ⑤: $\begin{bmatrix} \alpha_1 \\ \alpha_2 \\ \alpha_3 \end{bmatrix} = \begin{bmatrix} (a_{11} + sC_1) & a_{12} & a_{13} \\ a_{21} & (a_{22} + sC_2) & a_{23} \\ a_{31} & a_{32} & (a_{33} + sC_3) \end{bmatrix} \underline{v}(s)$

(Real life: C_1, C_2, C_3 3 caps, 2 poles)

Call $\underline{\alpha}$ Call $\underline{B}$

Recall "Cramer's Rule"

$$\Rightarrow v_k(s) = \frac{\Delta_k(s)}{\Delta(s)} \quad \text{where } \Delta(s) = \det(\underline{B}) \quad (= \text{polynomial in } s)$$

$\Delta_k(s) = \det(\underline{B} \text{ with } k\text{th column replaced by } \underline{\alpha})$

Note: $\Delta_2(s) = \Delta_2(s)$ in (4), so $G(s) = \frac{\Delta_2(s)}{\Delta(s)}$

(i.e. we can calculate impulse response from Cramer's rule)

We know denominator of $G(s)$ has form $b_0 + b_1 s + b_2 s^2$

$$= b_0 (1 + \beta_1 s + \beta_2 s^2)$$

(Because of pole-zero cancellation, we have 2nd order polynomial in real life rather than 3rd order polynomial)

$$= b_0 (1 - s/p_1) (1 - s/p_2)$$

Algebra $\Rightarrow \beta_1 = -\sum_{k=1}^n 1/p_k, \quad n=2$

true for any $n \geq 1$

(7), (8), defn. of $\det(B) \Rightarrow b_0 = \Delta(s) \Big|_{G=C_2=C_3=0} = \Delta(0)$ (9)

& $b_0 \beta_1 s \equiv b_1 s = h_1 s_1 + h_2 s_2 + h_3 s_3$

where h_1, h_2, h_3 are real #'s, i.e. $\in \mathbb{R}$

Let $\Delta_{ij} = (-1)^{i+j} \det(B_{ij})$ where $B_{ij} = B$ with its row i & j th column deleted.

Can expand $\det(B)$ as

$$\Delta(s) = (a_1 + s_1) \Delta_{11} + a_{21} \Delta_{21} + a_{31} \Delta_{31}$$

inspection of (7) $\Rightarrow C_1$ only occurs in 1st term

$$h_1 = \Delta_{11} \Big|_{C_2=C_3=0} = \Delta'_{11}(0)$$

Similarly, $h_2 = \Delta_2(0)$, $h_3 = \Delta_3(0)$

$$\therefore \textcircled{1} \Rightarrow \beta_1 = \frac{\Delta_{11}(0)}{\Delta(0)} C_1 + \frac{\Delta_{22}(0)}{\Delta(0)} C_2 + \frac{\Delta_{33}(0)}{\Delta(0)} C_3$$

Now set $C_1 = C_2 = C_3 = 0$

& $i_2 = i_3 = 0$ to get

$$\begin{bmatrix} i_1 \\ 0 \\ 0 \end{bmatrix} = \underline{A} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \end{bmatrix}$$

Cramer's Rule $\Rightarrow$ $i_1 = i_1 \det \begin{pmatrix} a_{22} & a_{23} \\ a_{32} & a_{33} \end{pmatrix}$
 $\det(\underline{A})$

$$= i_1 \frac{\Delta_{11}(0)}{\Delta(0)} \quad \text{by defn.}$$

$$= R_1 = \frac{\Delta_{11}(0)}{\Delta(0)}$$

$C_1 = C_2 = C_3 = 0$
 $i_2 = i_3 = 0$

Similarly for R_2 and R_3

$$\therefore \beta_1 = R_1 C_1 + R_2 C_2 + R_3 C_3$$

$$\beta_1 \approx RC$$


- 1) One RC should dominate
- 2) One pole should dominate

$$s = \frac{1}{RC} (2\sigma - p_1) + \frac{1}{RC} (2\sigma - p_2) + \dots$$

$$\left[\frac{1}{s^2 + 2\zeta\omega_n s + \omega_n^2} \right] = \frac{1}{s^2 + 2\zeta\omega_n s + \omega_n^2}$$

Freq. Response of Common Gate (Casode) Stage

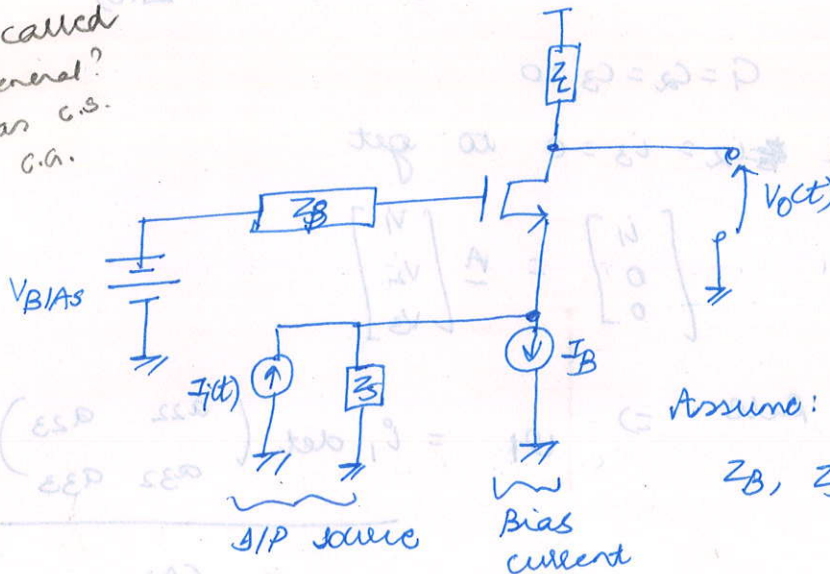
Is CG. called casode in general?
Thought it was C.S. followed by C.G.



Assume:

$$Z_B, Z_S, Z_L \equiv \text{[Symbol: Impedance in parallel with a capacitor]}$$

SSM:

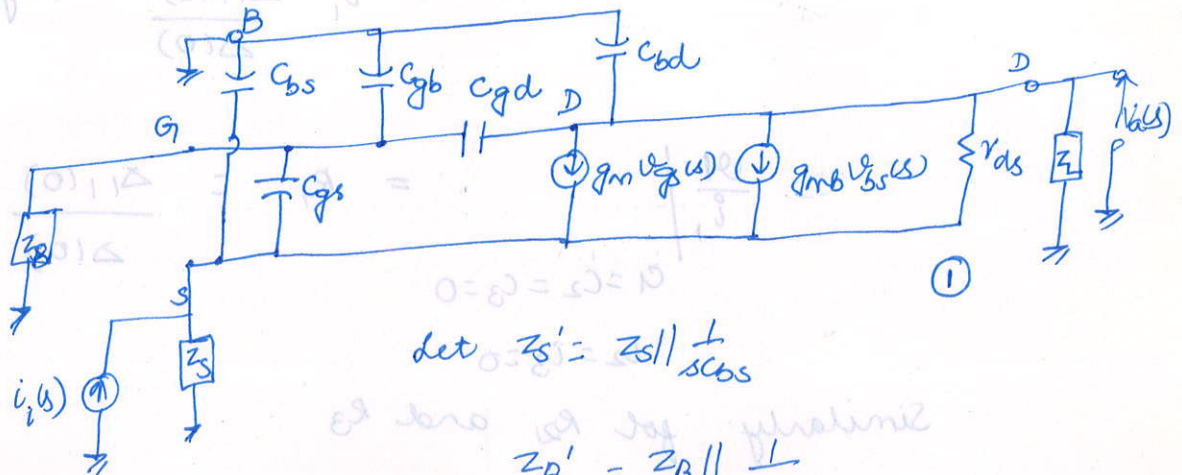

$$\text{let } Z_S' = Z_S \parallel \frac{1}{sC_{gs}}$$

$$Z_B' = Z_B \parallel \frac{1}{sC_{gb}}$$

$$Z_L' = Z_L \parallel \frac{1}{sC_{db}}$$

KCL @ G:

$$\frac{v_g}{Z_B'} + (v_g - v_d) sC_{gd} + (v_g - v_s) sC_{gs} = 0$$

$$\Rightarrow v_g = \left[\frac{1}{Z_B'} + s(C_{gd} + C_{gs}) \right]^{-1} [sC_{gs} v_s + sC_{gd} v_d] \quad \text{--- (2)}$$

all v(s)


KCL @ S:

$$v_s = \underbrace{\left[\frac{1}{z_s} + g_m + g_{mb} + \frac{1}{r_{ds}} + sC_{gs} \right]^{-1}}_{\text{call } b(s)} \left[i_i + (g_m + sC_{gs})v_g \right] + \frac{1}{r_{ds}}v_d \rightarrow (3)$$

KCL @ D:

$$v_d = \underbrace{\left[\frac{1}{z_d} + \frac{1}{r_{ds}} + sC_{gd} \right]^{-1}}_{\text{call } c(s)} \left[\left(\frac{1}{r_{ds}} + g_m + g_{mb} \right) v_s + (sC_{gd} - g_m)v_g \right] \rightarrow (4)$$

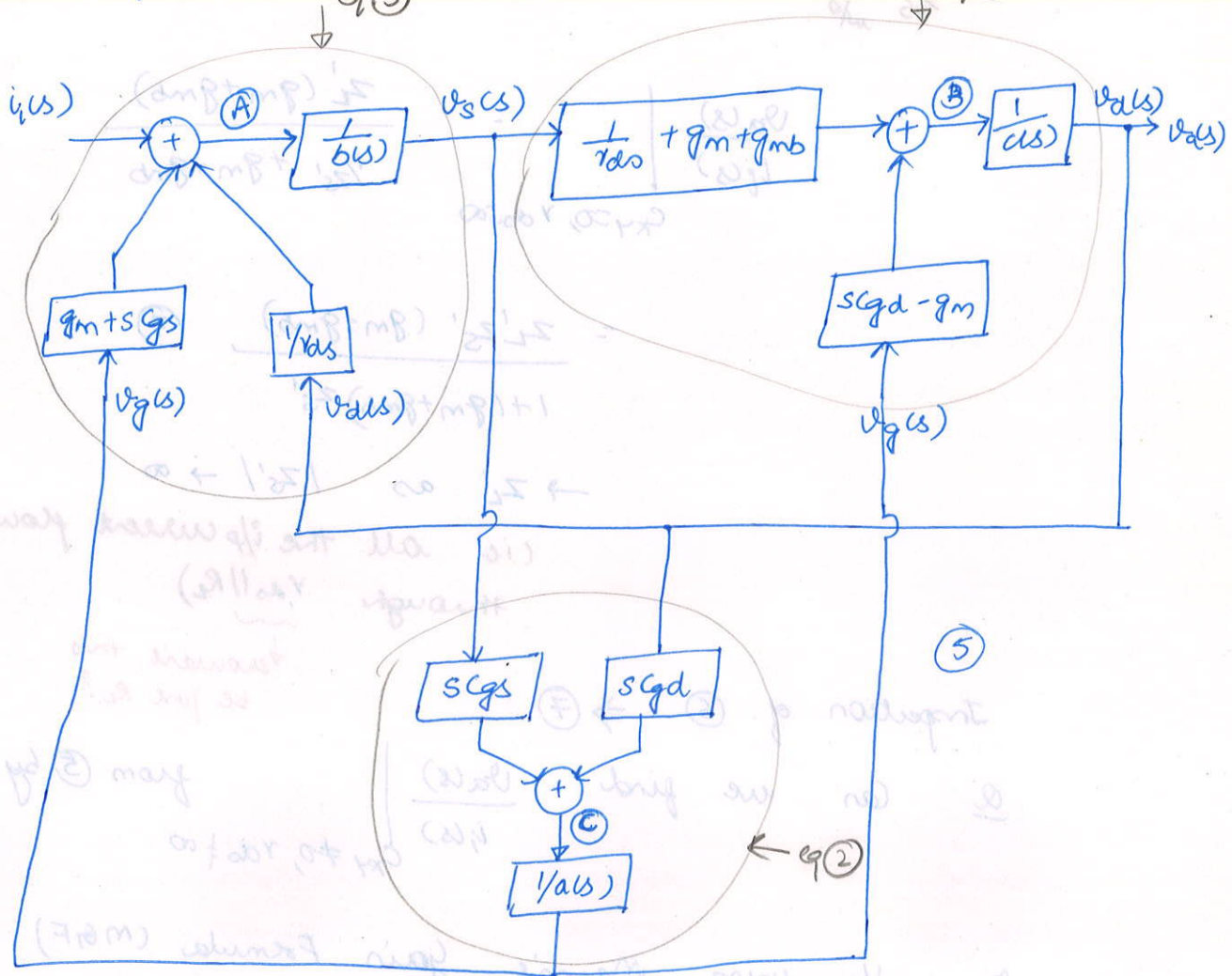Can generate "block diagram" from (2)-(4):



Observations:-

- 1) All blocks are unidirectional (in direction of arrows)
- 2) All feedback paths are from parasitic elements
i.e., if $C_{xy} = 0$ & $r_{ds} = \infty$, then no feedback loops)

With $C_{xy} = 0$, $r_{ds} = \infty$, ⑤ reduces to

$$i_i(s) \rightarrow \left[\frac{1}{b(s)} \right] \rightarrow [g_m + g_{mb}] \rightarrow \left[\frac{1}{c(s)} \right] \rightarrow v_o(s) \quad (6)$$

$$\equiv \frac{1}{\frac{1}{z_s'} + g_m + g_{mb}} \quad \equiv Z_L'$$

$z_s' = z_s$ caps into

$$\frac{v_o(s)}{i_i(s)} \bigg|_{C_{xy}=0, r_{ds}=\infty} = \frac{Z_L' (g_m + g_{mb})}{\frac{1}{z_s'} + g_m + g_{mb}}$$

$$= \frac{Z_L' z_s' (g_m + g_{mb})}{1 + (g_m + g_{mb}) z_s'} \quad (7)$$

$\rightarrow Z_L'$ as $|z_s'| \rightarrow \infty$

(i.e. all the i/p current flows through $r_{ds} || R_L$)

↓ should this be just R_L ?

Inspection of ⑥ $\Rightarrow$ ⑦

Q Can we find $\frac{v_o(s)}{i_i(s)} \bigg|_{C_{xy} \neq 0, r_{ds} \neq \infty}$ from ⑤ by inspection

A Yes, using Mason's Gain Formula (MGF)
(It applies to both digital & analog systems)

Application of MGF to ⑤:

(7.B) "4 loops": 1:

$$A \rightarrow B \rightarrow A$$

2:

$$A \rightarrow C \rightarrow A$$

3:

$$A \rightarrow C \rightarrow B \rightarrow A$$

4:


$$A \rightarrow B \rightarrow C \rightarrow A$$

5:

$$B \rightarrow C \rightarrow B$$

Note: All loops touch each other

(i.e. they share a common node)

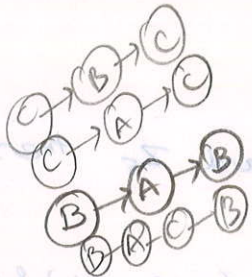

"Forward Paths":

$$1: A \rightarrow B \rightarrow \text{vd}$$

$$2: A \rightarrow C \rightarrow B \rightarrow \text{vd}$$

Note: deleting either path breaks all loops.

"Loop Gains":

$$L_1 = \left(\frac{1}{r_{as}} + g_m + g_{mb} \right) \frac{1}{r_{as} b(s) c(s)}$$

$$L_2 = s g_s (g_m + s g_s) \frac{1}{a(s) b(s)}$$

$$L_3 = s g_s (s g_d - g_m) \frac{1}{r_{as} a(s) b(s) c(s)}$$

$$L_4 = s g_d (g_m + s g_s) \left(\frac{1}{r_{as}} + g_m + g_{mb} \right) \frac{1}{a(s) b(s) c(s)}$$

$$L_5 = s g_d (s g_d - g_m) \frac{1}{a(s) c(s)}$$

"Path Gains":

$$P_1 = \left(\frac{1}{r_{as}} + g_m + g_{mb} \right) \frac{1}{b(s) c(s)}$$

$$P_2 = s g_s (s g_d - g_m) \frac{1}{a(s) b(s) c(s)}$$

⑧

⑨

Part: MGF $\Rightarrow \frac{V_a(s)}{I_i(s)} = \frac{P_1 + P_2}{1 - L_1 - L_2 - L_3 - L_4 - L_5}$ (10)

(this case)

Can easily find $G(s) = \frac{V_a(s)}{I_i(s)}$ but it's really

messy to look at.

For negligible capacitance in Z_L , Z_B and Z_S then

$G(s) \cong \frac{\text{second-order poly}}{\text{Third-order poly}}$ ($a(s)$, $b(s)$ & $c(s)$ are first order polynomials)

(Call Full version of $G(s)$ (11))

have 3rd-order system w/ 2 zeros & 3 poles.

The good news: (11) = "exact" expression

The bad news: "Exact" expression is too complicated to give insight.

So what now?


Plug #s (i.e., frequencies and component values) into boxes in (5) and eliminate highly attenuated paths

eg Z_B usually arises from parasitics
- often $Z_B \neq 0$ causes stability problem in feedback applications

$V_{BIAS} = 0$, so can use bypass cap to reduce $|Z_B|$

Suppose $|Z_B| \cong 0$. Then $\left| \frac{1}{a(s)} \right| \cong 0$

and ⑤ becomes

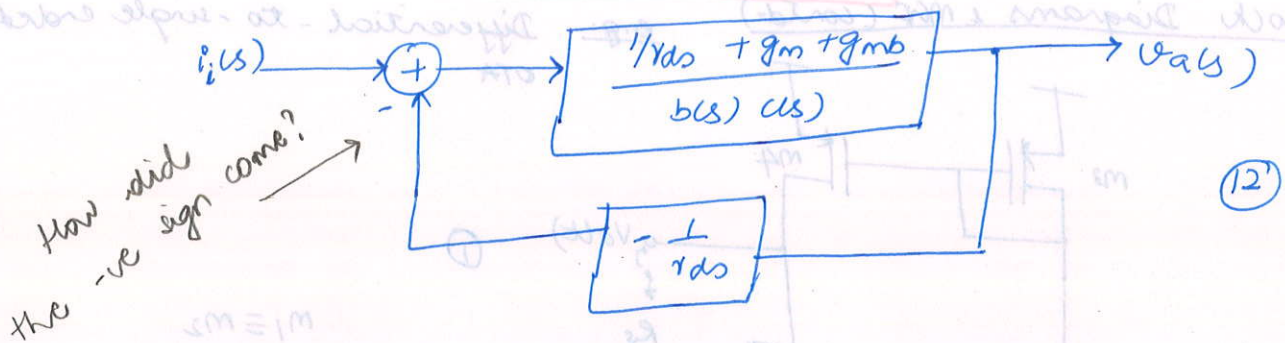

Now, MGF gives

$$G(s) \Big|_{Z_B=0} = \frac{1/r_{ds} + g_m + g_{mb}}{b(s) c(s)} \left[1 - \frac{1}{r_{ds}} \left(\frac{1/r_{ds} + g_m + g_{mb}}{b(s) c(s)} \right) \right]$$

Let $g_m' = g_m + g_{mb} (\approx 1.2 g_m)$, assume $g_m \gg \frac{1}{r_{ds}}$

Then

$$b(s) = \frac{1}{Z_s'} + g_m' + s C_{gs}$$

$$c(s) = \frac{1}{Z_L'} + \frac{1}{r_{ds}} + s C_{gd}$$

$$G(s) \Big|_{Z_B=0} = \frac{g_m'}{\left(\frac{1}{Z_s'} + g_m' + s C_{gs} \right) \left(\frac{1}{Z_L'} + \frac{1}{r_{ds}} + s C_{gd} \right) - g_m' / r_{ds}} \quad (13)$$

Sanity checks: 1) Units = $\frac{V}{I}$

$$2) A(j\omega) \Big|_{r_{ds}, Z_s = \infty} = Z_L'$$

⑬ $\Rightarrow$ 2nd order behavior, 2 poles, no zeros

$\Rightarrow$ always stable, denominator of ⑬ has form


$$\alpha_0 + \alpha_1 s + \alpha_2 s^2$$

$$\text{w/ poles} = \frac{-\alpha_1}{2\alpha_2} \pm \frac{1}{2\alpha_2} \sqrt{\alpha_1^2 - 4\alpha_0\alpha_2}$$

$\therefore \text{Re}\{\text{Poles}\} < 0$

Block Diagrams & MGF (Contd)

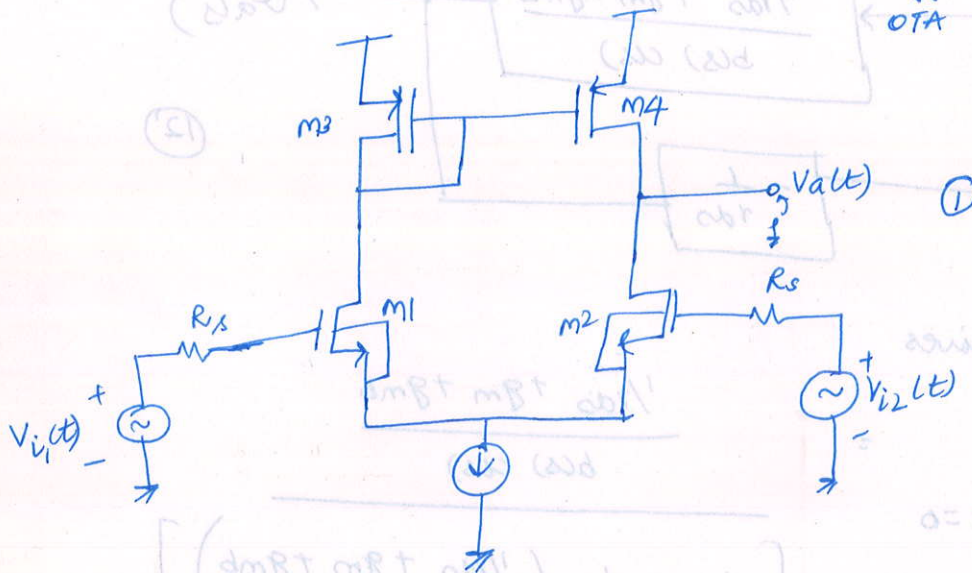e.g. Differential - to - single ended
OTA




$$M_1 \equiv M_2$$

$$M_3 \equiv M_4$$

(OTA generally means that op is from a high impedance node)

S.S.M. of ①:

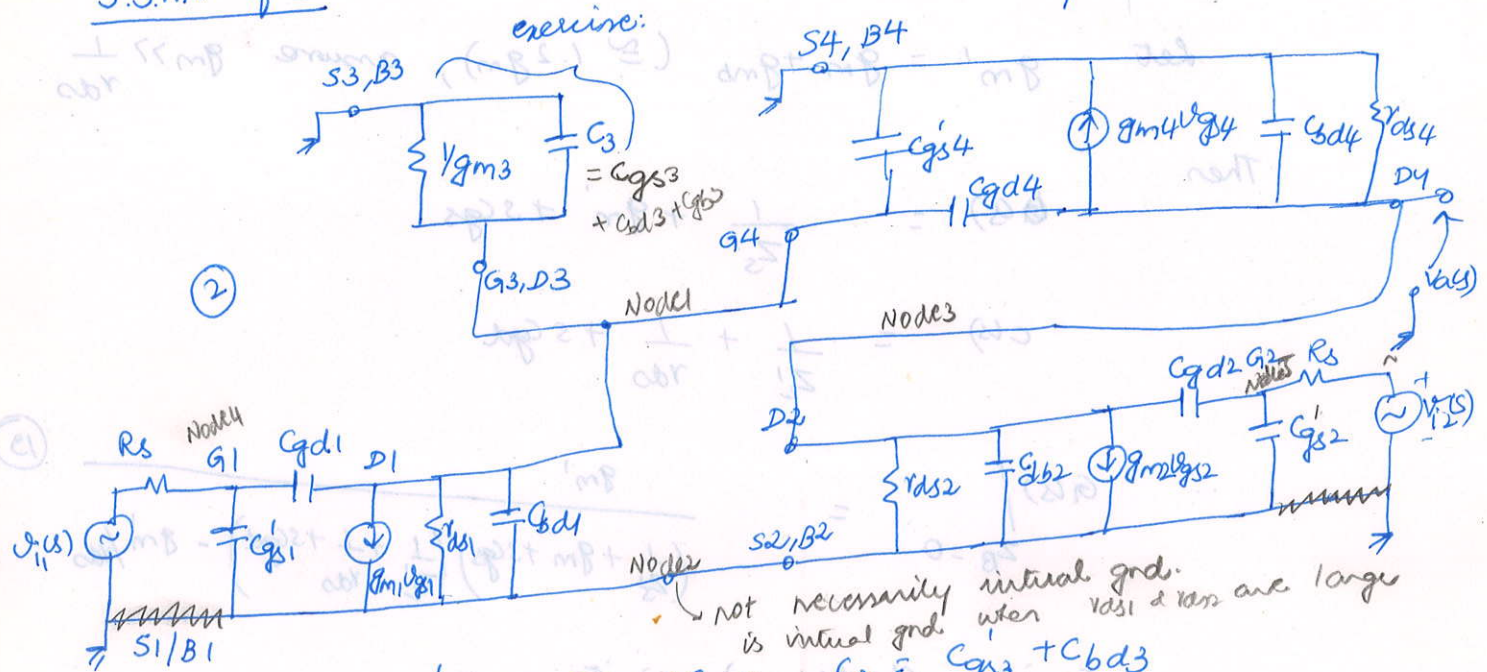

where $C_{gsi} = C_{gsi} + C_{gsi}$, $C_3 = C_{gs3} + C_{bd3}$

Want to analyze differential mode (DM) operation:

$$v_{i1} = \frac{v_{id}}{2}, \quad v_{i2} = -\frac{v_{id}}{2}$$

Assume $R_s = \text{negligible for analysis}$ (based on application this has to be determined)

Want block diagram (BD) containing nodes: ② - ③

$$v_{id}, v_{d1}, v_s \equiv v_{s1} = v_{s2}, v_a$$

KCL @ D1:

$$v_{d1} [g_{m3} + s(C_3 + C_{gs4})] + \frac{v_{d1} - v_s}{r_{ds1} \parallel C_{bd1}} + (v_{d1} - v_a) s g_{d1} + (v_{d1} - \frac{v_{id}}{2}) s g_{d1} + g_{m1} (\frac{v_{id}}{2} - v_s) = 0$$

What happened to r_{ds1} in v_{d1} ?
 $\therefore g_{m3} \gg \frac{1}{r_{ds1}} \Rightarrow g_{m3} + \frac{1}{r_{ds1}} \sim g_{m3}$

where " $r_x \parallel C_y$ " = $(\frac{1}{r_x} + s C_y)^{-1}$

$$\Rightarrow v_{d1} [g_{m3} + \frac{1}{r_{ds1}} + s(C_3 + C_{gs4} + C_{bd1} + C_{gd1} + C_{gd4})] - v_s [g_{m1} + \frac{1}{r_{ds1} \parallel C_{bd1}}] - v_a s g_{d1} + \frac{1}{2} v_{id} (g_{m1} - s g_{d1}) \frac{1}{\frac{1}{r_x} + s C_y} = 0$$

$\approx g_{m1} + s C_{bd1}$

$$\therefore \frac{v_{d1}}{v_{id}} = \frac{1}{a(s)} [v_s (g_{m1} + s C_{bd1}) + v_a s g_{d1} - \frac{1}{2} v_{id} (g_{m1} - s g_{d1})] \quad (3)$$

KCL @ D2:

$$\therefore v_a = \frac{1}{b(s)} [v_s (g_{m2} + s C_{bd2}) + v_{d1} (s g_{d1} - g_{m1}) + \frac{1}{2} v_{id} (g_{m2} - s g_{d2})] \quad (4)$$

where $b(s) = \frac{1}{r_{ds4} \parallel r_{ds2}} + s(C_{bd4} + C_{bd2} + C_{gd1} + C_{gd2})$


KCL @ S1, S2:

$$v_s = \frac{1}{c(s)} \left[\frac{v_{d1}}{r_{ds1} \parallel C_{bd1}} + \frac{v_a}{r_{ds2} \parallel C_{bd2}} \right] \quad (5)$$

where $c(s) = g_{m1} + g_{m2} + s(C_{gs1} + C_{gs2})$

Just this C_{gd4} ?
 How is C_{gd1} coming in?
 (Used $g_{m2} \gg \frac{1}{r_{ds2}}$)
 where is this used?
 used $m_1 = m_2$ & $m_3 = m_1$
 What happened to C_{bd1} & C_{bd2} ?

③ - ⑤ $\Rightarrow$ block diagram

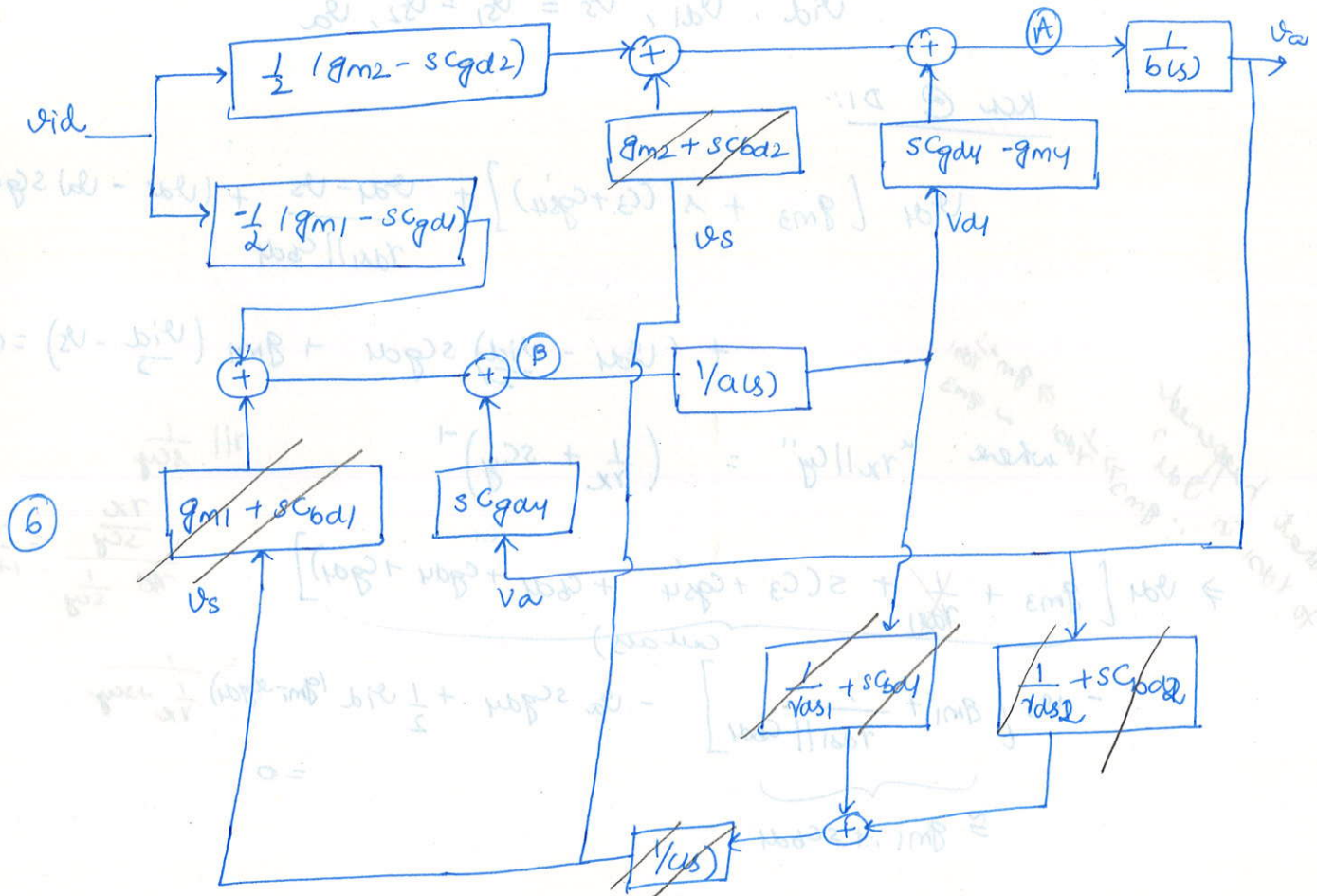

Let $P_1, P_2, \dots$ be the poles of $A_{v(s)} = \frac{v_{o(s)}}{v_{id(s)}}$ w/ $|P_1| \leq |P_2| \leq \dots$

⑥ Provided $\left| \frac{1}{r_{ds1,2}} + j\omega C_{gd1,2} \right|$ is sufficiently small that

$$|v_s(\omega)| \ll |v_d(\omega)|, \quad \text{for } |\omega| \leq |P_2| \quad (7)$$

can eliminate the feedback paths in ③.

(Asymmetry $\Rightarrow v_s \neq 0$)

We'll assume ⑦ holds for now, can later check assumption by testing with resulting value at p_2 .

Sanity check: Find $A_{v0} = A_v(\omega)|_{\omega=0}$ $\quad \omega=0 \Rightarrow s=0$

$$a(\omega) = g_{m3}$$

$$b(\omega) = \frac{1}{r_{ds2} \parallel r_{ds1} \parallel r_{ds4}}$$

$$\therefore \textcircled{6} \Rightarrow v_o = \left(\frac{1}{2} g_{m2} r_{ds2} \parallel r_{ds1} - \frac{1}{2} g_{m1} \frac{-g_{m4} r_{ds2} \parallel r_{ds1}}{g_{m3}} \right) v_{id}$$

$$A_{vo} = g_{m1} r_{as2} || r_{as4}$$

Loop: (A) → (B) → (A) Forward paths: 1) $v_{id} \rightarrow (A) \rightarrow v_o$

2) $v_{id} \rightarrow (B) \rightarrow (A) \rightarrow v_o$

$$P_1 = \frac{g_{m2} - sC_{gd2}}{2b(s)}$$

$$P_2 = \frac{(g_{m1} - sC_{gd1})(-sC_{gd4} + g_{m4})}{2a(s)b(s)}$$

$$4 = \frac{sC_{gd4}(sC_{gd4} - g_{m4})}{a(s)b(s)}$$

$$MAF \Rightarrow A_v(s) = \frac{P_1 + P_2}{1 - 4}$$

$$= \frac{1}{2} \frac{a(s) (g_{m2} - sC_{gd2}) + (g_{m1} - sC_{gd1})(g_{m4} - sC_{gd4})}{a(s)b(s) - sC_{gd4}(sC_{gd4} - g_{m4})} \quad (8)$$

⇒ 2 zeros, 2 poles

2nd-order ⇒ Can easily find poles & zeros but results give little insight

Instead, note: feedback depends on sC_{gd4} (no miller effect, why?)

Usually $g_{m4} \ll g_{s1} - C_{gd1}$
 ∴ Taking $sC_{gd4} \approx 0$ in (8) = reasonable approx.

∴ gain of M_4 is 100
 if $A_3 \approx 0$ then no miller effect on M_4

$$Now \quad MAF \Rightarrow A_v(s) = \frac{P_1 + P_2}{1 - 4} \approx 0 = \text{2nd order poly } a(s)b(s)$$

$$= \frac{g_{m1} (r_{ds2} || r_{ds4})}{(1-s/p_1) (1-s/p_2)}$$

where $p_1 = \frac{-1}{(r_{ds2} || r_{ds4}) C_2}$, $p_2 = \frac{-g_{m3}}{C_1}$

where $C_1 = C_{gs3} + C_{bd3} + C_{gs4} + C_{bd4} + C_{gd4}$

$$C_2 = C_{bd2} + C_{bd4} + C_{gd2} + C_{gd4}$$

C_1 and C_2 have same order of magnitude

$r_{ds2} || r_{ds4} \gg 1$ (typ.) $\Rightarrow p_1 = \text{dominant pole}$

$p_2 = \text{non-dominant pole}$
 (this may not be true for sub-90nm processes)

Observation:-

$1/g_{m3} = \text{resistance to s.s. grd. @ } D_1 \text{ (2)}$

$C_1 = \text{cap to " " " "}$

(3) $(r_{ds2} || r_{ds4}) = \text{resistance to s.s. grd @ } D_2 \text{ (2)}$

$C_2 = \text{cap. to " " " "}$

$\therefore$ In (2) could have found p_1 & p_2 by calculating

R_i, C_i where $R_i = \text{res. to } \overset{\text{s.s.}}{\wedge} \text{ground @ node } i$

$C_i = \text{cap to } \overset{\text{s.s.}}{\wedge} \text{" " " "}$

Then $p_1 = \frac{-1}{\text{largest } \{R_i C_i\}}$, $p_2 = \frac{-1}{\text{next largest } \{R_i C_i\}}$

Q: Coincidence?

A: No, This method is reasonable approx in many cases (where there is a unilateral condition).

Slang: Because of this, people often say that dominant pole occurs @ node D_2 and the non-dominant pole occurs @ node D_1 .

Full Version of MGF:

Block diagram defs:

- 1) "path": route through B.D. (in direction of arrows) connecting a pair of nodes.
- 2) "path gain": product of block gains along the path
- 3) "loop": path which starts and ends @ same node w/ no node along path encountered more than once.
- 4) "loop gain": path gain of loop.
- 5) "determinant" Δ : $1 - \sum (\text{all loop gains})$
 $+ \sum (\text{product of loop gains of all loop pairs w/ no common nodes})$
 $- \sum (\text{product of loop gains of all loop triples w/ no common nodes})$
 $+ \dots$
- 6) "Forward Path": path from i/p to o/p containing no full loops



Let $H = \frac{X_{out}}{X_{in}}$ where $X_{in} =$ i/p of B.D.
 $X_{out} =$ o/p of B.D.

Then $H = \frac{1}{\Delta} \sum_{k=1}^L P_k \Delta_k$ (M.G.F.) $\Delta =$ determinant
 $L =$ # of forward paths
 $P_k =$ kth forward path

Δ_k = determinant of B.D. that remains after deleting k th path, P_k

LEC #8 JAN 31 '08

Blackman's Impedance Relation

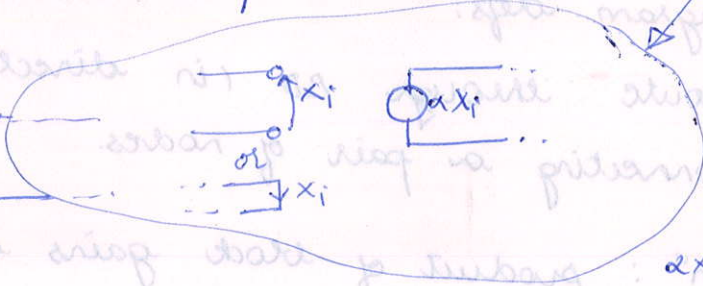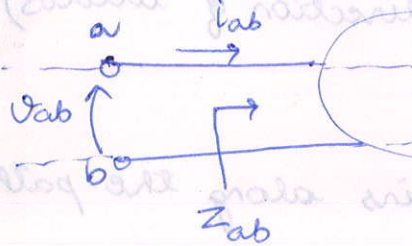

arbitrary s.s.m. ckt. containing ≥ 1 controlled source.

x_i = voltage or current

$\alpha x_i =$ " "

(eg. $x_i = v_{gs}$, $\alpha = g_m$)

$\therefore \alpha x_i$ = current

$$Z_{ab} = Z_{ab}^0 \frac{1+T_{SC}}{1+T_{OC}} \quad (1)$$

$$\left(\equiv \frac{V_{ab}(s)}{i_{ab}(s)} \right)$$

where $Z_{ab}^0 \equiv$ Impedance between a & b w/ controlled source removed ($\alpha=0$)

(determinant Δ - 1) Δ "transmission"

Loop gain of all (other) paths as the loop gain of all

Loop gain of all (other) paths as the loop gain of all

Forward path from v_{in} to v_{out} containing no feedback loops

Let $H = \frac{v_{out}}{v_{in}}$ where $v_{in} =$ o/p of B.D. $v_{out} =$ o/p of B.D.

Then $H = \frac{1}{\Delta} \sum_{k=1}^n P_k \Delta_k$ (M.C.T.) Δ = determinant Δ = # of forward paths P_k = the forward path

$$Z_{ab} = Z_{ab}^0 \frac{1+T_{sc}}{1+T_{oc}} \quad (1)$$

$$\left(\equiv \frac{V_{ab}(s)}{I_{ab}(s)} \right)$$

where $Z_{ab}^0 =$ Impedance $4w$ a & b w/ controlled source removed ($\alpha=0$)

(2) $T_{sc} = -\alpha \frac{x_i^0}{x_x}$ when $V_{ab}=0$ (a,b shorted)


and αx_i is replaced by an "independent test source", x_x

$T_{oc} \equiv$ same as T_{sc} except w/ $I_{ab}=0$ (a,b open circuit)

Note: If have >1 controlled sources, pick any one (call it the reference source)

eg 1 CS Amp.

Recall ssm:

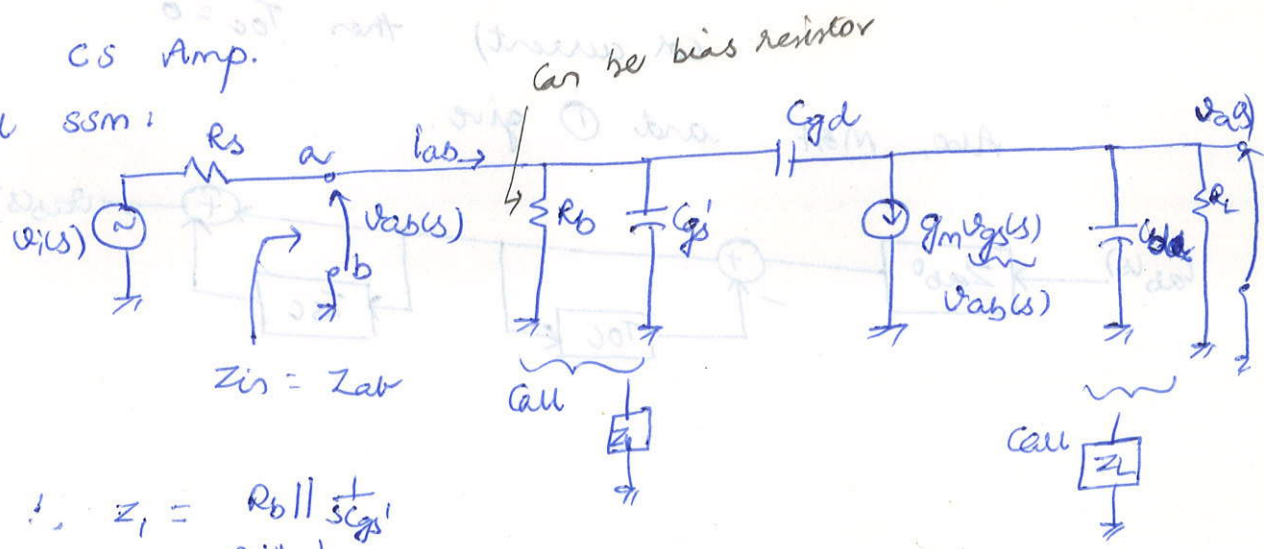

BIR : $\alpha = g_m$, $x_i = V_{ab}$, $x_o = i_x$

$$Z_{ab}^o = Z_1 \parallel \left(\frac{1}{sC_{gd}} + Z_L \right)$$

$$Z_1 (1 + sC_{gd} Z_L)$$

$T_{sc} = 0$ (because $x_i = V_{ab} = 0$)

$$T_{oc} = -g_m \cdot \frac{1}{i_x} \left[-i_x \underbrace{\left(Z_1 \parallel \left(Z_L + \frac{1}{sC_{gd}} \right) \right)}_{V_{ab}(s)} \cdot \frac{Z_L}{Z_L + \frac{1}{sC_{gd}}} \right]$$

$$= \frac{g_m Z_L Z_1}{Z_L + Z_1 + \frac{1}{sC_{gd}}}$$

(How is $T_{oc} = 0$ when $g_d = 0$?)

(note: $\rightarrow 0$ as $g_d \rightarrow 0$)

$\therefore \textcircled{1} \Rightarrow Z_{in} = Z_{ab}^o \cdot \frac{1}{1 + T_{oc}}$


$$Z_{in} = Z_1 \frac{1 + sC_{gd} Z_L}{1 + \left[Z_L + Z_1 (1 + g_m Z_L) \right] sC_{gd}} \quad \textcircled{2}$$


Miller Effect ✓

Observations:

- T_{oc} represents feedback around reference source
Why? def of $T_{oc} \Rightarrow$ if o/p of ref. source has no connection to its controlling voltage (or current) then $T_{oc} = 0$

Also, M&F and $\textcircled{1}$ give:

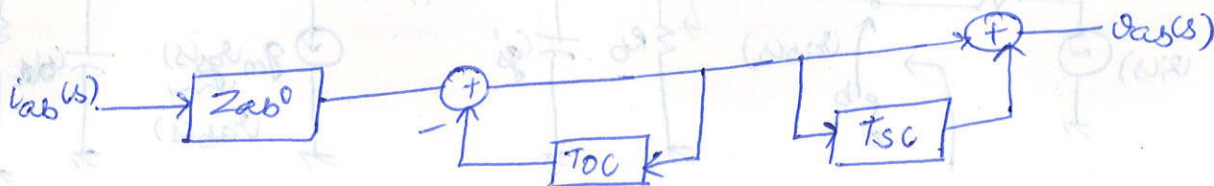


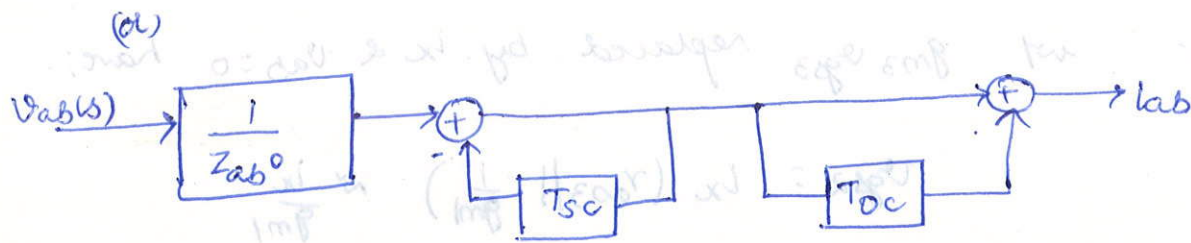

$\therefore T_{sc}$ also arises from a feedback path within the system.

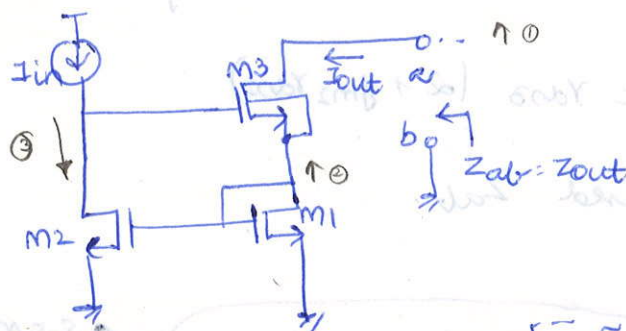- 2) Feedback can either increase or decrease Z_{ab}
 In case of C.S.A, $\downarrow$ reduced Z_{in} by miller effect of C_{gd}

eg 2 Wilson current mirror (low freq. analysis)



$$\downarrow V_{g3} = V_{a3} \quad \downarrow \frac{1}{g_{m3}}$$

$$\downarrow V_{d3} \uparrow, \text{ then } I_{d3} \uparrow$$


$$\Rightarrow V_{a1} \uparrow \Rightarrow V_{g2} \uparrow$$

$$\Rightarrow V_{d2} \downarrow \Rightarrow V_{g3} \downarrow$$

$$\Rightarrow I_{d3} \sim \text{const.}$$

low freq. s.s.m. (using $\frac{1}{g_m}$)

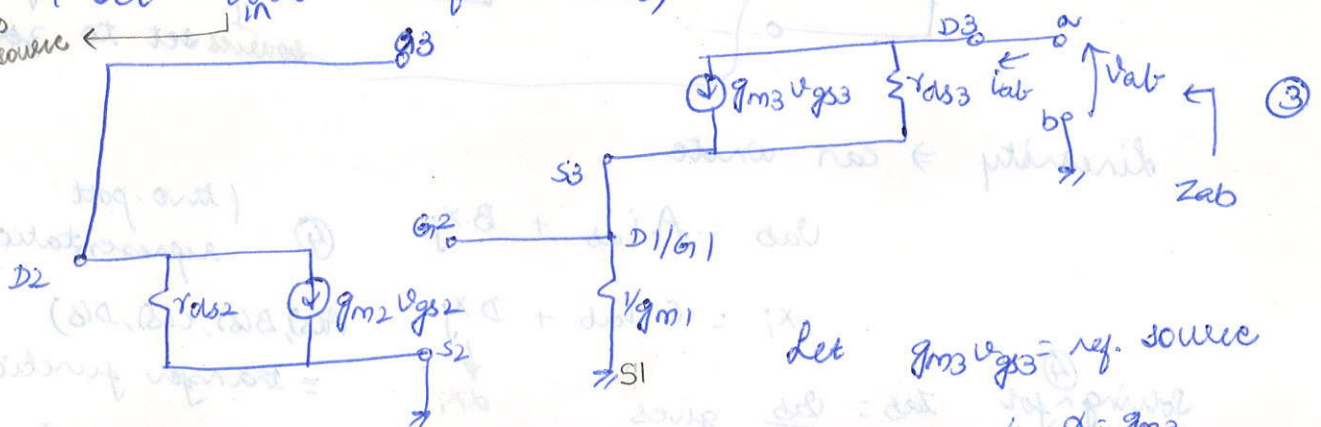1 Set $I_{in} = 0$ to find Z_{out}
 the indep. current source $\leftarrow$



Let $g_{m3} V_{gs3} = \text{ref. source}$

$$\therefore \alpha = g_{m3}$$

$$X_i = V_{gs3}$$

$$\text{Inspection of } \textcircled{3} \Rightarrow Z_{ab}^0 = r_{ds3} + \frac{1}{g_{m1}}$$

$$\approx r_{ds3}$$

$$\text{Inspection of } \textcircled{3} \Rightarrow I_{ab} = 0 \Rightarrow V_{gs2} = 0 \Rightarrow V_{gs3} = 0$$

$$\Rightarrow X_i = 0 \therefore T_{oc} = 0$$

$$T_{sc} = ?$$

Tsc:- w/ $g_{m3} v_{gs3}$ replaced by i_x & $v_{ab} = 0$ have:

$$v_{gs2} = i_x (r_{ds3} \parallel \frac{1}{g_{m1}}) \approx \frac{i_x}{g_{m1}}$$

KVL $\Rightarrow v_{gs2} + v_{gs3} = -g_{m2} v_{gs2} r_{ds2}$

$$\Rightarrow v_{gs3} = -\frac{i_x}{g_{m1}} (1 + g_{m2} r_{ds2})$$


$$\therefore T_{sc} = \frac{g_{m3}}{g_{m1}} (g_{m2} r_{ds2} + 1) = g_{m2} r_{ds2} + 1$$

(for $m_1 = m_2 = m_3$)

$$\therefore \textcircled{1} \Rightarrow Z_{ab} = r_{ds3} (2 + g_{m2} r_{ds2})$$

$\therefore$ Feedback increased Z_{ab} .

Proof of BIR:

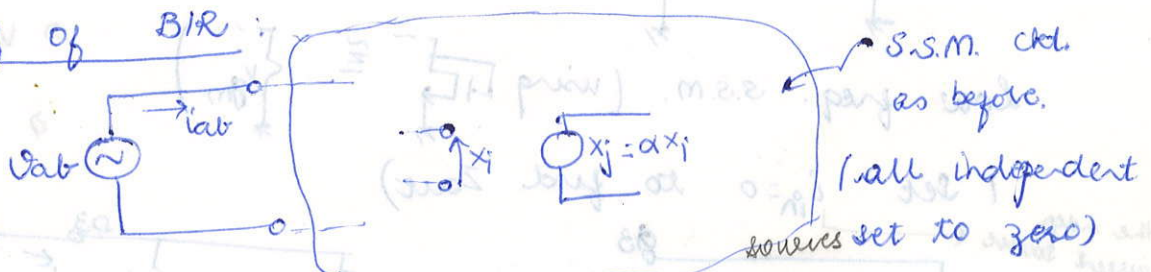

linearity $\Rightarrow$ can write

$$v_{ab} = A i_{ab} + B x_j$$

$$x_j = C i_{ab} + D x_j$$

(two-port representation)

$A(s), B(s), C(s), D(s)$

= transfer functions.

solving $\textcircled{4}$ for $Z_{ab} = \frac{v_{ab}}{i_{ab}}$ gives

$$Z_{ab} = A \frac{1 - \frac{\alpha (AD - BC)}{A}}{1 - \alpha D} \quad \textcircled{5}$$

$$\textcircled{4} \quad A = \left. \frac{v_{ab}}{i_{ab}} \right|_{x_j=0} = \text{def. of } Z_{ab}^0 \quad \textcircled{6}$$

Now suppose $V_{ab}=0$ and $x_j = x_x$ (independent of x_i):

Then (4) $\Rightarrow i_{ab} = \frac{-B}{A} x_x$

$x_i = C i_{ab} + D x_x$

$\Rightarrow -\alpha \frac{x_i}{x_x} = \frac{-\alpha (AD - BC)}{A}$ (7)


$\equiv T_{sc}$

Now suppose $i_{ab}=0$ and $x_j = x_x$ (indep. of x_i):

Then (4) similarly $\Rightarrow T_{oc} = -\alpha D$ (8)

$\therefore$ (5) - (8) $\Rightarrow Z_{ab} = Z_{ab0} \frac{1+T_{sc}}{1+T_{oc}}$

Asymptotic Gain Relation (A.G.R.)

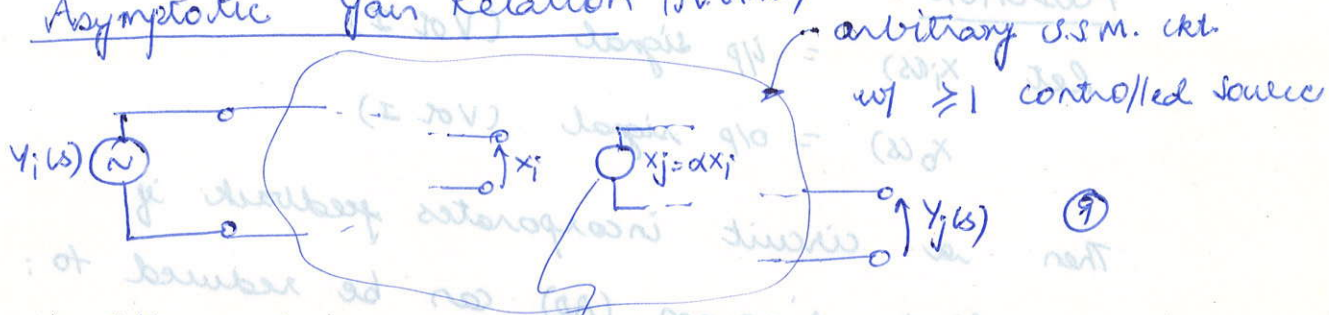

$x_i \neq Y_i$ reqd

(if $x_i = Y_i \Rightarrow$ no F.B.)

$\Rightarrow$ result is current
no F.B. $\therefore$ that node of i_i in c.s.a. is pegged @ $Y_i(s)$

any controlled source is ckt.
($\equiv$ "ref source")

$\left. \begin{matrix} x_i, x_j \\ Y_i, Y_j \end{matrix} \right\} = \text{voltages and/or currents}$

A.G.R. $A(s) \left(= \frac{Y_j(s)}{Y_i(s)} \right) = A_{\infty} \frac{T}{1+T} + A_0 \frac{1}{1+T}$ (10)

where $T = -\frac{\alpha x_i}{x_x}$ where $Y_i=0$ & x_j replaced by an "independent test source, x_x "


loop gain

$A_{\infty}(s) \equiv \left. \frac{Y_j(s)}{Y_i(s)} \right|_{\alpha \rightarrow \infty} \equiv \text{"asymptotic gain"}$

$A_0(s) = \left. \frac{Y_j(s)}{Y_i(s)} \right|_{\alpha=0} \equiv \text{"direct transfer term"}$

Observations: A_0

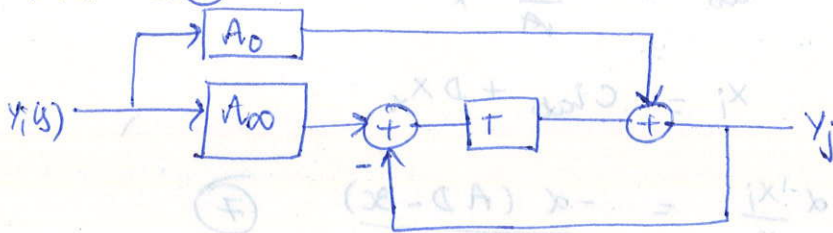MAG & (10) $\Rightarrow$ can redraw (9) as



$\Rightarrow$ large $T \Leftrightarrow$ feedback dominates behavior

$$A(s) \approx A_0(s)$$

$A_0(s)$ arises from forward path through feedback $Y(s)$.


LEC #9 FEB 12'08

FEEDBACK

Let $X_i(s) \equiv$ i/p signal (Vol I)

$X_o(s) \equiv$ o/p signal (Vol I)

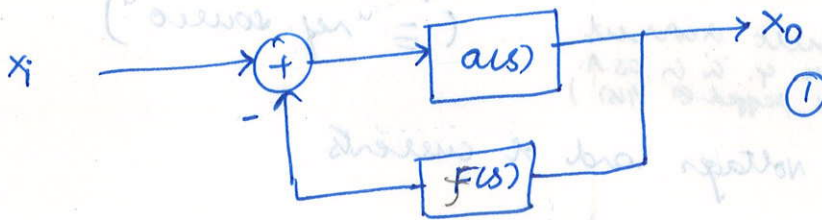
Then a circuit incorporates feedback if its block diagram (BD) can be reduced to:



$$\text{MGF + ①} \Rightarrow A(s) = \frac{a(s)}{1 + a(s)f(s)} \quad \text{②}$$

$$\text{where } A(s) \triangleq \frac{X_o(s)}{X_i(s)}$$

"Ex 1" "Passive Feedback"

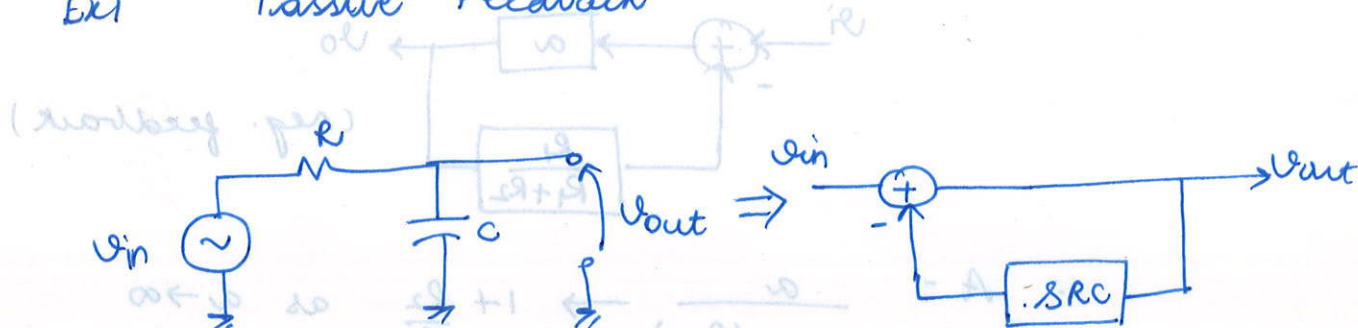

$$\therefore a(s) = 1, f(s) = SRC$$

(More generally, poles $\Rightarrow$ feedback)

(Dig world;
poles $\nRightarrow$ F.B.)

$\therefore$ poles & zeros cancel

(a(s) may have poles


$\therefore$ BD $\nRightarrow$ F.B.)

But F.B. loop in BD
 $\nRightarrow$ F.B.)

"Ex 2" "Parasitic Feedback"

C.G. Amp.

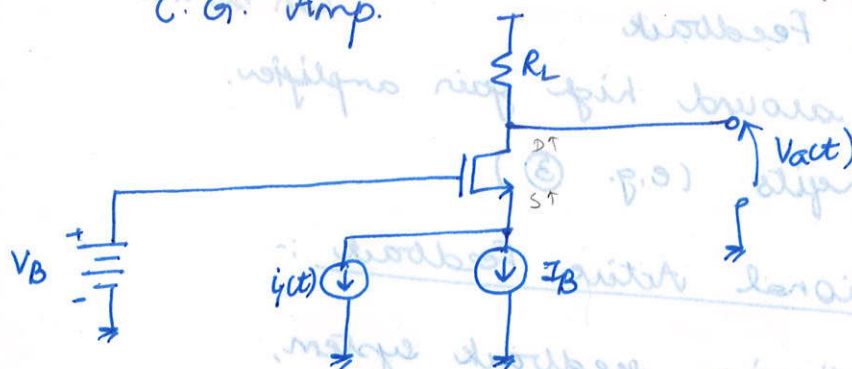
$\therefore r_{ds}$ is C.L.M. & undesired.



- pole-zero cancellation
in dig. blk.



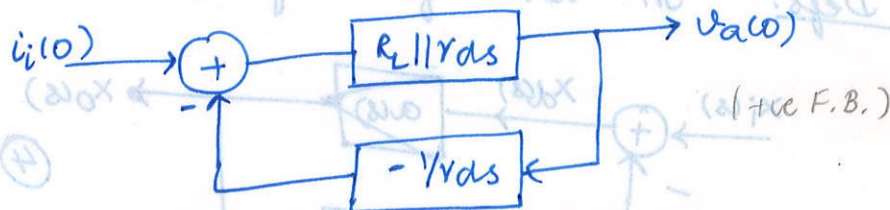$\Rightarrow$
(found previously)
(low freq. analysis)



Note: In Ex 1, feedback reduces the magnitude of


$x_0 \Rightarrow$ "negative feedback"

In Ex 2, feedback increases the magnitude of

$x_0 \Rightarrow$ "positive feedback".

"Ex 3" "Intentional Active Feedback"

(will focus mostly on
-ve F.B.)

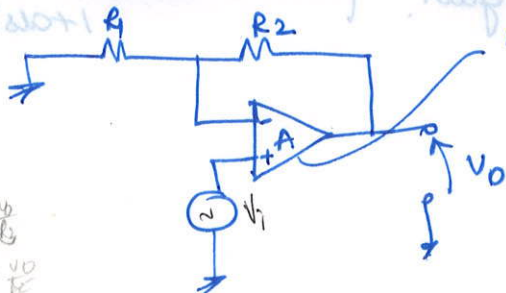


For now assume
 ∞ i/p imp.
& 0 o/p imp.

$$V_o = A V_i - \frac{R_1}{R_1 + R_2} V_o$$

$$V_o \frac{R_1 + R_2}{R_1} = \frac{V_i}{R_1}$$

$$V_o \frac{R_1 + R_2}{R_1} = \frac{V_i}{R_1}$$
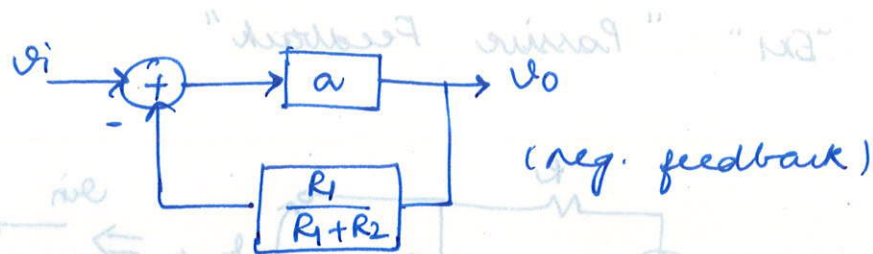
$$V_o \left[\frac{R_1 + R_2}{R_1} \right] = \frac{V_i}{R_1}$$



$$A = \frac{a}{1 + \frac{a/R_1}{R_1+R_2}} \rightarrow 1 + \frac{R_2}{R_1} \text{ as } a \rightarrow \infty$$

$\therefore$ large $a \Rightarrow A$ depends only on the 3

easy in IC's
 (all max @
 low freq.)

ratio of R 's.
 accurate in IC's

(abs R 's
 may have Temp.
 but relative R 's
 can be matched)

Benefits
 in today's IC's
 Can use
 DSP to
 correct
 non-linearity

Intentional Active Feedback

$\Rightarrow$ Feedback around high gain amplifier.

$\Rightarrow$ many benefits (e.g. 3)

Negative Intentional Active Feedback :-

Defn: In the following feedback system,



$a(s) \equiv$ "open loop gain"

$f(s) \equiv$ "feedback factor"

$T(s) \equiv a(s)f(s) \equiv$ "loop gain"

$A(s) \equiv$ "closed loop gain" (Recall $A(s) = \frac{a(s)}{1+a(s)f(s)}$)

Let $A_{ideal} = \lim_{a \rightarrow \infty} A = \frac{1}{f}$ (Dropping 'S' for now)

(eg. $A_{ideal} = 1 + \frac{R_2}{R_1}$ in Ex 3)

$$\therefore \textcircled{2} \Rightarrow A = A_{ideal} \left(1 - \frac{1}{1+T} \right)$$

Also, MGF & ④

$$\Rightarrow x_d = \frac{1}{1+T} x_i \rightarrow 0 \text{ as } T \rightarrow \infty$$

($a \rightarrow \infty$)

$\hookrightarrow$ Typically $a \rightarrow \infty$ & not $f \rightarrow \infty$

fractional deviation
of A from A_{ideal} .

$$x_f = \frac{1}{1+T_f} x_i \rightarrow x_i \text{ as } T \rightarrow \infty \text{ (} a \rightarrow \infty \text{)}$$

$\therefore x_f$ "tracks" x_i w/ "error signal" x_d

Benefits: (i) gain desensititivity

(basically $|a|$ must be high, need not be accurate)

(ii) non-linear distortion reduction.

(iii) in-loop noise suppression. (eg. VCO in PLL has too freq. noise performance)

(iv) broadbanding (high gain $\Rightarrow$ typ. low b/w)

(v) input/output impedance adjustment (big cap (high imp) to gnd)

Drawbacks: (i) $A < a$

(Potential)

(ii) excessive phase shift can cause instability.

(1) Gain Desensititivity:

$$\textcircled{2} \Rightarrow -\frac{dA}{da} = \pm \frac{1}{(1+aT)^2} \Rightarrow \frac{\Delta A}{A} \cong \frac{1}{(1+aT)^2} \text{ (small } \Delta a \text{)}$$

$$\therefore \frac{\Delta A}{A} \cong \left(\frac{1}{1+T} \right) \frac{\Delta a}{a} \text{ , large variation in 'a' } \Rightarrow \text{small " " " 'A'}$$

$\Rightarrow A$ is "stable" w.r.t. variations in a .

$\hookrightarrow$ w.r.t. same value Valter then w.r.t. BICO stability i.e. not variable

$$② \Rightarrow \frac{dA}{df} = -A^2$$

$$\therefore \frac{\Delta A}{\Delta f} \cong -A \cdot \frac{1}{f} \cdot \frac{T}{1+T}$$

$$\therefore \frac{\Delta A}{A} \cong -\left(\frac{T}{1+T}\right) \frac{\Delta f}{f}$$



$\cong 1$ for large T

$\Rightarrow A$ is not "stable" w.r.t. variations in f .
(variable)

$\Rightarrow$ Want high gain amp. (not necessarily well defined)
and precise feedback factor.

ii) Non-Linear Distortion Reduction: (Transfer fn. $\Rightarrow$ LTI system)

Ex4

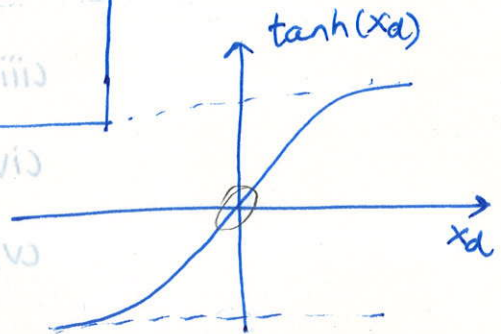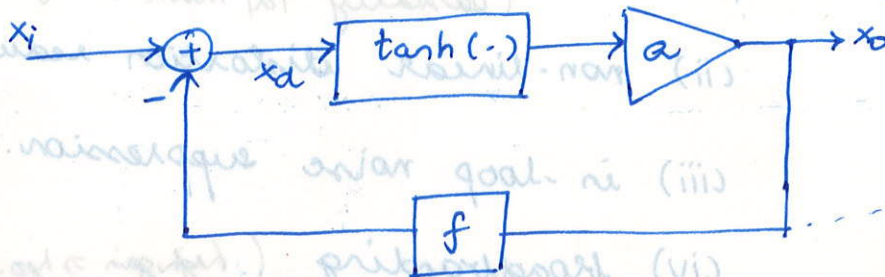

$$x_o = a \tanh(x_d)$$

$$= a \tanh(x_i - x_o f)$$

$$\therefore \tanh^{-1}\left(\frac{x_o}{a}\right) = x_i - f x_o$$

$$\frac{x_o}{a} + \frac{x_o^3}{3a^3} + \frac{x_o^5}{5a^5} + \dots = x_i - f x_o$$

$$\Rightarrow \frac{x_o}{a} + \frac{x_o^3}{3a^3} + \frac{x_o^5}{5a^5} + \dots = a(x_i - f x_o)$$

$\rightarrow 0$ as $a \rightarrow \infty$

$\therefore x_o \cong A x_i$ for large a & $x_o \rightarrow \frac{x_i}{f}$ as $a \rightarrow \infty$
no distortion.

Intuitively,
 $x_d \rightarrow 0$ if $a \rightarrow \infty$
where $\tanh(x_d) \dots$
is linear.

Heuristics:

1) Follows from gain sensitivity

(distortion prior to a


$\Rightarrow$ i/p dependent gain variation)

What's intuitive
is what I have seen
before; therefore
real iterations
are w/ Math

2) Large $a \Rightarrow$ small $x_d \Rightarrow$ small portion of
non linear curve is traversed $\Rightarrow \approx$ linear

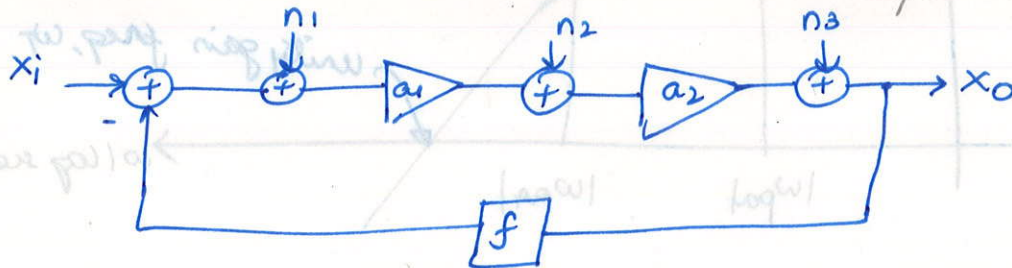(iii) In loop Noise suppression:

(Whether noise gets
suppressed depends
upon where it is
added)



Open loop gain: $a = a_1 a_2$

$$[(x_i + n_1) a_1 + n_2] a_2 + n_3 = x_o$$

$$\text{MAG} \Rightarrow x_o = \frac{a}{1 + a f} \left(x_i + n_1 + \frac{n_2}{a_1} + \frac{n_3}{a_1 a_2} \right)$$


not suppressed
somewhat suppressed
most suppressed
i.e. 0, 1/2, 1 to
have more
noise @ o/p.

(iv) Broadbanding:

Ex 5 Suppose $a \approx \frac{a_0}{1 - j\omega/\omega_{p0}}$ (dominant pole approx.)

$f \approx$ independent of ω .

eg:

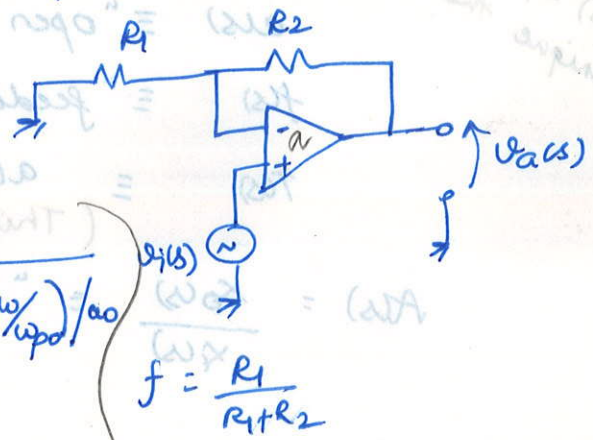

Then ②


$$\Rightarrow A(j\omega) = \underbrace{\left(1 + \frac{R_2}{R_1}\right)}_{1/f} \frac{1}{1 + (1 + R_2/R_1)(1 - j\omega/\omega_{p0})/a_0}$$

$$f = \frac{R_1}{R_1 + R_2}$$

algebra $\Rightarrow A(j\omega) = \frac{A_0}{1 - j\omega/\omega_{pA}}$

where $A_0 = \left(1 + \frac{R_2}{R_1}\right) \frac{1}{1 + (1 + R_2/R_1)/a_0}$ (5)

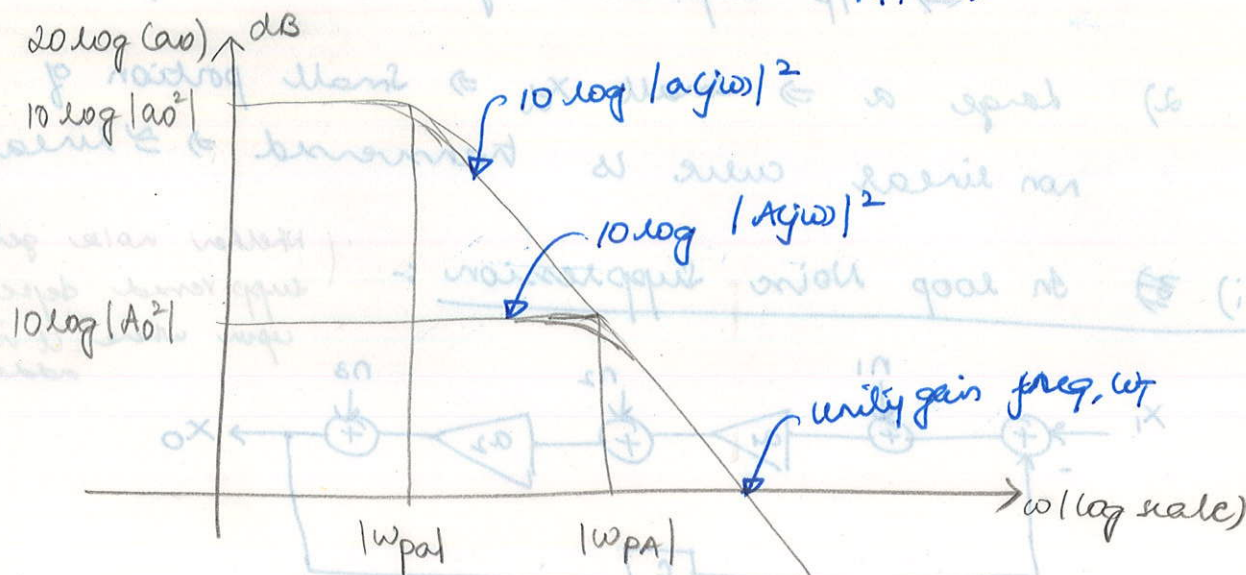
& $\omega_{PA} = \omega_{P0} \left(1 + a_0 \frac{R_1}{R_1 + R_2}\right)$ (6)



BEC #10 JAN FEB 14 '08

Negative intentional active feedback (contd.)

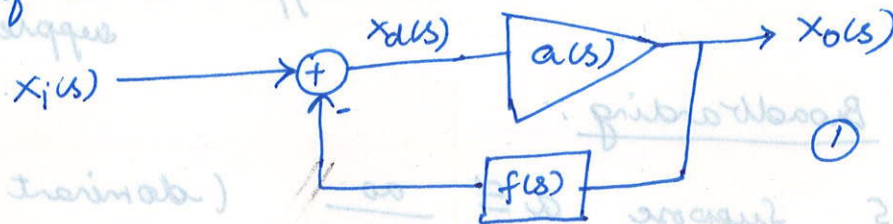Recall: Can always write the block diagram of a ckt. w/ feedback as:



$a(s) \equiv$ "open loop gain"

$f(s) \equiv$ "feedback factor"

$T(s) \equiv a(s)f(s) \equiv$ "loop gain"

(This is diff. from m.a.f. where $T(s) = -a(s)f(s)$)

$A(s) = \frac{X_o(s)}{X_i(s)} \equiv$ "closed loop gain" = $\frac{a(s)f(s)}{1 + a(s)f(s)}$ (defn. inconsistency)

Can model any system like this (1), but $a(s)$ & $f(s)$ are not unique then.

$$MGF \Rightarrow A(s) = \frac{a(s)}{1 + a(s)f(s)} \quad (2)$$

Broadbanding (contd.)

$$\text{Suppose : } a(j\omega) = \frac{a_0}{DC \text{ gain}} \frac{1}{1 - j\omega/\omega_{pa}} \quad (3)$$

dominant pole approximation.

What if we have ω_c ?

$$f(j\omega) = \text{const.}$$

$$(2), (3) \Rightarrow A(j\omega) = A_0 \frac{1}{1 - j\omega/\omega_{pa}} \quad \text{where}$$

$$A_0 = \frac{a_0}{1 + a_0 f}$$

(DC closed loop gain) (4)

$$\omega_{pa} = (1 + a_0 f) \omega_{pa}$$

$|A_0 \omega_{pa}| \equiv$ closed loop gain bandwidth product,

$GBW_{\text{closed loop}}$

$|a_0 \omega_{pa}| \equiv$ open loop gain bandwidth product,

$GBW_{\text{open loop}}$

$$(4) \Rightarrow A_0 \omega_{pa} = a_0 \omega_{pa}$$

$$\therefore GBW_{\text{open loop}} = GBW_{\text{closed loop}} \quad \text{in this case.}$$

Increasing f (between 0 & 1) decreases a_0 , but increases the 3dB B/W.

$f > 0$: we need -ve F.B.

Unity gain ($f=1$)

$f > 1 \Rightarrow$ Attenuator.

Using op-amps to build attenuators is not efficient.

$f > 1 \Rightarrow$ stability $\downarrow$
 $f=1$ spec opamp spec


But this is used in switched caps.

"Unity Gain Freq"

$$\equiv \omega_f \text{ such that } |a(j\omega_f)| = 1 \quad \omega_f \in \mathbb{R}$$

$$(3) \Rightarrow \left| a_0 \cdot \frac{1}{1 - j\omega_f/\omega_{pa}} \right| = 1$$
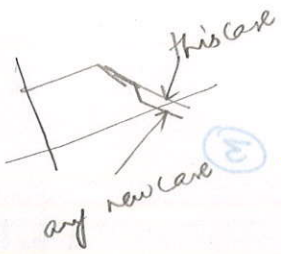
$$\Rightarrow (a_0^2 - 1) \omega_{pa}^2 = \omega_f^2$$




$$\Rightarrow \omega_f \approx a_0 / \omega_{pa} \quad (a_0 \gg 1)$$

↳ This is true for just this case

∴ $GBW = \omega_f$ in this case (not always in other cases)


dominant pole + indep. of freq. ✓
a dominant pole?

Ex1 (from last time)

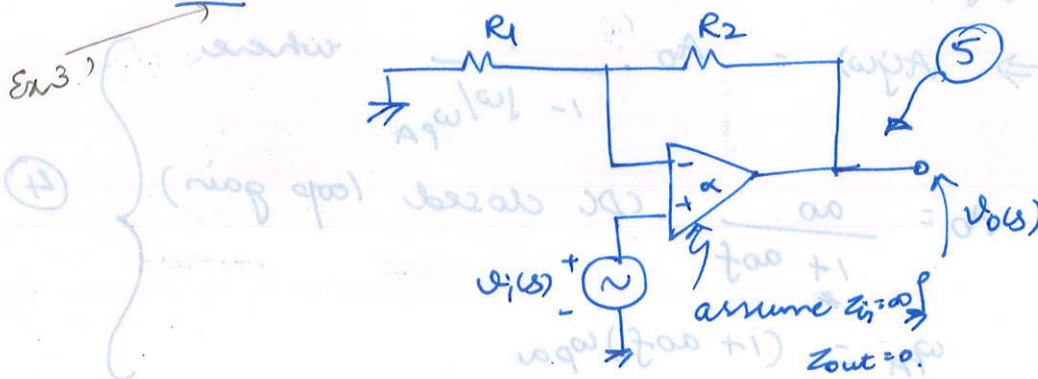

$$\Rightarrow \textcircled{1} \quad \omega_f \approx a_0 \quad ; \quad f = \frac{R_1}{R_1 + R_2}$$


Ex2 Same except different i/p location:-

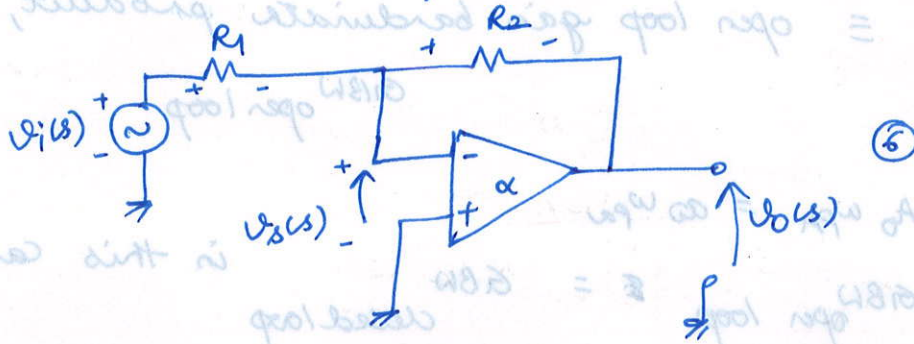

$$V_o(s) = A(s) [-V_s(s)]$$

$$V_s(s) = V_i(s) - \frac{R_1}{R_1 + R_2} V_o(s)$$
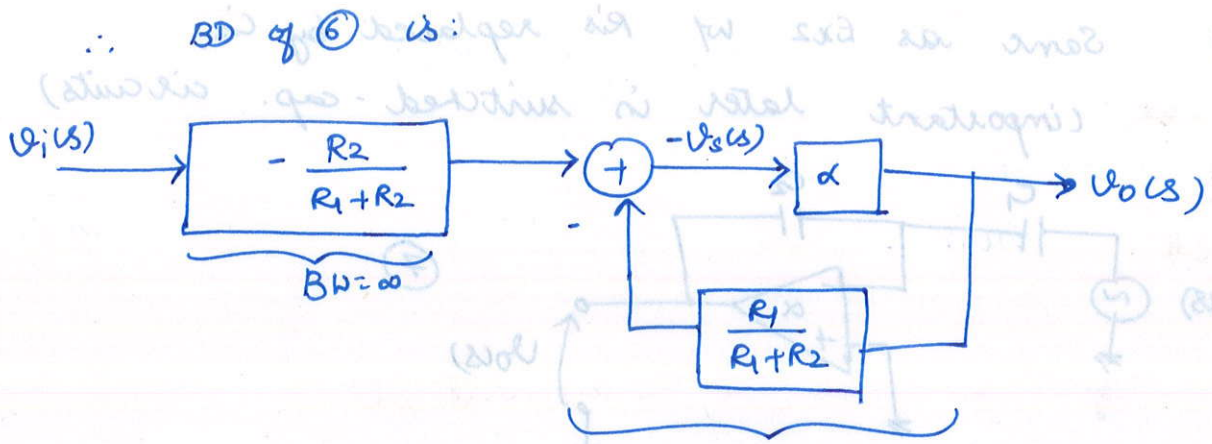
$$-V_s(s) = -V_i(s) \left[1 - \frac{R_1}{R_1 + R_2} \right] - V_o(s) \left[\frac{R_1}{R_1 + R_2} \right]$$




≡ ① w/ $a = \alpha$ & $f = \frac{R_1}{R_1 + R_2}$

(same as Ex 1)

⇒ BW = same as Ex 1 (∵ α is same as before
 $\frac{R_2}{R_1 + R_2}$ in forward path doesn't limit BW)

But GBW of ⑥ less than that of Ex 1 by $\frac{R_2}{R_1 + R_2}$

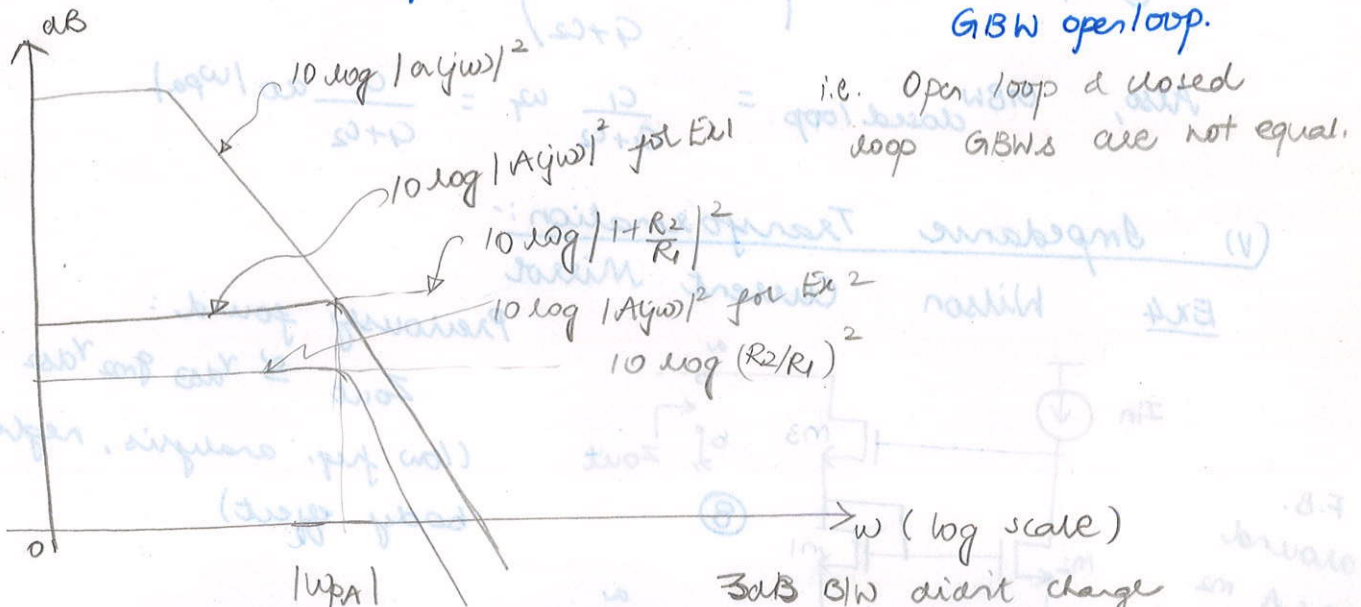Also, $GBW_{\text{closed-loop}} = \frac{R_2}{R_1 + R_2} \cdot \omega_t = \frac{R_2}{R_1 + R_2} \cdot \underbrace{a_o / \omega_{pa}}_{GBW \text{ open-loop}}$




i.e. Open loop & closed loop GBWs are not equal.

30dB BW didn't change but closed loop GBW diff from open loop GBW.


Ex 3

Same as Ex2 w/ R's replaced by C's.

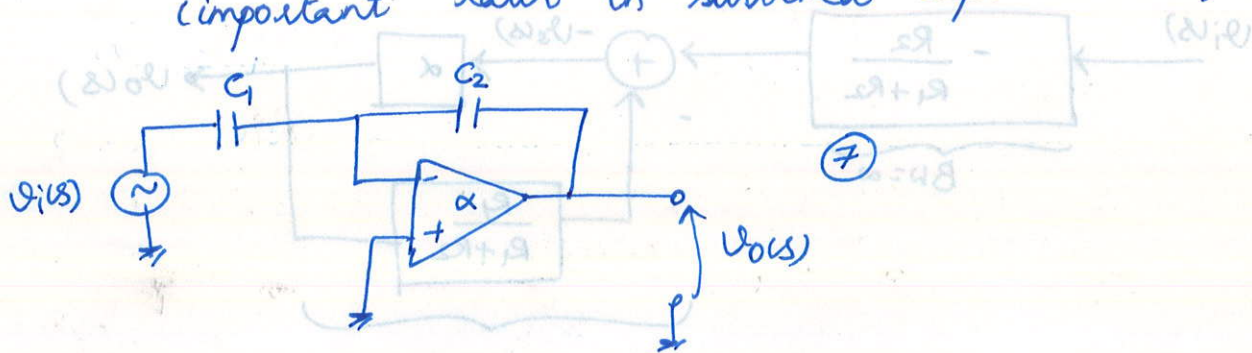(important later in switched-cap. circuits)



Exercise:- Show BD of ⑦ is:

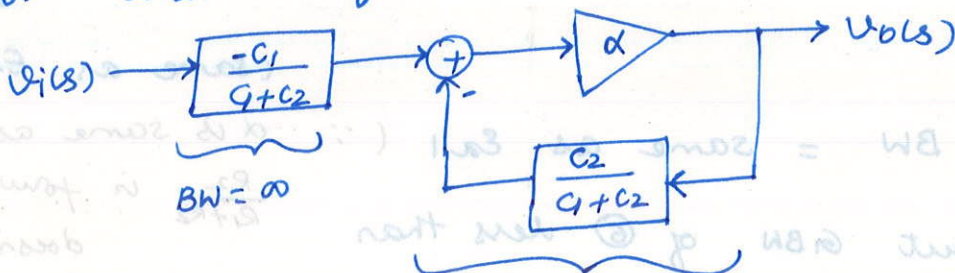


① w/ $\begin{cases} a = \alpha \\ f = \frac{C_2}{s+C_2} \Rightarrow f = \text{const. (EIR)} \end{cases}$

$\therefore ④ \Rightarrow BW = \left(1 + a_0 \frac{C_2}{s+C_2} \right) |w_{pa}|$

Also, $GBW_{\text{closed loop}} = \frac{C_1}{s+C_2} w_f = \frac{C_1}{s+C_2} a_0 |w_{pa}|$

(V) Impedance Transformation:-

Ex4 Wilson Current Mirror

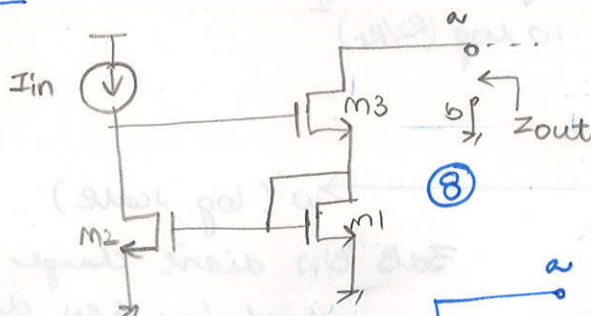


Previously found:

$Z_{out} \cong r_{ds3} \parallel g_{m2} r_{ds2}$

(low freq. analysis, neglecting body effect)

Now consider

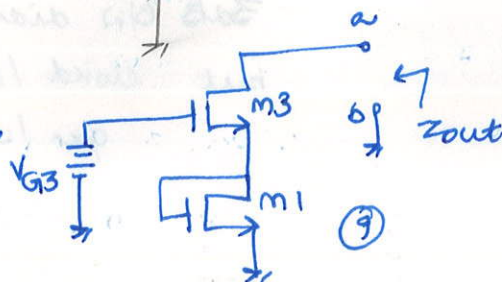

where


V_{GS} = DC component of V_{GS} in ⑧

Can show that: $Z_{out} \text{ of } \textcircled{9} \cong r_{ds3} (2 + \frac{1}{g_{m1} r_{ds3}})$

Note: $\textcircled{9}$ is equivalent to $\textcircled{8}$ with feedback disabled $\cong 2r_{ds3}$
 $\therefore$ Feedback increases Z_{out} by $\frac{1}{2} g_{m2} r_{ds2}$ factor
 (This circ. is typically used in high gain op amp loads; called as gain boosting)
 Why this factor intuitively?

Heuristics:

$\textcircled{8} \equiv$

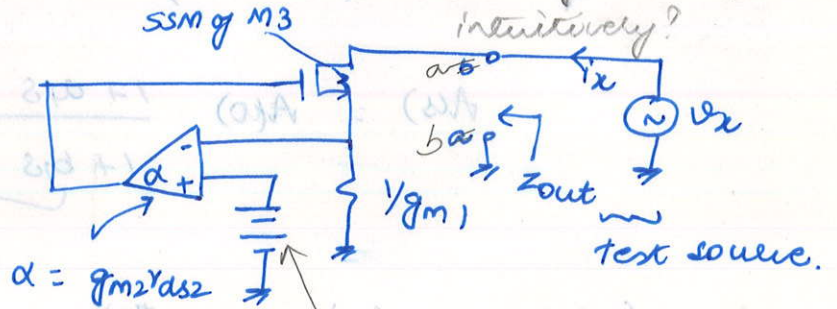


If V_x increases, i_x increases

$\Rightarrow V_{g2}$ increases

$\Rightarrow V_{g3}$ decreases


$\Rightarrow$ Feedback acts to reduce i_x ($\Rightarrow Z_{out} \uparrow$)

Ex 5 Voltage Source

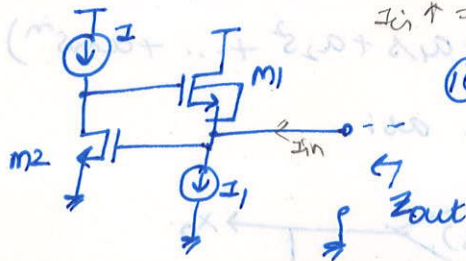

$I_{in} + I_{ds1} = 0$
 $I_{in} \uparrow \Rightarrow V_{gs1} \uparrow \Rightarrow V_{s1} \uparrow \Rightarrow V_{g2} \uparrow \Rightarrow V_{g1} \downarrow$
 $M1$: source follower, V_{s1} need not change a lot to accommodate current changes.

low freq. s.s.m:

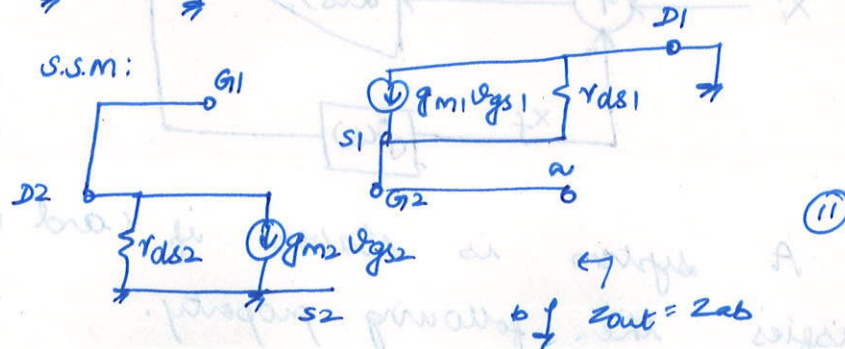

B.R.I: Let $g_{m1} V_{gs1} \equiv \text{ref source}$ $\therefore V_{gs1} = x_i, \alpha = g_{m1}$

$Z_{ab}^0 = r_{ds1}$, Exercise 1: $T_{sc} = 0; T_{oc} = +g_{m1} g_{m2} r_{ds1} r_{ds2}$

$\therefore Z_{ab} \cong \frac{1}{g_{m1} g_{m2} r_{ds2}} = \text{small!!} \sim \text{few ohms.}$

Feedback reduced o/p impedance by factor of $g_{m1} r_{ds2}$

Stability

Let $A(s) = \frac{a_0' + a_1's + a_2's^2 + \dots + a_m's^m}{b_0' + b_1's + b_2's^2 + \dots + b_n's^n}$; $m \leq n$. ①

If $A(0) \neq 0$ or ∞ , can write ① as,

$A(s) = A(0) \frac{1 + a_1s + a_2s^2 + \dots + a_ms^m}{1 + b_1s + b_2s^2 + \dots + b_ns^n}$ ②

$\equiv T(s)$


(Other choices of $T(s)$ are possible if we allow $a(s)$ to have poles).

$\therefore A(s) = \frac{a(s)}{1 + a(s)f(s)}$

where $a(s)f(s) = T(s)$

and $a(s) = A_0 (1 + a_1s + a_2s^2 + \dots + a_ms^m)$

$\therefore$ ② can be implemented as:

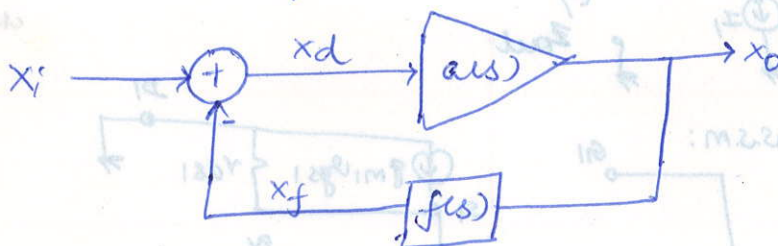

Def: A system is stable if (and only if) it satisfies the following property.

For each bounded I/P, $x_i(t)$, the output signal, $x_o(t)$ must also be bounded.

($x(t)$ is bounded means $\exists B \in \mathbb{R}$ such that $|x(t)| \leq B \forall t$)

∴ "Stability" $\equiv$ "bounded i/p, bounded o/p" stability
 (BIBO)

Claim 1: Let $h(t)$ be the impulse response of a linear time invariant system, and let $H(s)$ be its transfer function.
 (If not LTI, $H(s)$ is not defined).

Then the system is stable iff either of the following hold:

(i) All poles of $H(s)$ are in the L.H.P. (not including imaginary axis) (i.e. if s_0 is a pole, then $\text{Re}\{s_0\} < 0$)

(ii) $\int_{-\infty}^{\infty} |h(\tau)| d\tau < \infty$

Proof Exercise (Review Material) (Common Interview Q!!)

Claim 2: If an LTI has a transfer function given by ②, then it is stable iff

$$T(s_0) = -1 \Rightarrow \text{Re}\{s_0\} < 0$$

Proof: Exercise.

Def "Nyquist Plot" $\equiv$ plot of $\text{Im}\{T(j\omega)\}$ vs. $\text{Re}\{T(j\omega)\}$ as ω increases from $-\infty$ to ∞ .

Nyquist Criterion:

Provided there are no R.H.P. pole-zero cancellations in $T(s) = a(s)f(s)$, an LTI system is stable iff the net # of counter-clockwise encirclements of the point $(-1, 0)$ by the Nyquist plot equals the # of RHP poles in $T(s)$.
 (Does this mean that if O.L. is unstable, C.L. is unstable?)

∴ Nyquist criterion $\Rightarrow$ stability test. (not so useful these days 'coz of computers)

Will soon see: Nyquist criterion $\Rightarrow$ insight $\Rightarrow$ concepts of phase & gain margin.


Very useful.

Ex 1:


Suppose

$$T(s) = \frac{1}{(1+s)(1+s/2)}$$

poles: $-1, -2$

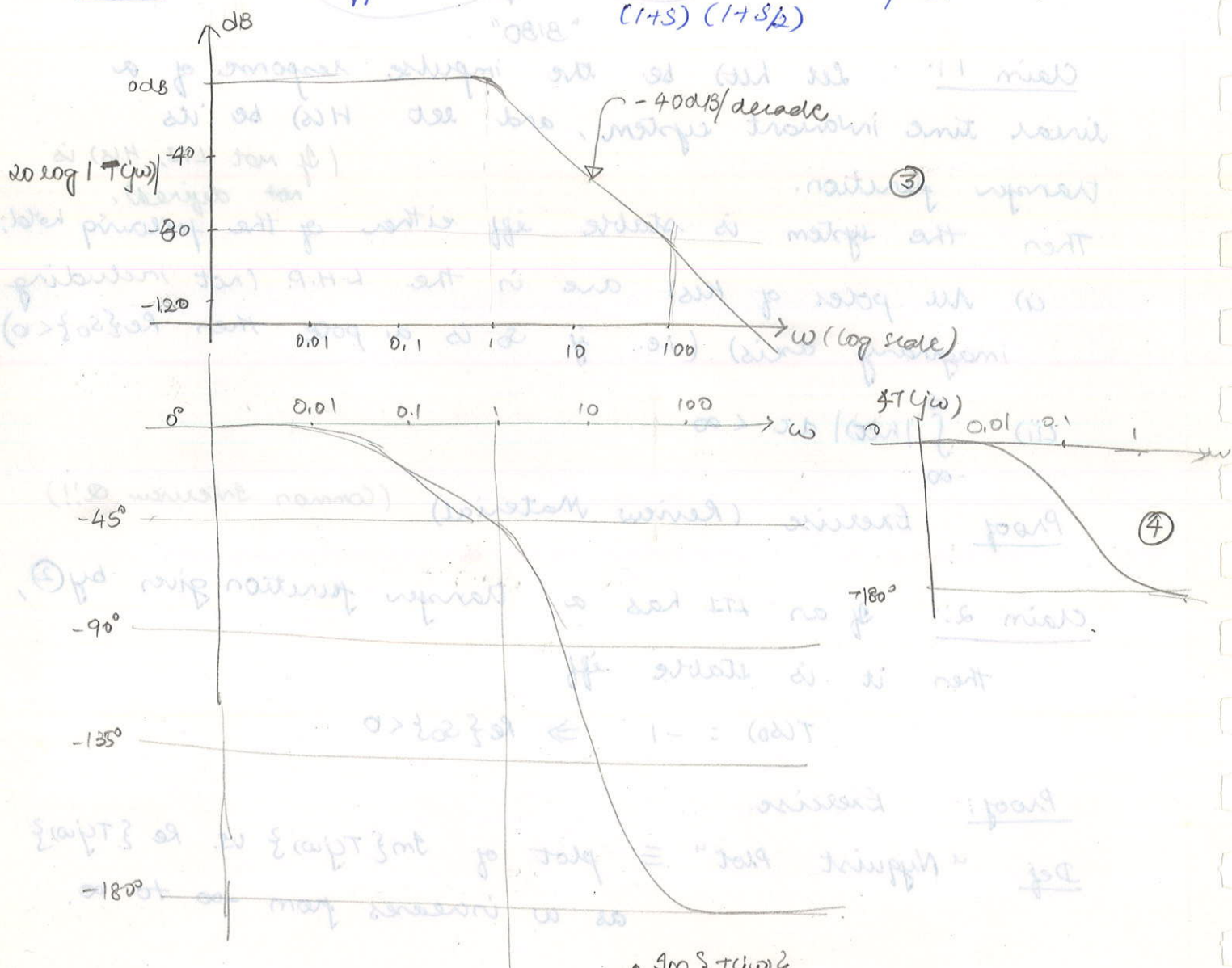

③, ④ $\Rightarrow$ Nyquist plot.

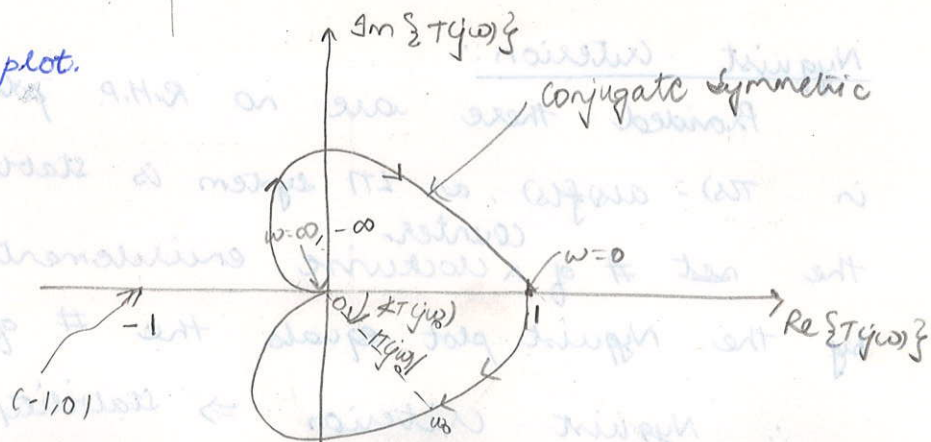

$\Rightarrow$ No encirclements of $(-1, 0)$ ($T(s)$ has no RHP poles by inspection)

Nyquist criterion $\Rightarrow$ System w/ transfer function $A(s) = \frac{a(s)}{1+T(s)}$ is stable (provided there are no pole-zero cancellations) in $a(s)f(s)$ way?

Ex 2:


Suppose

$$a(s) = \frac{a_0}{(1-s/p_1)(1-s/p_2)(1-s/p_3)} \quad \text{and}$$


$$f = \text{const.}$$

$$\therefore T(j\omega) = f \cdot q(j\omega)$$

For $|P_1| \cong \frac{1}{10}$ $|P_2| \cong \frac{1}{100}$ $|P_3|$ & $\text{Re } \{P_i\} < 0$ $i=1,2,3$
(i.e. all poles in L.H.P.)

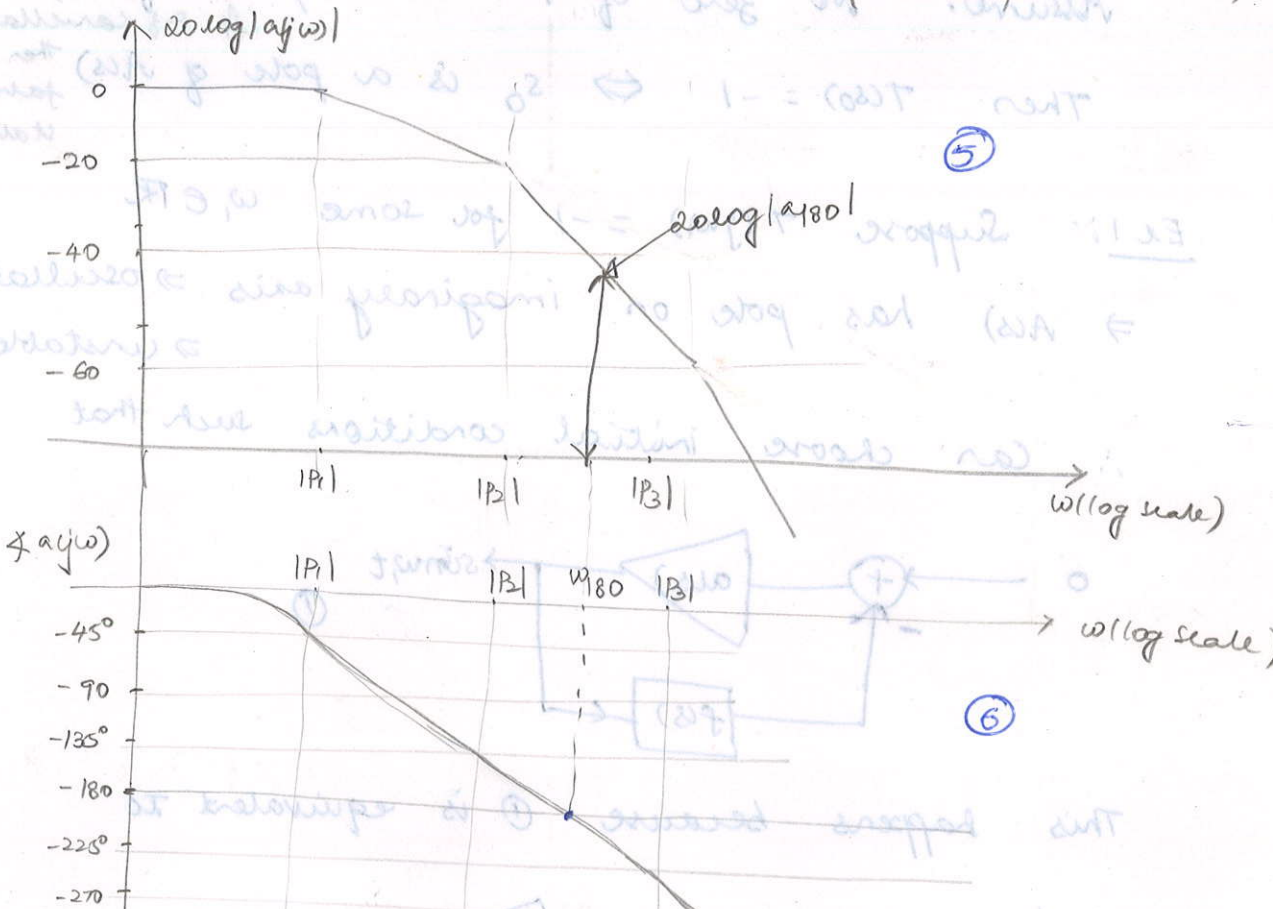

Nyquist plot (not to scale)

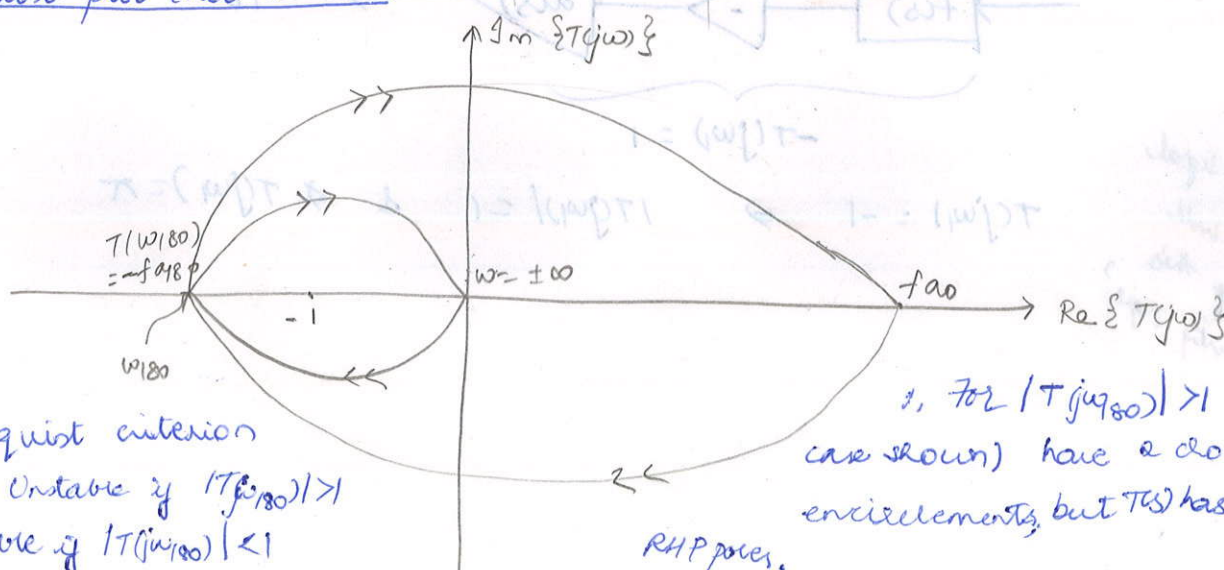

$\therefore$ Nyquist criterion

$\Rightarrow$ Unstable if $|T(j\omega_{180})| > 1$


$\Rightarrow$ stable if $|T(j\omega_{180})| < 1$

For $|T(j\omega_{180})| > 1$ (the case shown) have a clockwise encirclement, but $T(s)$ has no RHP poles.

Nyquist Criterion (contd.)

$$\text{Ret } A(s) = \frac{a(s)}{1+a(s)f(s)}$$

$\Leftrightarrow$

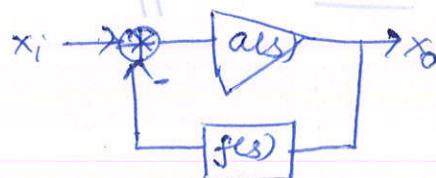

$$T(s) = a(s)f(s)$$


Assume: No zero of $f(s)$ is a pole of $a(s)$

Then $T(s_0) = -1 \Leftrightarrow s_0$ is a pole of $A(s)$ (if p-z cancellation, then can safely conclude stability)


Ex 1: Suppose $T(j\omega) = -1$ for some $\omega \in \mathbb{R}$

$\Rightarrow A(s)$ has pole on imaginary axis $\Rightarrow$ oscillation $\Rightarrow$ unstable.

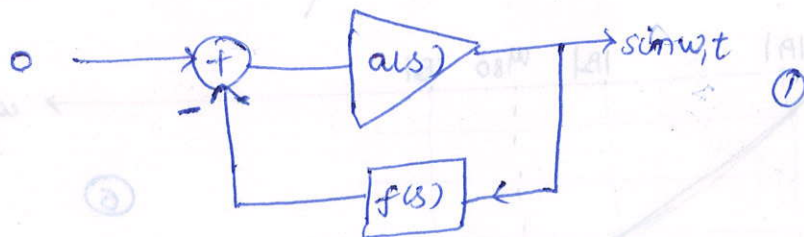$\therefore$ Can choose initial conditions such that



This happens because ① is equivalent to

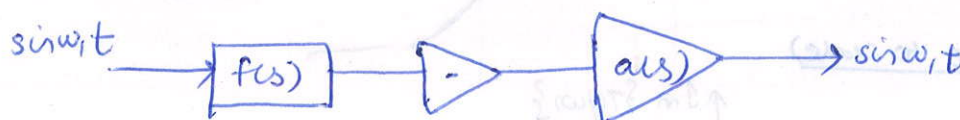

$$-T(j\omega) = 1$$

$$T(j\omega) = -1 \Rightarrow |T(j\omega)| = 1 \text{ \& } \angle T(j\omega) = \pi$$

Q: Any signal $x(t)$ will satisfy this property right?

Ex2 Suppose $T(s_0) = -1$ for $s_0 = \sigma_0 + j\omega_0$, $\sigma_0 \geq 0$

Complex roots must occur in pairs right?

$\Rightarrow$ have ① w/ $\sin \omega t$ replaced by $\underbrace{e^{\sigma_0 t}}_{\rightarrow \infty \text{ as } t \rightarrow \infty} e^{j\omega_0 t}$

$\Rightarrow$ 0 i/p $\Rightarrow$ Unbounded o/p. (Unstable)

Ex3 Suppose $A(s)$ is stable (i.e. the system whose T.F. / G.D. T.F. is $A(s)$ is stable) but for some $\omega_i \in \mathbb{R}$

$$|T(j\omega_i)| = 1 - \epsilon \text{ where } \epsilon = \text{small } \#$$

$$\angle T(j\omega_i) = \pi$$

Then have ringing for any input step

eg: $x_i = \text{step}$ $x_o = \text{ringing}$

(Basically underdamped system)

$\downarrow$
but need complex conjugate poles?

$\downarrow$
why is ringing good in regulators?

In many systems, ringing is undesirable because it slows settling time.

$\Rightarrow$ Need to design w/ "gain margin" s.t. $|T(j\omega)| \neq 1$ when $\angle T(j\omega) = \pi$ ~~not~~ sufficient "margin" to minimise ringing.

Nyquist criterion = method of evaluating "marginal stability" using simulated or calculated freq. response plots.

Recall: Nyquist plot $\equiv$ Plot of $\text{Im}\{T(j\omega)\}$ vs $\text{Re}\{T(j\omega)\}$ as ω increases from $-\infty$ to ∞ .

Nyquist criterion $\equiv$ An LTI system is stable iff the net # of counter clockwise encirclements of the point $(-1, 0)$ by the Nyquist plot equals the # of R.H.P. poles of $T(s)$.

i.e. No can have unstable o.l. systems which by f.b. become stable systems. (e.g. fighter planes)

The Nyquist criterion is based on "The Encirclement Property" (EP).

E.P.



Let $R(s)$ be any rational function. The plot of $R(s)$ along a closed, clockwise path, C , in the complex s -plane encircles the point $s=0$ in a clockwise direction in a net number of times equal to the net number of zeros minus the number of poles within contour.
(Free to choose contour)

Rational
 $\Rightarrow \# \text{ of } Z < \# \text{ of } P$
 $\Rightarrow \text{net } \# \text{ of } Z - \# \text{ of } P$
 $\Rightarrow \text{counter-clockwise} = +ve$
 $\Rightarrow \text{clockwise} = -ve$

Ex 4.1: $R(s) = \frac{s-1}{(s+1)(s^2+s+1)}$

poles: $-1, -\frac{1}{2} \pm \frac{\sqrt{3}}{2}j$

zero: 1

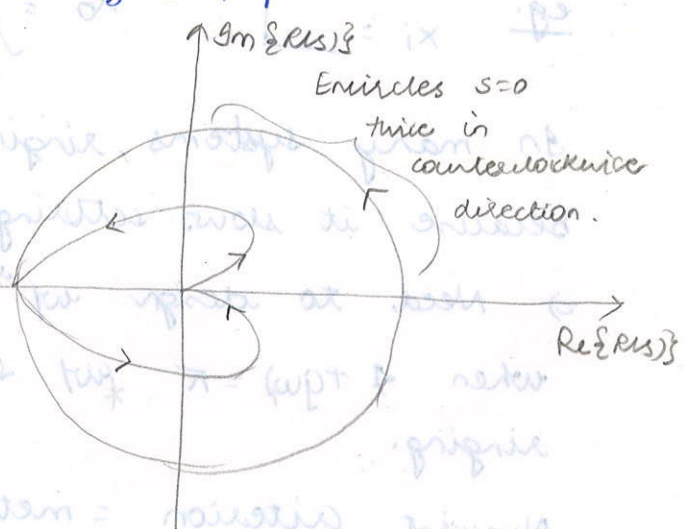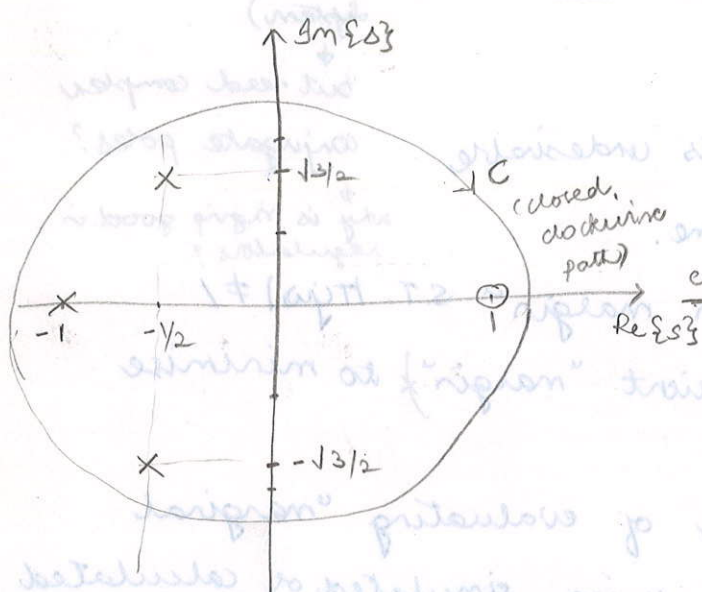


Why does this work?

Ex 5 Suppose $R(s)$ has only 2 (RHP) zeros and no poles.

$(v_1, v_2 \in \mathbb{R}, > 0)$

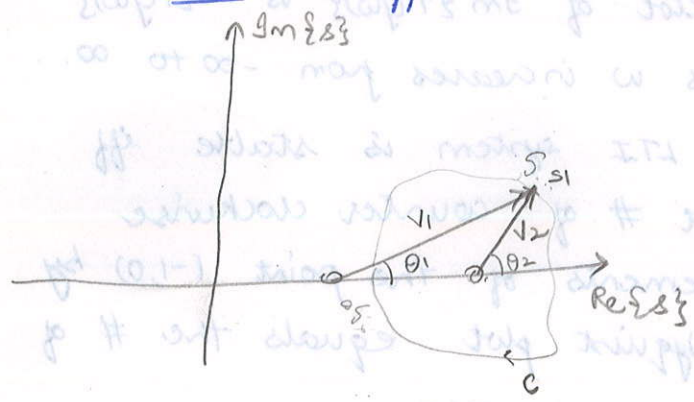$\therefore R(s) = v_1 v_2 e^{j(\theta_1 + \theta_2)}$



Verify

$$\frac{v_1 e^{j\theta_1} v_2 e^{j\theta_2}}{v_3 e^{j\theta_3}} = \frac{(s-z_1)(s-z_2)}{(s-z_3)}$$

$\left. \begin{array}{l} \text{net change in } \theta_1 \text{ is } 0 \\ \text{"net change in } \theta_2" \text{ is } -360^\circ (-2\pi) \end{array} \right\}$

② $\Rightarrow \angle R(s) = \theta_1 + \theta_2$

$\therefore$ As C is traversed, the net change in phase of $R(s)$ is $-2\pi \Rightarrow R(s)$ evaluated

$\Rightarrow R(s)$ circles origin once in clockwise direction
 $cs=0$
 $se\zeta$ contour

Proof of Nyquist Criterion:

Restrictions of proof: 1) Rational $T(s)$


2) $|T(j\omega)| < \infty \quad \forall \omega \in \mathbb{R}$
 (i.e. no poles on imaginary axis)

1) $\Rightarrow$ 3)

3) $T(s)$ has # of poles $\geq$ # of zeros.

(But Nyquist criterion also applies w/o restrictions 1) & 3) and can be modified to handle poles on imaginary axis)

Consider contour C as

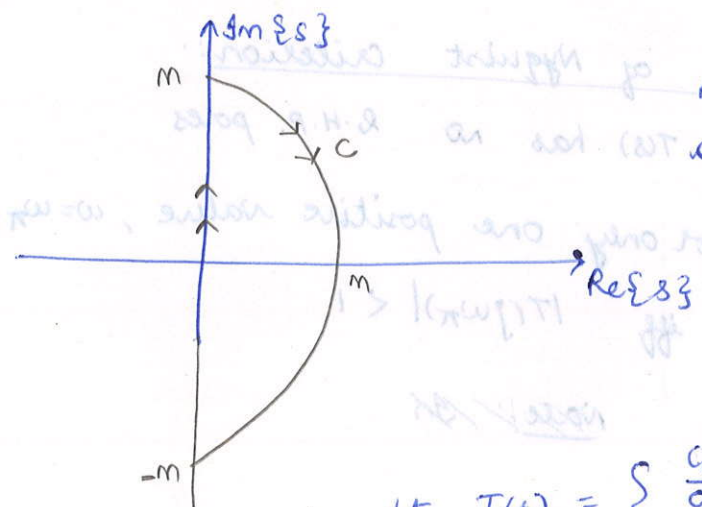

As $m \rightarrow \infty$, C contains all R.H.P. poles of $A(s)$

1), 3) $\Rightarrow$

$$T(s) = \frac{c_0 + c_1 s + \dots + c_{N_1} s^{N_1}}{d_0 + d_1 s + \dots + d_{N_2} s^{N_2}}$$

$\therefore \lim_{|s| \rightarrow \infty} T(s) = \begin{cases} \frac{c_{N_1}}{d_{N_2}} & \text{if } N_1 = N_2 \\ 0 & \text{if } N_1 < N_2 \end{cases} = \text{const.}$

where $N_1 \leq N_2$.

- $\Rightarrow$ The plot of $T(s)$ along the semi-circular part of C approaches a single point on real axis as $m \rightarrow \infty$.
- $\Rightarrow$ The Nyquist plot is equivalent to the plot of $T(s)$ along C as $m \rightarrow \infty$.

e.g., recall: Nyquist plot of $T(s) = \frac{1}{(1+s)(1+s/2)}$ is

⇒ Can apply encirclement property to Nyquist plot.



Let $R(s) = 1+T(s)$. Then plot of $R(s)$ along C encircles origin exactly as many times as that of $T(s)$ encircles $(-1,0)$.

∴ Encirclement property ⇒ Net # of clockwise encirclements of $(-1,0) = \# \text{ of zeros of } 1+T(s) - \# \text{ of poles of } 1+T(s) \text{ inside } C.$

But • zeros of $1+T(s) \equiv$ poles of $A(s)$

• poles of $1+T(s) \equiv$ poles of $T(s)$ (zeros of $A(s)$)

• inside $C =$ all RHP as $M \rightarrow \infty$

⇒ Nyquist criterion.


Important Special Case of Nyquist Criterion:

Suppose $T(0) \neq 0$ and $T(s)$ has no R.H.P. poles

if $|XT(j\omega)| \leq \pi$ for only one positive value, $\omega = \omega_\pi$,

then $A(s)$ is stable iff $|T(j\omega_\pi)| < 1$

e.g. picture:-

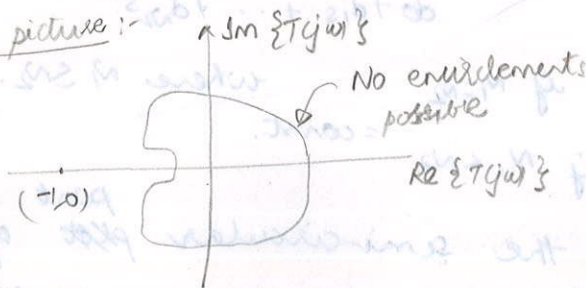

Note! ~~AK~~

Note! In general, $|T(j\omega_\pi)| > 1 \Rightarrow$ instability (!)