


website: ece264.ucsd.edu

Username: ece264

pwd: 74lopamp

Poles Zeros & Freq. Response

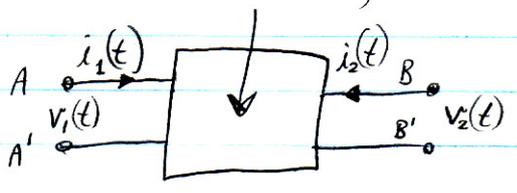SSM (small signal model) of circ. containing trans. and RLC networks



①

A, A' ≡ any two nodes of the circuit  
B, B' ≡ " " " "

Def. Let  $x(t)$  be any real signal  
then  $\mathcal{L}\{x(t)\} = \int_{-\infty}^{\infty} x(t)e^{-st} dt \equiv$  Bilateral Laplace transform  
lowercase  $\rightarrow x(s)$

Let  $G(s) = \frac{x(s)}{y(s)}$  where  $x(t) = v_1(t), i_1(t), v_2(t), i_2(t)$   
 $y(t) =$  " " " "

eg.  $G(s) = \frac{v_2(s)}{v_1(s)} =$  Laplace trans. of gain from A, A' to B, B'

or  $G(s) = \frac{v_1(s)}{i_1(s)} =$  " " " impedance at A, A' terminals.

Fact  $G(s)$  is always rational with real coefficients.

ie.  $G(s) = \frac{a_n s^n + a_{n-1} s^{n-1} + \dots + a_1 s + a_0}{b_n s^n + b_{n-1} s^{n-1} + \dots + b_1 s + b_0}$

where  $a_k, b_k \in \mathbb{R}$

②

rational  
ratio of two  
polynomial functions


Q Do  $\exists$  practical circ. for which  $G(s) \neq$  rational

A Yes! Ex: Delay element:  $G(s) = e^{-sT} \equiv T$  second delay

Can write (2) as

$$G(s) = G' \frac{(s-z_1)(s-z_2)\dots(s-z_n)}{(s-p_1)(s-p_2)\dots(s-p_m)} \quad (3) \quad \text{where } G', z_k, p_k \in \mathbb{C}$$

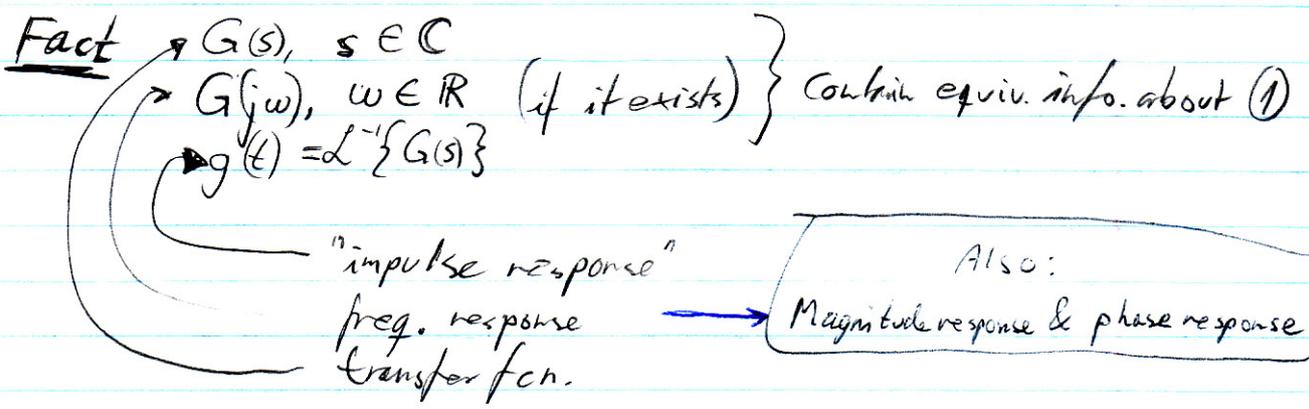$z_k =$  zeros of  $G(s)$   
 $p_k =$  poles of  $G(s)$



Goal: Find simple way to deduce "shape" of  $G(j\omega)$  from poles & zeros of  $G(s)$

Claim 1 real coeff  $\iff$  If  $s_0 = \alpha + j\beta$  ( $\alpha, \beta \in \mathbb{R}$ ) is a pole (or zero) of  $G(s)$  Then  $s_0^* = \alpha - j\beta$  is also a pole (or zero) of  $G(s)$

Proof: exercise

Ex  $(s-s_0)(s-s_0^*) = s^2 - s(\overbrace{s_0+s_0^*}^{2 \cdot \text{Re}\{s_0\}}) + \overbrace{s_0 s_0^*}^{|s_0|^2} = s^2 + s(2\zeta \cdot \omega_0) + \omega_0^2$

where  $\omega_0 \equiv |s_0| \equiv$  resonant frequency  
 $\zeta \equiv -\text{Re}\{s_0\}/\omega_0 \equiv$  damping ratio (Claim 1  $\implies \zeta, \omega_0 \in \mathbb{R}$ )

$\therefore$  Can group conjugate poles & zeros together

$$G(s) = G' \left[ \prod_{\text{real zeros}} (s-z_k) \cdot \prod_{\text{complex zero pairs}} (s^2 + s(2\zeta_i \omega_{0i}) + \omega_{0i}^2) \right] \quad (4)$$

$$\cdot \left[ \prod_{\text{real poles}} \left( \frac{1}{s-p_k} \right) \cdot \prod_{\text{complex pole pairs}} \left( \frac{1}{s^2 + s(2\zeta_i \omega_{0i}) + \omega_{0i}^2} \right) \right]$$



①

New room: Tuesday '15 (website)  
Homework on Tuesday. Gjør tutorial for Cadence

cont.:

recall ⑩ ...  $-\sum_{\text{complex pole pairs}} 10 \cdot \lg \left[ \left(1 - \frac{\omega^2}{\omega_{op_i}^2}\right)^2 + 4 \frac{\zeta_{pi}^2}{\omega_{op_i}^2} \omega^2 \right]$

Claim 2 The max departure of the exact curve for real pole and zero factors from the asymptotic approx is a factor of 0.707 in both ⑦ and ⑧.

Proof exercise

⑨, ⑩  $\rightarrow 0 \text{ dB}$  as  $\omega \rightarrow 0$

$Q = \frac{1}{2\zeta}$

⑨  $\rightarrow 40 \cdot \lg \omega - \text{const}$  as  $\omega \rightarrow \infty$


⑩  $\rightarrow -40 \cdot \lg \omega - \text{const}$  as  $\omega \rightarrow \infty$

Peaking for  $0 \leq \zeta < \frac{1}{\sqrt{2}}$   $Q > \frac{1}{\sqrt{2}}$

Peak @ DC for  $\zeta \geq \frac{1}{\sqrt{2}}$

$\zeta$	Mag. at $\omega = \omega_{op_i}$	$Q$
0	$\infty$	$\infty$
1/4	+6 dB	2
1/2	0 dB	1
1/√2	-3 dB	1/√2
1	-6 dB	1/2

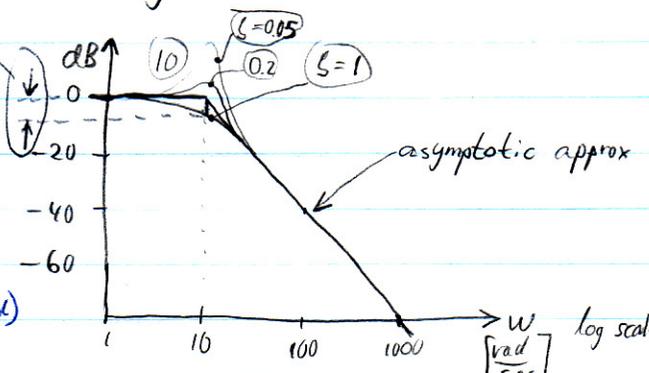
e.g. picture for  $\omega_{op_i} = 10 \frac{\text{rad}}{\text{sec}}$  (Butterworth) (critically damped)



Voltage amplitude at  $\omega = \omega_{op_i}$

$\therefore$  asymptotic approx  $\neq$  good approx near  $\omega = \omega_{op_i}$  / or  $\zeta \approx 0.2$

poles associated with ⑩ (verify)

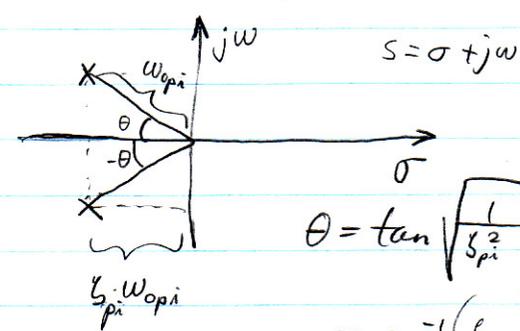

Voltage amplitude at the peak freq.:

$$\frac{1}{2\zeta \cdot \sqrt{1-\zeta^2}}$$

or  $\frac{Q^2}{\sqrt{Q^2-1/4}}$  or  $\frac{1}{\sin(2\theta)}$

$$\theta = \tan^{-1} \sqrt{\frac{1}{\zeta_{pi}^2} - 1}$$

$$= \cos^{-1}(\zeta_{pi}) \quad (\zeta_{pi} < 1)$$

RLC:	Parallel	Series	} $\Omega$
damping:	$\frac{L}{4RC}$	R	
critical damping:	$\frac{1}{2} \sqrt{\frac{L}{C}}$	$2 \cdot \sqrt{\frac{L}{C}}$	
damping ratio $\zeta$ :	$\frac{1}{2R} \cdot \sqrt{\frac{L}{C}}$	$\frac{R}{2} \cdot \sqrt{\frac{C}{L}}$	
Q-factor	$R \sqrt{\frac{C}{L}}$	$\frac{1}{R} \sqrt{\frac{L}{C}}$	

$\omega_r = \omega_0 \cdot \sqrt{1 - 2\zeta^2}$

$\omega_d = \omega_0 \cdot \sqrt{1 - \zeta^2}$

2

(start of "New" lecture)

$$G(s) = \frac{a_m s^m + a_{m-1} s^{m-1} + \dots + a_1 s + a_0}{b_n s^n + \dots + b_1 s + b_0} \quad (1)$$

where  $a_k, b_k \in \mathbb{R}$  and  $s \in \mathbb{C}$

Let  $\{\omega_{zk} : k=1, 2, \dots, N\} =$  non-zero real zeros of (1) (if any)

$\{\omega_{pk} : k=1, 2, \dots, N'\} =$  poles

$\{s_{zk}, s_{zk}^* : k=1, \dots, N''\} =$  non-real conj. zeros of (1)

$\{s_{pk}, s_{pk}^* : k=1, \dots, N'''\} =$  poles

$$\omega_{0xk} = |s_{xk}| \quad (x=z \text{ or } p) \quad (\equiv \text{natural freq. when } x=p)$$

$$\zeta_{xk} = -\frac{\text{Re}\{s_{xk}\}}{\omega_{0xk}} \quad (\equiv \text{damping ratio when } x=p)$$

2

Using (2), (1) becomes

$$G(s) = G(0) \cdot s^{n_0} \left[ \prod_{k=1}^N (1 - s/\omega_{zk}) \right] \left[ \prod_{k=1}^{N''} \frac{1}{\omega_{0zk}^2 (s^2 + 2\zeta_{zk}\omega_{0zk}s + \omega_{0zk}^2)} \right] \cdot \left[ \prod_{k=1}^{N'} (1 - s/\omega_{pk}) \right]^{-1} \left[ \prod_{k=1}^{N'''} \frac{1}{\omega_{0pk}^2 (s^2 + 2\zeta_{pk}\omega_{0pk}s + \omega_{0pk}^2)} \right]^{-1} \quad (3)$$

where  $G(0) = \frac{a_0}{b_0}$ ,  $n_0 = \begin{pmatrix} \# \text{ zero-freq zeros} \\ -\# \text{ poles} \end{pmatrix}$

$$G(j\omega) = \underbrace{|G(j\omega)|}_{\text{magnitude}} e^{j \underbrace{\angle G(j\omega)}_{\text{phase}}}$$

3

Phase response

Exercise: verify  $\angle G(j\omega) = \sum \angle (\text{each factor in } \textcircled{3})|_{s=j\omega}$

where  
(factor in  $\textcircled{3}$ )  $\rightarrow \angle (\text{factor in } \textcircled{3})|_{s=j\omega}$


$$G(0) = \frac{a_0}{b_0} \rightarrow \begin{cases} 0 & \text{if } G(0) > 0 \\ \pi & \text{if } G(0) < 0 \end{cases}$$

$$s^{n_0} \rightarrow \frac{\pi}{2} \cdot n_0$$

$$\left(1 - \frac{s}{\omega_{xk}}\right)^{\pm 1} \rightarrow \mp \tan^{-1}\left(\frac{\omega}{\omega_{xk}}\right) \quad (x=p \text{ or } z)$$

$$\left[\frac{1}{\omega_{oxk}^2} (s^2 + 2\zeta_{xk}\omega_{oxk}s + \omega_{oxk}^2)\right]^{\pm 1} \rightarrow \mp \tan^{-1}\left(\frac{2\zeta_{xk}\omega_{oxk}\omega}{\omega_{oxk}^2 - \omega^2}\right) \quad x=p \text{ or } z$$

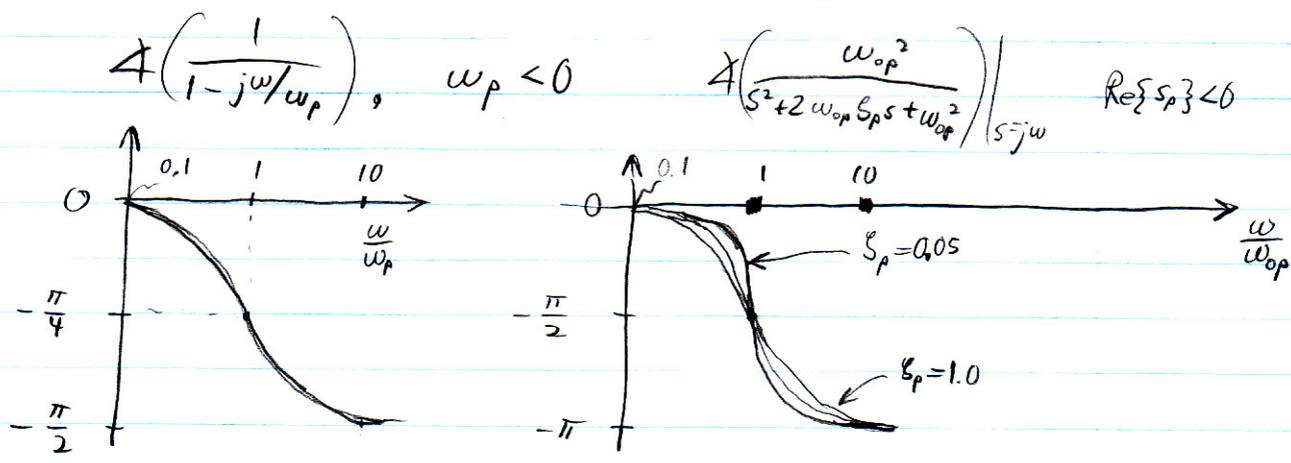Picture (for LHP poles; only the sign changes for LHP zeros, same for RHP zeros)



4

# Poles & Zeros - time response

$$\left. \begin{aligned} \text{Let } p(s) &= a_m s^m + a_{m-1} s^{m-1} + \dots + a_0 \\ q(s) &= b_n s^n + b_{n-1} s^{n-1} + \dots + b_0 \end{aligned} \right\} \Rightarrow G(s) = \frac{p(s)}{q(s)}$$

Recall "Partial Fraction Expansion" (PFE)

Ex 1  $m < n$   $p_i \neq p_j$  for  $i \neq j$

$\Leftrightarrow$  roots of  $q(s)$  are all "first order"

$$= \frac{p(s)}{b_1 (s-p_1) (s-p_2) \dots (s-p_n)}$$

Then  $G(s) = \sum_{k=1}^n \frac{A_k}{s-p_k}$ ,  $A_k \in \mathbb{R}$  where  $A_k = \lim_{s \rightarrow p_k} [(s-p_k) G(s)]$

Ex 2  $m < n$   $p_1, p_2, p_3, \dots, p_n = 1^{st}$  order roots of  $q(s)$

where  $n' \leq n-2$   
 $4 \leq 7-2$

and  $p_{n'+1} = p_{n'+2} = \dots = p_n$

"multiple roots" of  $q(s)$  where  $r = n - n'$   
 $3 = 7 - 4$

minst 2 like rotter  
(example no.s)

$$\text{Then } G(s) = \sum_{k=1}^{n'} \left( \frac{A_k}{s-p_k} \right) + \sum_{k=1}^r \frac{B_k}{(s-p_n)^k}$$

where  $A_k \equiv$  4

$$B_k = \lim_{s \rightarrow p_n} \frac{1}{(r-k)!} \frac{d^{r-k}}{ds^{r-k}} \left[ (s-p_n)^r G(s) \right] \quad \text{5}$$

Similar results hold for any comb. of 1<sup>st</sup> order and multiple roots of  $q(s)$ .

Can extend for  $m \geq n$

1/5

ECE 264A

Jan 15, 2008

E.G.

Cont. from last time

(Mid-term calc.: maybe)

$$\text{let } g(t) = \mathcal{L}^{-1}\{G(s)\}$$

PFE  $\Rightarrow g(t) =$  weighted sum of terms of types

$$\left\{ \begin{array}{l} \mathcal{L}^{-1}\left\{\frac{1}{s-p_k}\right\} = e^{p_k t} \cdot u(t) \quad (6) \\ \mathcal{L}^{-1}\left\{\frac{1}{(s-p_k)^r}\right\} = \frac{t^{r-1}}{(r-1)!} \cdot e^{p_k t} \cdot u(t) \quad (7) \end{array} \right.$$

(Note: (7) = (6) \* (6) \* (6) \* ... \* (6)  
r times

In circuits, rarely have multiple roots of  $g(s)$   
(i.e., rarely have multiple equal poles)  
 $\Rightarrow$  only concerned with (6) usually

For real non-zero poles, (6)  $\propto \mathcal{L}^{-1}\left\{\frac{1}{1-s/\omega_{pk}}\right\}$

For non-real poles, we can group conj. pairs for which (6) results in terms of form

$$\mathcal{L}^{-1}\left\{\frac{\omega_{pk}^2}{s^2 + s(2\zeta_{pk}\omega_{pk}) + \omega_{pk}^2}\right\}$$

$\omega_{pk}$  is an absolute value  
(Jan 10, pg. 2)

Jan 15, 2008

2/5


Step Response

$$\mathcal{L}\{u(t)\} = \frac{1}{s}$$

Response of "output" with the input =  $u(t)$  = "step response"

$$\therefore g_{\text{step}} = \mathcal{L}^{-1}\left\{\frac{1}{s} \cdot G(s)\right\}$$

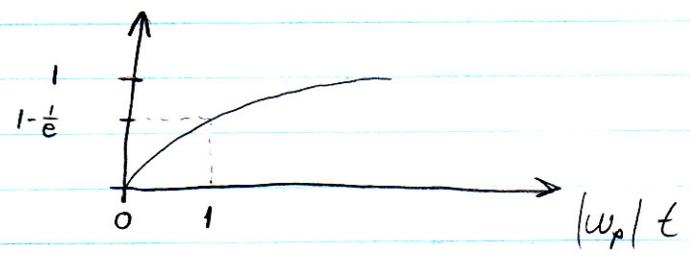
$$\mathcal{L}^{-1}\left\{\frac{1}{s} \cdot \frac{1}{1-s/\omega_p}\right\} = u(t) \cdot (1 - e^{-\omega_p t})$$



$$\mathcal{L}^{-1}\left\{\frac{1}{s} \cdot \frac{\omega_{op}^2}{s^2 + s(2\zeta_s \omega_{op}) + \omega_{op}^2}\right\} = u(t) \cdot \left[1 - \frac{1}{\sqrt{1-\zeta_s^2}} e^{-\zeta_s \omega_{op} t} \cdot \sin(\omega_{op} \sqrt{1-\zeta_s^2} \cdot t + \theta)\right]$$

where  $\theta = \tan^{-1}\left(\frac{\sqrt{1-\zeta_s^2}}{\zeta_s}\right)$

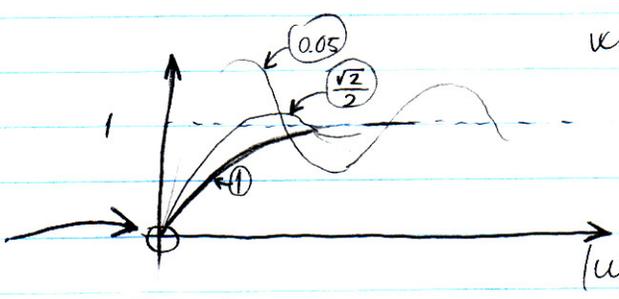Den deriverte i starten av step-responser er 0 dersom vi ikke har zeros i t.f.



- For  $\zeta_s = 0$ , poles on imag. axis  $\Rightarrow$  oscillation.
- For  $\zeta_s < 0$  poles in RHP  $\Rightarrow$  oscillation with exp. increasing amplitude
- For  $0 < \zeta_s < 1$  "overshoots" but settles to 1.

$$\rightarrow = u(t) \cdot \left[1 - \frac{1}{\sqrt{1-\zeta_s^2}} \cdot e^{-\zeta_s \omega_{op} t} \cdot \cos\left[\omega_{op} \sqrt{1-\zeta_s^2} \cdot t - \tan^{-1}\left(\frac{\zeta_s}{\sqrt{1-\zeta_s^2}}\right)\right]\right]$$

3/5

Dominant pole approx.

Provided have no DC poles or zeros

$$G(s) = G(0) \cdot \frac{(1 - s/z_1)(1 - s/z_2) \dots (1 - s/z_m)}{(1 - s/p_1)(1 - s/p_2) \dots (1 - s/p_n)}$$

Suppose  $|p_1| \ll |p_k|, 2 \leq k \leq n$

$|p_1| \ll |z_k|, 1 \leq k \leq m \quad (\Rightarrow p_1 \in \mathbb{R} \text{ why?})$

Then  $|G(j\omega)| \cong \frac{G(0)}{\sqrt{1 + \frac{\omega^2}{|p_1|^2}}} \quad \therefore |G(j\omega_{-3dB})| = \frac{G(0)}{\sqrt{2}}$

$\Rightarrow \omega_{-3dB} = |p_1| \quad (\text{3dB Bandwidth})$

(New numbering)

Common source amplifiers / freq. response

Aside Course convention


$$I_d = I_D + i_d$$

$$V_{gs} = V_{GS} + v_{gs}, \text{ etc...}$$

Variations about a constant "bias" value  
 a constant "bias" level  
 "total" or "absolute" value


Løse boken bruker  $i_d$  og  $v_{gs}$  for dette.  $\leftrightarrow$  page 7

4/5

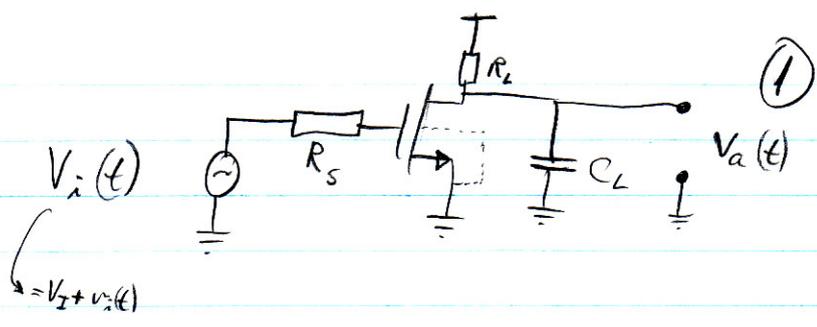

( $R_L$  &  $R_s$  often from active circuits, not actual resistors)

SSM:

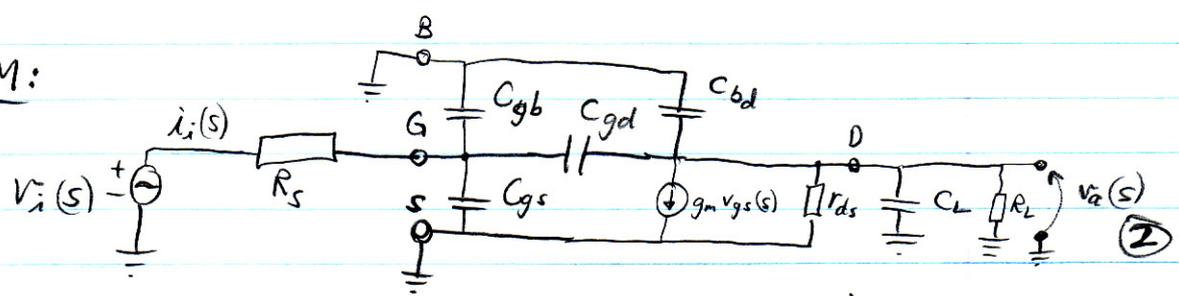

Let  $C_{gs}' = C_{gs} + C_{gb}$  ( $\approx C_{gs}$  usually)

$C_d = C_{bd} + C_L$

$R_L' = R_L \parallel r_{ds}$

eg. for  $I_D = 200 \mu A$ ,  $\frac{W}{L} = 50$ ,  $C_{gs}' = 90 \text{ fF}$ ,  $C_{gd} = 20 \text{ fF}$ ,  $C_d = 80 \text{ fF}$ ,  $g_m = 1.710^{-3} \Omega^{-1}$ ,  $r_{ds} = 500 \text{ k}\Omega$  } (3)

Note: (2) also SSM of diff pair DM  $\frac{1}{2}$  circuit

KCL at G:  $\frac{v_i(s) - v_{gs}(s)}{R_s} - v_{gs}(s) \cdot s \cdot C_{gs}' - [v_{gs}(s) - v_a(s)] \cdot s \cdot C_{gd} = 0$

$\therefore v_{gs}(s) = \left[ \frac{1}{\frac{1}{R_s} + s(C_{gs}' + C_{gd})} \right] (v_a(s) \cdot s \cdot C_{gd} + v_i(s) \cdot \frac{1}{R_s})$  (4)

KCL at D:  $[v_{gs} - v_a(s)] \cdot s \cdot C_{gd} - g_m v_{gs}(s) - v_a(s) \left[ \frac{1}{R_L'} + s C_d \right] = 0$

$\therefore v_a(s) = \left[ \frac{1}{\frac{1}{R_L'} + s(C_d + C_{gd})} \right] (s C_{gd} - g_m) \cdot v_{gs}(s)$  (5)


Let  $G(s) = \frac{1}{R_s} \left[ \frac{1}{\frac{1}{R_s} + s(C_{gs}' + C_{gd})} \right]$   
 $A(s) = \frac{s C_{gd} - g_m}{\frac{1}{R_L'} + s(C_d + C_{gd})}$ ,  $F(s) = -s C_{gd} \left[ \frac{1}{\frac{1}{R_s} + s(C_{gs}' + C_{gd})} \right]$  } (6)

5/5

Jan 15, 2008

$$\left. \begin{aligned} (4), (6) &\Rightarrow v_{gs}(s) = -F(s)v_a(s) + G(s)v_i(s) \\ (5), (6) &\Rightarrow v_a(s) = A(s) \cdot v_{gs}(s) \end{aligned} \right\} (7)$$

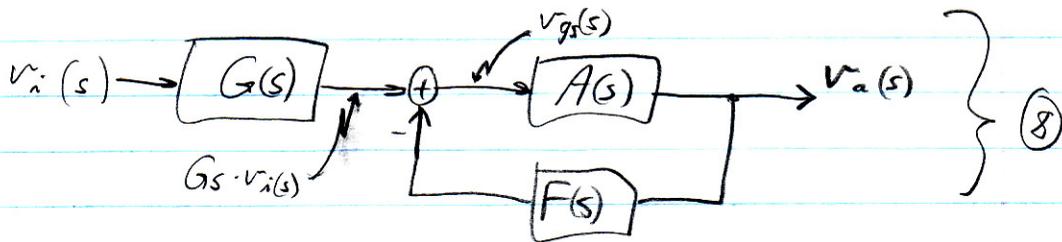(7)  $\Rightarrow$  "Block Diagram" of (2):



$$\left. \begin{aligned} (8) \text{ using Mason's gain formula} \\ \text{OR} \\ (7) \text{ using algebra} \end{aligned} \right\} \Rightarrow A_v(s) = G(s) \frac{A(s)}{1 + A(s)F(s)} \quad (9)$$


$$\equiv \left( \frac{v_a(s)}{v_i(s)} \right)$$

### Block Diagrams


SSM  $\iff$  system of equations in  $s$   $\iff$  block diagram  
 (eg. (2))  $\iff$  (eg. (4) & (5))  $\iff$  (eg. (8))

- SSM is symbolic  $\Rightarrow$  good for insight
- but components are bidirectional  $\Rightarrow$  bad for insight
- can't go directly from SSM to gain & impedances (need syst. of eqs. first)
- Block diagrams provide insight because components are uni-directional  $\Rightarrow$  Feedback paths are obvious
- Can go directly from block diagrams to gain & impedances (using Mason's gain formula)

SSM of CS Amp. (recall from last time)

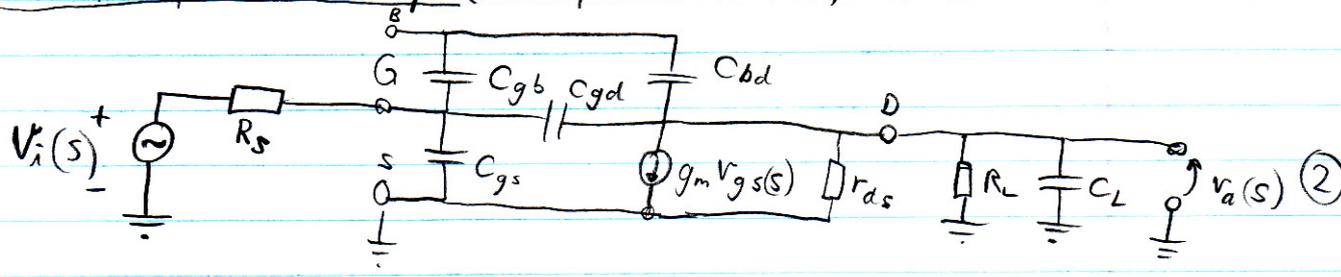
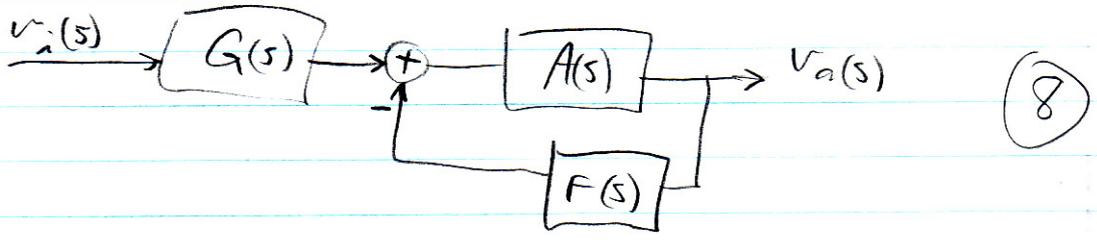
$$\left. \begin{aligned} v_{gs}(s) &= -F(s) \cdot v_a(s) + G(s) v_i(s) \\ v_a(s) &= A(s) \cdot v_{gs}(s) \end{aligned} \right\} \textcircled{7}$$



$$A_r(s) = G(s) \cdot \frac{A(s)}{1 + A(s)F(s)} \textcircled{9}$$

Recall Stability  $\Leftrightarrow$  no poles in RHP (incl. imag axis?)<sub>E.G.</sub>

$$\textcircled{9} \Rightarrow \dots \Leftrightarrow A(s_0)F(s_0) \neq -1 \text{ for any } s_0 \text{ with } \text{Re}\{s_0\} \geq 0$$

(assumes  $F(s) \neq 0$  and no pole of  $A(s)$  is a zero of  $F(s)$ )

First consider  $A_{r_0} = A_r(j\omega)|_{\omega=0}$  "DC-gain"

$$A_{r_0} = G(j\omega) \frac{A(j\omega)}{1 + A(j\omega)F(j\omega)} \Big|_{\omega=0}$$

Jan 17, 2008

(2/5)

$F(j\omega)|_{\omega=0} = 0$  (makes sense because  $F(s)$  represents feedback through  $C_{gd}$ )

$\therefore A_{v0} = -g_m R_L'$  (10)

Now consider poles & zeros: Let  $H(j\omega) = \frac{1}{A_{v0}} \cdot A_v(j\omega)$

$\therefore A_v(j\omega) = A_{v0} \cdot H(j\omega)$


(6), (9)  $\Rightarrow H(s) = \frac{1 - s/z_1}{1 + a_1 s + a_2 s^2}$

where  $\begin{cases} z_1 = g_m / C_{gd} \\ a_1 = R_s [C_{gs} + C_{gd} (1 + g_m R_L')] + R_L' (C_{gd} + C_d) \\ a_2 = R_s R_L' [C_d C_{gs} + C_d C_{gd} + C_{gs} C_{gd}] \end{cases}$

$\therefore A_v(s) = A_{v0} \left[ \frac{1 - s/z_1}{(1 - s/p_1)(1 - s/p_2)} \right]$  where  $\left. \begin{aligned} p_1 &= -\frac{1}{2a_2} (a_1 + \sqrt{a_1^2 - 4a_2}) \\ p_2 &= -\frac{1}{2a_2} (a_1 - \sqrt{a_1^2 - 4a_2}) \end{aligned} \right\}$  (11)

Usually, device parameters  $\Rightarrow a_1^2 > 4a_2$  for CS amp.  
 $\Rightarrow p_1, p_2$  are real

pole-zero diagram

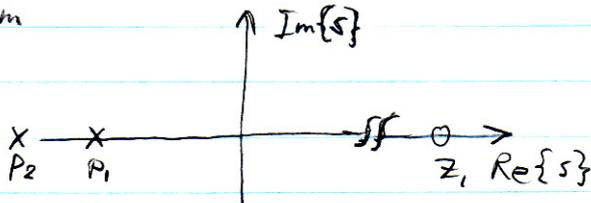

Hand-analysis:  
 10~20%  
 accuracy

Ex Using (3) with  $R_L = 10k\Omega$ ,  $R_s = 5k\Omega$  gives

$A_{v0} = -15.5$ ,  $f_z = \frac{z_1}{2\pi} = 13.56 \text{ GHz}$ ,  $f_{p1} = \left| \frac{p_1}{2\pi} \right| = 56 \text{ MHz}$

$f_{p2} = \left| \frac{p_2}{2\pi} \right| = 860 \text{ MHz}$

$\left. \begin{aligned} |p_1| &\ll |p_2| \\ |p_1| &\ll |z_1| \end{aligned} \right\} \Rightarrow p_1 = \text{dominant pole}$

$\Rightarrow |A_v(j\omega)| \approx \left| A_{v0} \left( \frac{1}{1 + j\omega / (2\pi \cdot 56 \text{ MHz})} \right) \right|$  for  $\omega \ll f_{p2} \cdot 2\pi$

$$\Rightarrow 3\text{dB BW} = 56\text{ MHz}$$

Now consider ① with capacitor  $C_c$  connected between D and G.

$\Rightarrow C_c$  in parallel with  $C_{gd}$  in ②

$\Rightarrow$  All eq. so far hold if  $C_{gd}$  is replaced } ⑫  
by  $C' = C_{gd} + C_c$


Can show using ⑪ & ⑫ (exercise)

$$p_1 \approx -\frac{1}{(C_d + C')R_L + (C_{gs}' C')R_s + g_m R_s R_L C'} \quad (13)$$

$$\approx \frac{-1}{g_m R_s R_L C'} \quad (\text{for large } R_s \& R_L)$$

$$p_2 \approx \frac{-g_m C'}{C_d C_{gs}' + C'(C_d + C_{gs}')}$$

$$z_1 = \frac{g_m}{C'}$$

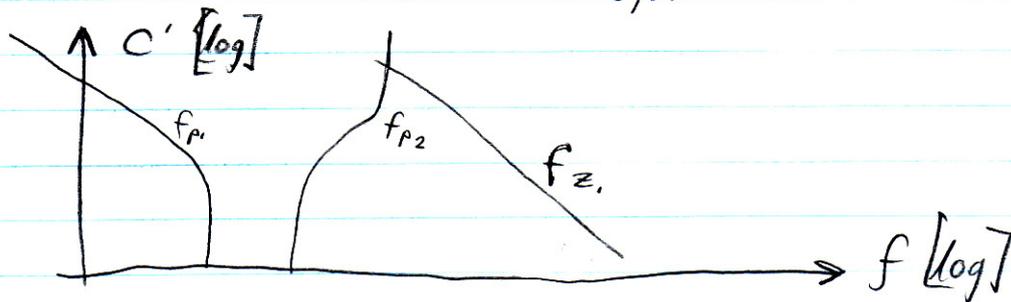



$\therefore$  Increasing  $C'$  splits poles but moves zero closer to origin

Reset Numbering system!

4/5

# Zero-Value Time Constant Analysis

Ex Recall CS Amp

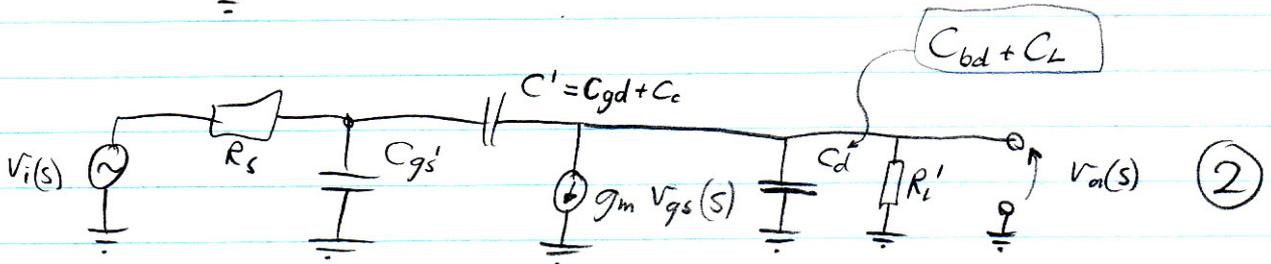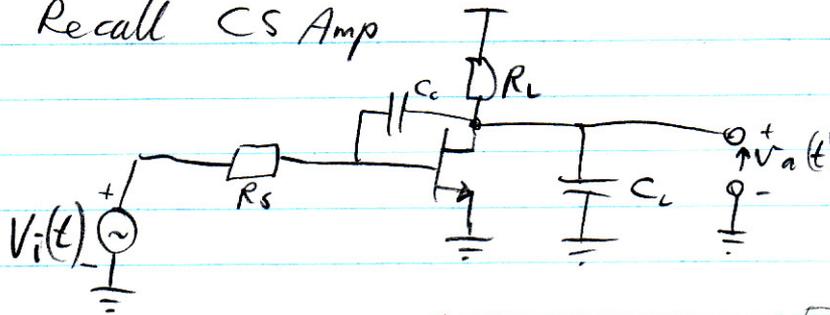

Last time: hard work gave us  $p_1 \approx \frac{-1}{(C_d + C')R_L' + (C_{gs}' + C)R_s + g_m R_L' R_s C'}$  (3)

$p_1 = \text{dom. pole so } 3\text{dB BW} = \left| \frac{f_1}{2\pi} \right|$

Q If only interested in dom. pole ( $\Rightarrow$  3dB BW) is there an easier way?

A Yes - ZVTC Analysis

## ZVTC Theorem

$\beta_1 = \text{negative of } \Sigma \text{ of all poles}$

Consider circuit containing only sources, resistors and capacitors and poles  $p_1, p_2, \dots, p_n$  where  $p_k \neq 0$

Let  $\beta_1 = -\sum_{k=1}^n +1/p_k$

$-\sum(\text{invers ar pol}) = \sum \text{tidskonst.}$

Then  $\beta_1 = \sum_{k=1}^n R_k C_k$  (4)

where  $C_k = \text{value of } k^{\text{th}} \text{ cap in circuit}$

and  $R_k = \text{resistance between nodes of circuit to which}$

$C_k$  is connected (i.e. impedance with all

caps removed)

Ex (cont...)


|p1| << |p2| => beta1 approx 1/|p1| :. p1 approx -1/beta1

Let Cgs' = C1, Cd = C2, C' = C3 (5)

Inspection of (2) => R1 = Rs

R2 = RL'

To find R3 use

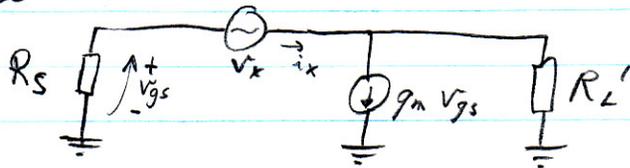

=> vgs = -ix \* Rs, vx = (ix - gm\*vgs) \* RL' - vgs } R3 = RL' + Rs + gm \* RL' \* Rs

(4) => p1 approx -1 / (Rs \* Cgs' + RL' \* Cd + (RL' + Rs + gm \* RL' \* Rs) \* C') = (3) ✓

Z.V.T.C. Analysis

Vi vet ikke sikkert hvilket RC-ledd som er størst... Men vi gjør et estimat:

W3dB approx |pdom| approx 1 / sum\_k Ck \* Rk

approx sum\_k 1/pk


"Zero Value" refererer muligens til at alle "de andre" kondensatorne er nullstilte. På norsk heter det "åpen krets tidskonstantmetoden".

(Nedre grensefrekvens: "Kortslutnings-tidskonstantmetoden", basert på sum\_k 1/(Ck \* Rk))

ZVTC Theorem (contd.) (same # system)PROOF:-

Have:

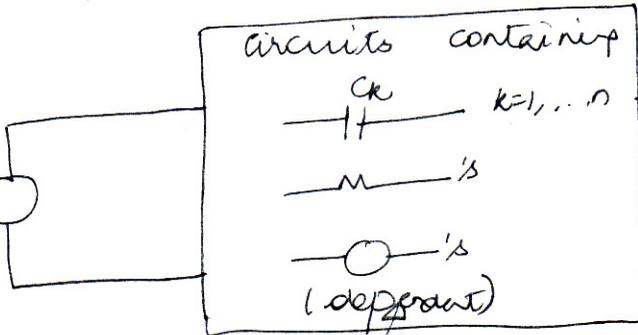Impulse:  
 $V_i(t) = \delta(t)$   
 $(V_i(s) = 1)$



Impulse Response

$$V_o(t) = g(t)$$

$$(V_o(s) = G(s))$$

②

∴ For calculating  $R_s$  &  $G(s)$  we need to turn off independent sources


where  $G(s) = A_0 \frac{P(s)}{(1-s/p_1)(1-s/p_2) \dots (1-s/p_n)}$

$P(s) \leftarrow$  some polynomial


Note: In ②,  $V_i(t) = \delta(t)$  sets initial condition of each capacitor  $C_k, k=1, \dots, n$ . After  $t=0$ ,  $V_i(t) = 0$  (At least one cap will get charged)

$\Rightarrow g(t) =$  transient of (2) if  $v_i(t) = 0$  but with appropriate initial conditions on  $C_1, C_2, \dots, C_n$ .

$\therefore$  (2) is equivalent to

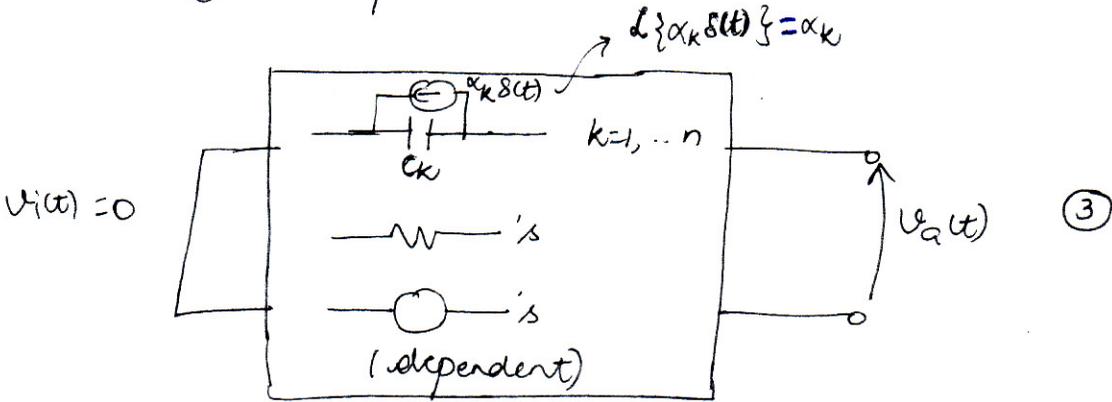


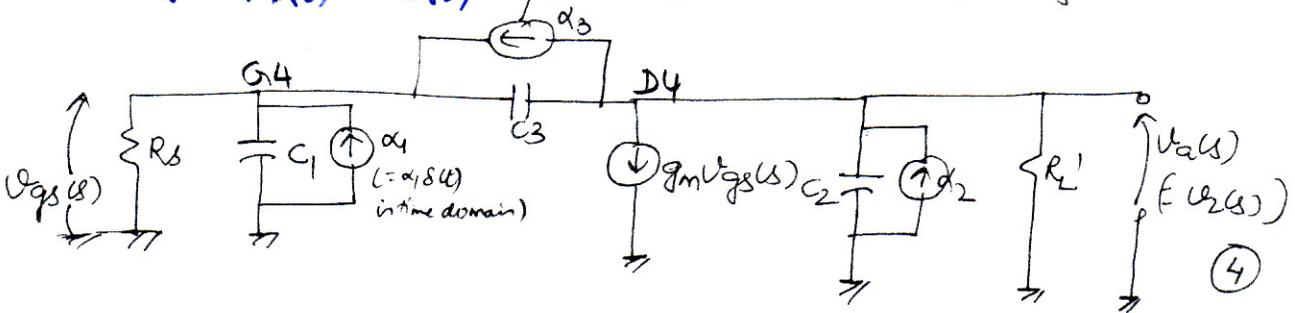e.g. s.s.m. of G.S. amplifier (last time)  
 if  $v_i(t) = \delta(t)$  produces some  $v_o(t)$  as



**NOTE:** To be specific will use (4) in place of (3) for today  
 But all results we find generalize to (3).

Define  $v_k$  and  $i_k$  as

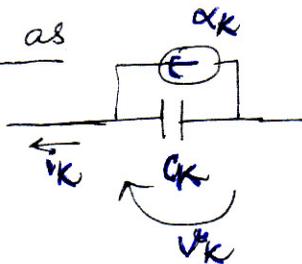

$$i_k(s) = \alpha_k - v_k(s) \cdot s C_k \quad (5)$$

KCL @ any node  $\Rightarrow$  equation of the form:

$$d_1 i_1(s) + d_2 i_2(s) + d_3 i_3(s) + g_1 v_1(s) + g_2 v_2(s) + g_3 v_3(s)$$

$= 0$

where  $d_k = 1, 0, \text{ or } -1$  (corresponding to current entering, leaving, or leaving a node)

and  $g_k =$  some conductance

e.g. KCL @ gate of ④:

$$-i_1(s) - i_3(s) + \frac{1}{R_S} v_1(s) = 0$$

Can solve all the equations of this form to get:

$$i_1(s) = a_{11} v_1(s) + a_{12} v_2(s) + a_{13} v_3(s)$$

$$i_2(s) = a_{21} v_1(s) + a_{22} v_2(s) + a_{23} v_3(s)$$

$$i_3(s) = a_{31} v_1(s) + a_{32} v_2(s) + a_{33} v_3(s)$$

⑥ where  $a_{jk} =$  some conductance

Note: To force ⑥ to be linearly independent, may need to add tiny resistors in series w/ some of the caps (add conceptually, not physically) ("tiny"  $\Leftrightarrow$  small enough to have negligible effect on ckt.)

In matrix notation, ⑥ is  $\underline{i}(s) = \underline{A} \cdot \underline{v}(s)$

$$\underline{i}(s) = \begin{bmatrix} i_1(s) \\ i_2(s) \\ i_3(s) \end{bmatrix}_{3 \times 1}, \quad \underline{A} = \begin{bmatrix} a_{11} & a_{12} & a_{13} \\ a_{21} & a_{22} & a_{23} \\ a_{31} & a_{32} & a_{33} \end{bmatrix}_{3 \times 3}, \quad \& \quad \underline{v}(s) = \begin{bmatrix} v_1(s) \\ v_2(s) \\ v_3(s) \end{bmatrix}_{3 \times 1}$$

Ladning på kondensatorne i start øjeblikket?

Using ⑤<sub>1</sub>:

$$\begin{bmatrix} \alpha_1 \\ \alpha_2 \\ \alpha_3 \end{bmatrix} = \begin{bmatrix} (a_{11} + sC_1) & a_{12} & a_{13} \\ a_{21} & (a_{22} + sC_2) & a_{23} \\ a_{31} & a_{32} & (a_{33} + sC_3) \end{bmatrix} \underline{v}(s) \quad \text{⑦}$$

Call  $\underline{\alpha}$  Call  $\underline{B}$

(Real life: c.s. Amp: 3 caps, 2 poles)

Recall "Cramer's Rule"

$$\Rightarrow v_k(s) = \frac{\Delta_k(s)}{\Delta(s)} \quad \text{where } \Delta(s) = \det(\underline{B}) \quad (= \text{polynomial in } s)$$

$$\Delta_k(s) = \det(\underline{B} \text{ with } k\text{th column replaced by } \underline{\alpha})$$

	unit
$\dot{i}(s)$	A·sec
$v(s)$	V·sec
$A, B$	$\sigma = \frac{A}{V} = \text{Siemens}$
$\alpha$	$C = \text{A·sec}$

$$\begin{aligned}
 \textcircled{5} \& \textcircled{6} \Rightarrow \alpha_1 &= \dot{i}_1(s) + v_1(s) \cdot s \cdot C_1 \\
 &= a_{11} \cdot v_1(s) + a_{12} \cdot v_2(s) + a_{13} \cdot v_3(s) + v_1(s) \cdot s \cdot C_1 \\
 &= (a_{11} + sC_1) \cdot v_1(s) + a_{12} \cdot v_2(s) + a_{13} \cdot v_3(s) \\
 &\Rightarrow \textcircled{7}
 \end{aligned}$$

Notes:

$$V_2(s) = V_1(s) \text{ in } \textcircled{4}, \text{ so } G(s) = \frac{\Delta_2(s)}{\Delta(s)} \quad \textcircled{8}$$

Jan 22, 2008

9.

(i.e. we can calculate impulse response from cramer's rule)

We know denominator of  $G(s)$  has form:  $b_0 + b_1 s + b_2 s^2$

$$= b_0 (1 + \beta_1 s + \beta_2 s^2)$$

(Because of pole-zero cancellation, we have 2nd order polynomial in real life rather than 3rd order polynomial)

$$= b_0 (1 - s/p_1) (1 - s/p_2)$$

$$\text{Algebra } \Rightarrow \beta_1 = \underbrace{-\sum_{k=1}^n 1/p_k}_{\text{true for any } n \geq 1}, \quad n=2$$

$$\textcircled{7}, \textcircled{8}, \text{ defn. of } \det(B) \Rightarrow b_0 = \Delta(s) \Big|_{G=C_2=C_3=0} = \Delta(0) \quad \textcircled{9}$$

$$\& \quad b_0 \beta_1 s \equiv b_1 s = h_1 s c_1 + h_2 s c_2 + h_3 s c_3$$

where  $h_1, h_2, h_3$  are real #'s, i.e.  $\in \mathbb{R}$

Let  $\Delta_{ij} = (-1)^{i+j} \det(\underline{B}_{ij})$  where  $\underline{B}_{ij} = \underline{B}$  with  $i$ th row &  $j$ th column deleted.

Can expand  $\det(\underline{B})$  as

$$\Delta(s) = (a_{11} + s c_1) \Delta_{11} + a_{21} \Delta_{21} + a_{31} \Delta_{31}$$

inspection of  $\textcircled{7} \Rightarrow c_1$  only occurs in 1st term

$$\therefore h_1 = \Delta_{11} \Big|_{c_2=c_3=0} = \Delta_{11}'(0)$$

Similarly,  $h_2 = \Delta_{22}(0)$ ,  $h_3 = \Delta_{33}(0)$

Jan 22, 2008 **10.**

$$\therefore \textcircled{1} \Rightarrow \beta_1 = \frac{\Delta_{11}(0)}{\Delta(0)} \cdot c_1 + \frac{\Delta_{22}(0)}{\Delta(0)} \cdot c_2 + \frac{\Delta_{33}(0)}{\Delta(0)} \cdot c_3$$

Now set  $c_1 = c_2 = c_3 = 0$

&  ~~$i_1$~~   $i_2 = i_3 = 0$  to get

$$\begin{bmatrix} i_1 \\ 0 \\ 0 \end{bmatrix} = \underline{A} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \end{bmatrix}$$

Cramer's Rule  $\Rightarrow v_1 = i_1 \det \begin{pmatrix} a_{22} & a_{23} \\ a_{32} & a_{33} \end{pmatrix}$

$\det(\underline{A})$

$$= i_1 \frac{\Delta_{11}(0)}{\Delta(0)} \quad \text{by defn.}$$

$$\therefore \left. \frac{v_1}{i_1} \right|_{c_1=c_2=c_3=0} = R_1 = \frac{\Delta_{11}(0)}{\Delta(0)}$$

$$i_2 = i_3 = 0$$

Similarly for  $R_2$  and  $R_3$

$$\therefore \beta_1 = R_1 c_1 + R_2 c_2 + R_3 c_3$$

1) One pole should dominate


2) One pole should dominate

1/5


(o.k. tomorrow with TA 11:00~12:30 in EBUL3329)

Freq resp of common gate (cascode) stage


assume Body to ground (lowest potential)

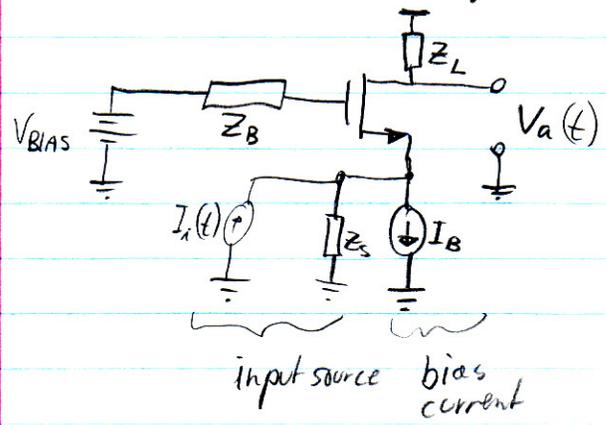

assume

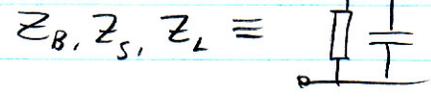

SSM

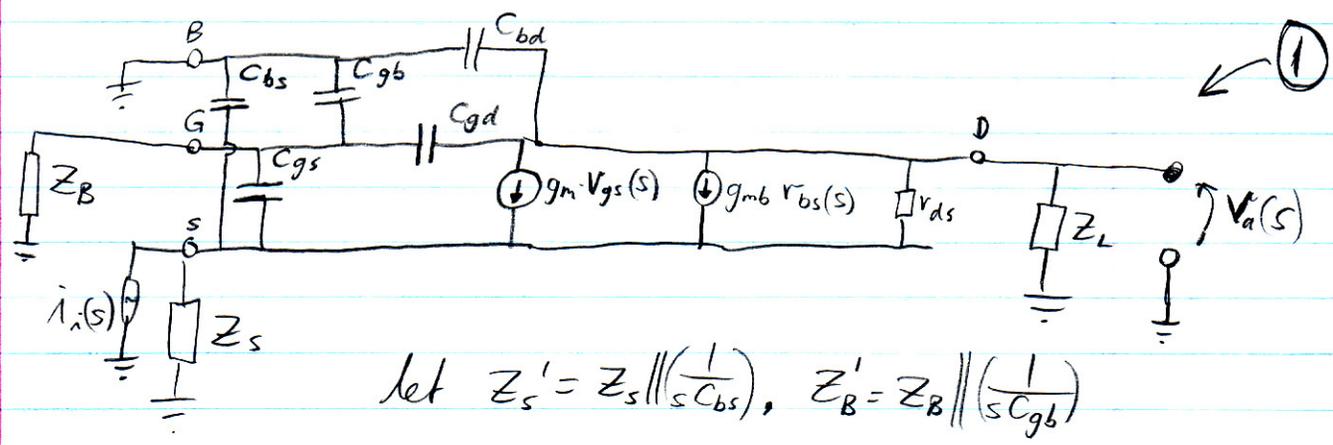

let  $Z'_s = Z_s \parallel \left( \frac{1}{s C_{bs}} \right)$ ,  $Z'_B = Z_B \parallel \left( \frac{1}{s C_{gb}} \right)$

$Z'_L = Z_L \parallel \frac{1}{s C_{bd}}$

KCL: (at G)  $\frac{V_g}{Z'_B} + (V_g - V_d) s C_{gd} + (V_g - V_s) s C_{gs} = 0$

$\therefore V_g = \left[ \frac{1}{Z'_B} + s(C_{gd} C_{gs}) \right]^{-1} \cdot [s C_{gs} V_s + s C_{gd} V_d]$  (2)

call it a(s)

KCL: (at S)  $\dots V_s = \left[ \frac{1}{Z'_s} + g_m + g_{mb} + \frac{1}{r_{ds}} + s C_{gs} \right]^{-1} \left[ I_i + (g_m + s C_{gs}) V_g + \frac{1}{r_{ds}} V_d \right]$  (3)


call it b(s)

KCL :  $\infty$

$$\frac{1}{(s+D)} v_d = \left[ \frac{1}{Z_i} + \frac{1}{r_{ds}} + sC_{gd} \right]^{-1} \left[ \left( \frac{1}{r_{ds}} + g_m + g_{mb} \right) v_s + (sC_{gd} - g_m) v_g \right] \quad (4)$$

call it  $C(s)$

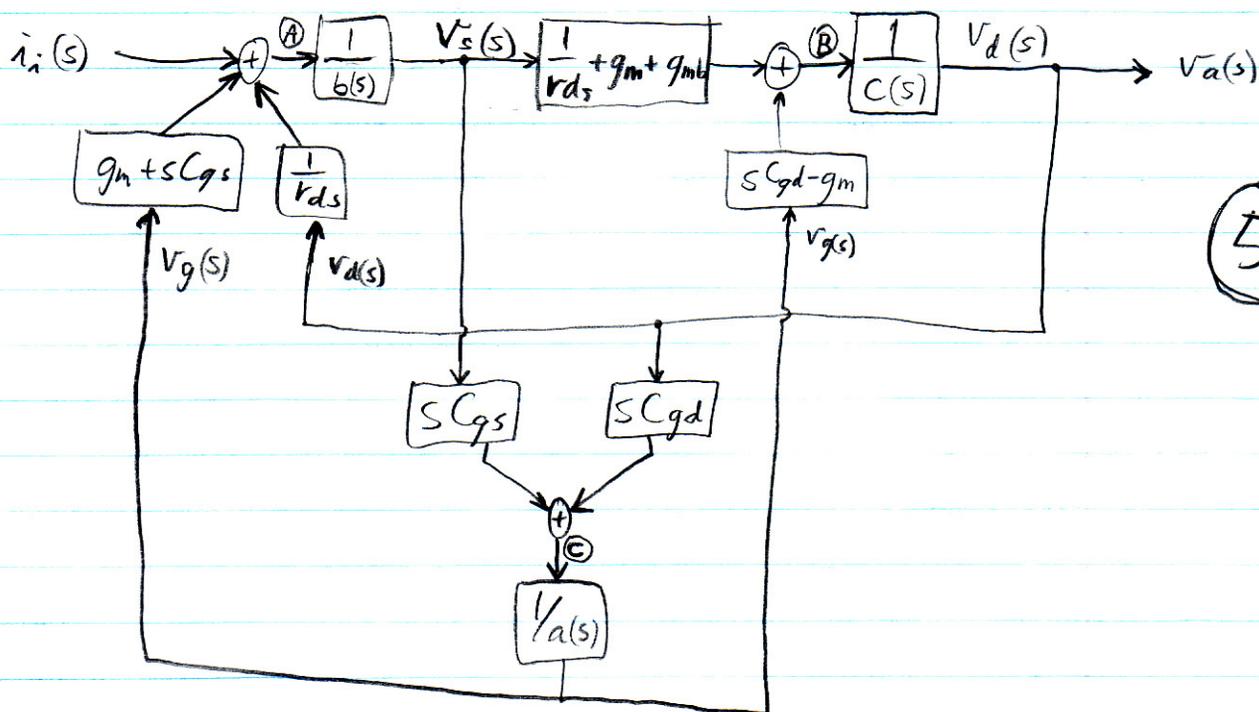can generate "block diagram" from (2), (3), (4):



(5)

- Observations
- 1) all blocks are unidirectional (in dir. of the arrows)
  - 2) all feedback paths arise from parasitic elements (i.e. if  $C_{xy} = 0, r_{ds} = \infty$ , then no feedback loops) with  $C_{xy} = 0, r_{ds} = \infty$ , (5) reduces to

$$i_i(s) \rightarrow \left[ \frac{1}{b(s)} \right] \rightarrow [g_m + g_{mb}] \rightarrow \left[ \frac{1}{C(s)} \right] \rightarrow v_a(s) \quad (6)$$

$$= \frac{1}{Z'_s + g_m + g_{mb}} = Z'_L$$

$$\therefore \frac{v_a(s)}{i_i(s)} \Big|_{C_{xy}=0, r_{ds}=\infty} = \frac{Z'_L (g_m + g_{mb})}{Z'_s + g_m + g_{mb}} = \frac{Z'_L Z'_s (g_m + g_{mb})}{1 + (g_m + g_{mb}) Z'_s} \quad (7)$$

$\rightarrow Z'_L a_s \mid Z'_s \rightarrow \infty$

3/5

Jan 24, 2008

Inspection of (6)  $\Rightarrow$  (7)

Q: Can we find  $\frac{v_a(s)}{i_i(s)} \Big|_{C_{xy} \neq 0, r_{ds} \neq \infty}$  from (5) by inspection?

A: Yes. Using Mason's Gain Formula (M.G.F.)

Application of MGF to (5)

- "Loops":
- 1:  $A \rightarrow B \rightarrow A$
  - 2:  $A \rightarrow C \rightarrow A$
  - 3:  $A \rightarrow C \rightarrow B \rightarrow A$
  - 4:  $A \rightarrow B \rightarrow C \rightarrow A$
  - 5:  $B \rightarrow C \rightarrow B$

Note: All loops touch each other

- "Forward Paths":
- 1:  $i_i \rightarrow A \rightarrow B \rightarrow v_d$
  - 2:  $i_i \rightarrow A \rightarrow C \rightarrow B \rightarrow v_d$

Note: deleting either path breaks all loops

"Loop gains":  $L_1 = \left(\frac{1}{r_{ds}} + g_m + g_{mb}\right) \frac{1}{r_{ds} b(s) c(s)}$

$$L_2 = s C_{gs} (g_m + s C_{gs}) \cdot \frac{1}{a(s) \cdot b(s)}$$

$$L_3 = s C_{gs} (s C_{gd} - g_m) \frac{1}{r_{ds} a(s) b(s) c(s)}$$

$$L_4 = s C_{gd} (g_m + s C_{gs}) \left(\frac{1}{r_{ds}} + g_m + g_{mb}\right) \cdot \frac{1}{a(s) b(s) c(s)}$$

$$L_5 = s C_{gd} (s C_{gd} - g_m) \frac{1}{a(s) c(s)}$$

(8)

"Path gains"  $P_1 = \left(\frac{1}{r_{ds}} + g_m + g_{mb}\right) \cdot \frac{1}{b(s) c(s)}$

$$P_2 = s C_{gs} (s C_{gd} - g_m) \cdot \frac{1}{a(s) b(s) c(s)}$$

(9) ← (units:  $\Omega$ )

Fact M.G.F.  $\Rightarrow \frac{v_a(s)}{i_i(s)} = \frac{P_1 + P_2}{1 - L_1 - L_2 - L_3 - L_4 - L_5}$

(10) (Both paths touch all the loops)

$\therefore$  Can easily find  $G(s) = \frac{v_a(s)}{i_i(s)}$  but it's really messy to look at

For negligible capacitance in  $Z_L, Z_B$  and  $Z_S$  then

$$G(s) \cong \frac{\text{second order poly.}}{\text{third order poly.}} \quad \left. \begin{array}{l} (a(s), b(s) \& c(s) \text{ are} \\ \text{1st order polys.}) \end{array} \right\} \begin{array}{l} \text{conductance} \\ \text{(Siemens)} \end{array}$$

(Call full version of  $G(s)$  (11))  $\Downarrow$


The good news is (11) = "exact" expr.  
 The bad news is ——— " ———  
 (exact expr. is too complicated to give insight)

have third-order system with  $\left\{ \begin{array}{l} 2 \text{ zeros} \\ 3 \text{ poles} \end{array} \right\}$

Q So what now?

A Plug in numbers (ie. freq. and comp. values) into boxes in (5) and eliminate highly attenuated paths.

Ex  $Z_B$  usually arises from parasitics  
 - often  $Z_B \neq 0$  causes stability problems in feedback applications  
 $V_{BIAS} = DC$ , so we can use bypass cap to reduce  $|Z_B|$   
 $\therefore$  Suppose  $|Z_B| \cong 0$  Then  $\left| \frac{1}{a(s)} \right| \approx 0$  and (5) becomes  $\approx$

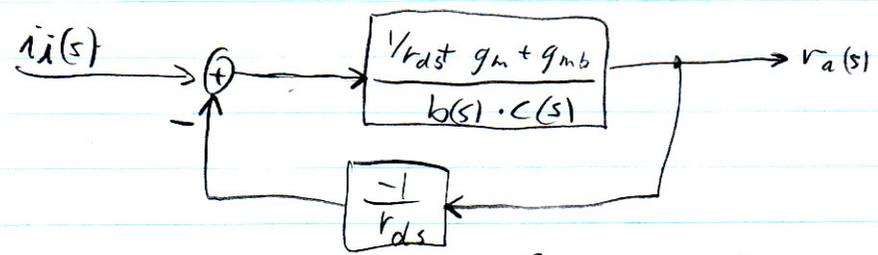

Now, MGF gives  $G(s) \Big|_{|Z_B|=0} = \frac{\left( \frac{1}{r_{ds}} + g_m + g_{mb} \right)}{b(s) \cdot c(s)} \cdot \frac{1}{1 - \frac{1}{r_{ds}} \left[ \frac{\left( \frac{1}{r_{ds}} + g_m + g_{mb} \right)}{b(s) \cdot c(s)} \right]}$

let  $g'_m = g_m + g_{mb}$  ( $\approx 1.2 \cdot g_m$ ) assume  $g_m \gg \frac{1}{r_{ds}}$

then  $b(s) = \frac{1}{Z'_s} + g'_m + sC_{gs}$ ,  $c(s) = \frac{1}{Z'_i} + \frac{1}{r_{ds}} + sC_{gd}$

(as before)

5/5

Jan 24, 2008

$$\therefore G(s) \Big|_{z_B=0} = \frac{g_m}{\left(\frac{1}{z_s} + g_m + sC_{gs}\right)\left(\frac{1}{z_l} + \frac{1}{r_{ds}} + sC_{gd}\right) - g_m/r_{ds}}$$

(13)

Sanity check: 1) units  $\checkmark$

$$2) A(j\omega) \Big|_{r_{ds}, z_s = \infty} = z_l \checkmark$$

(13)  $\Rightarrow$  2<sup>nd</sup> order behaviour: 2 poles, no zeros

$\Rightarrow$  always stable denom. of (13) has form  $\alpha_0 + \alpha_1 s + \alpha_2 \cdot s^2$

$$\text{with poles} = -\frac{\alpha_1}{2\alpha_2} \pm \frac{1}{2\alpha_2} \cdot \underbrace{\sqrt{\alpha_1^2 - 4\alpha_0\alpha_2}}_{< \alpha_1}$$

$$\therefore \text{Re}\{\text{poles}\} < 0$$


1/6.

closed book/notes (bring calc.) } mid-term  
 ↳ paper + penn (blyant)

Block diagrams & MGF (continued)

Ex: Diff to single-ended OTA


Operational transconductance amplifier

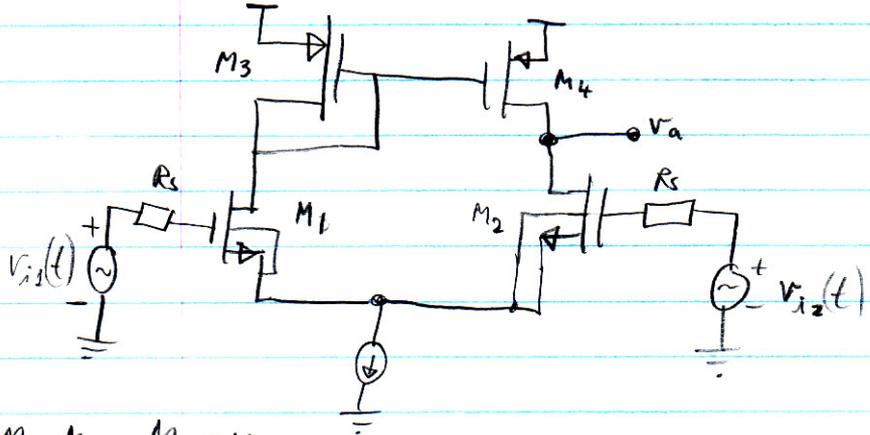

①

$M_1 = M_2, M_3 = M_4$

SSM of ①

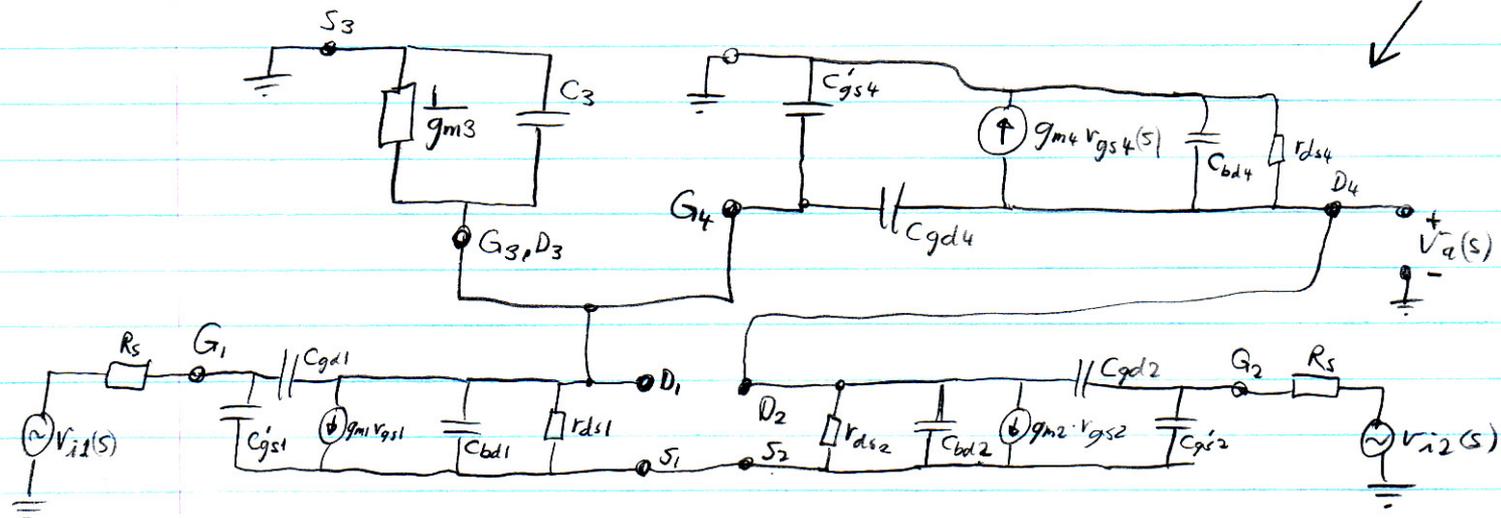

②


where  $C_{gsi} = C_{gsi} + C_{gsi}$ ,  $C_3 = C_{gs3} + C_{bd3}$

See textbook pp. 140-181

want to analyze differential mode (DM) operation:  $v_{i1} = \frac{v_{id}}{2}$ ,  $v_{i2} = -\frac{v_{id}}{2}$

Assume  $R_S = \text{negligible}$  for analysis

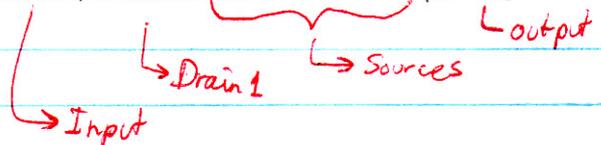want BD. contributing nodes:  $v_{id}$ ,  $v_{d1}$ ,  $v_s \equiv v_{s1} = v_{s2}$ ,  $v_a$



KCL at D1

$$v_{d1} [g_{m3} + s(C_3 + C_{gs4})] + \frac{v_{d1} - v_s}{r_{ds1} \parallel C_{bd1}} + (v_{d1} - v_a) s C_{gd4} + (v_{d1} - \frac{v_{id}}{2}) s C_{gd1} + (\frac{v_{id}}{2} - v_s) g_{m1} = 0$$

Where "rx // Cy" =  $(\frac{1}{r_x} + sC_y)^{-1}$

$$v_{d1} \left[ g_{m3} + \frac{1}{r_{ds1}} + s(C_3 + C'_{gs4} + C_{bd1} + C_{gd4} + C_{gd1}) \right] - v_s \left[ g_{m1} + \frac{1}{r_{ds1} \parallel C_{bd1}} \right] - v_a s C_{gd4} + \frac{1}{2} v_{id} (g_{m1} - s C_{gd1}) = 0$$

(call it a(s)) ≈ g<sub>m1</sub> + sC<sub>bd</sub>

$$\therefore v_{d1} = \frac{1}{a(s)} \left[ v_s (g_{m1} + s C_{bd1}) + v_a \cdot s \cdot C_{gd4} - \frac{1}{2} v_{id} (g_{m1} - s C_{gd1}) \right] \quad (3)$$

KCL at D2

...

$$\therefore v_a \approx \frac{1}{b(s)} \left[ v_s (g_{m2} + s C_{bd2}) + v_{d1} (s C_{gd4} - g_{m4}) + \frac{1}{2} v_{id} (g_{m2} - s C_{gd2}) \right] \quad (4)$$

where  $b(s) = \frac{1}{r_{ds4} \parallel r_{ds2}} + s(C_{bd4} + C_{bd2} + C_{gd4} + C_{gd2})$  (used  $g_{m2} \gg \frac{1}{r_{ds2}}$ )

KCL at S1, S2

...

$$\therefore v_s = \frac{1}{c(s)} \left[ \frac{v_{d1}}{r_{ds1} \parallel C_{bd1}} + \frac{v_a}{r_{ds2} \parallel C_{bd2}} \right] \quad (5)$$


} used  $M_1 = M_2$   
&  $M_3 = M_4$

where  $c(s) = g_{m1} + g_{m2} + s(C'_{gs1} + C'_{gs2})$

(3) ~ (5) ⇒ block diagram

$\left[ \frac{1}{a(s)} \right] = \left[ \frac{1}{b(s)} \right] = \left[ \frac{1}{c(s)} \right] = \Omega$

← 1<sup>st</sup> order polynomials

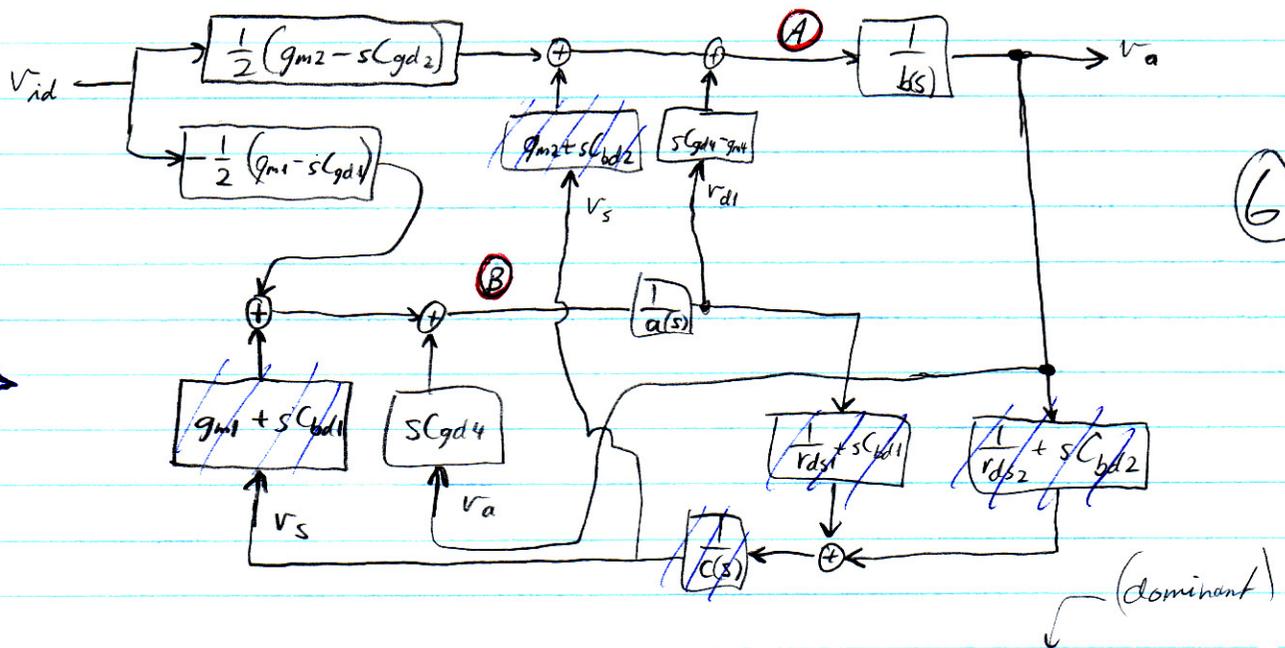

Let  $p_1, p_2, \dots$  be the poles  $A_v(s) = \frac{v_a(s)}{v_{id}(s)}$  with  $|p_1| \leq |p_2| \leq \dots$

Provided  $\left| \frac{1}{r_{ds1,2}} + j\omega C_{bd1,2} \right|$  is sufficiently small that  $|v_s(j\omega)| \ll |v_{d1}(j\omega)|, |v_a(j\omega)|$  for  $|\omega| \leq |p_2|$  (7)

can eliminate the  $v_s$  feedback paths in (6) (asymmetry  $\Rightarrow v_s \neq 0$ )

We'll assume (7) holds for now. Can later check the assumption by testing with resulting value of  $p_2$ .

Sanity check: Find  $A_{v0} = A_v(j\omega)|_{\omega=0} \quad \omega=0 \Rightarrow s=0$

$\therefore a(0) = g_{m2} \quad b(0) = \frac{1}{r_{ds2} \parallel r_{ds4}}$


$\therefore (6) \Rightarrow v_a = \left( \frac{1}{2} g_{m2} r_{ds2} \parallel r_{ds4} - \frac{1}{2} g_{m1} \cdot \frac{-g_{m4}}{g_{m3}} \cdot r_{ds2} \parallel r_{ds4} \right) v_{id}$

$\therefore A_{v0} = g_{m1} \cdot r_{ds2} \parallel r_{ds4} \quad (\checkmark)$

4/6

Jan 29, 2008

Now, apply MGF:

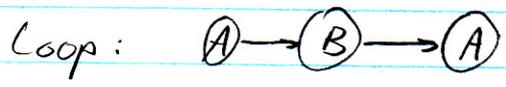

Forward paths 1.  $v_{id} \rightarrow A \rightarrow v_a$   
2.  $v_{id} \rightarrow B \rightarrow A \rightarrow v_a$

$$\textcircled{6} \Rightarrow P_1 = \frac{g_{m2} - sC_{gd2}}{2 - b(s)}, \quad P_2 = \frac{(g_{m1} - sC_{gd1})(g_{m4} - sC_{gd4})}{2 - a(s) - b(s)}$$

$$L_1 = \frac{sC_{gd4}(sC_{gd4} - g_{m4})}{a(s) b(s)}$$

$$\text{MGF} \Rightarrow A_v(s) = \frac{P_1 + P_2}{1 - L_1}$$

$$= \frac{1}{2} \cdot \frac{a(s)(g_{m2} - sC_{gd2}) + (g_{m1} - sC_{gd1})(g_{m4} - sC_{gd4})}{a(s)b(s) - sC_{gd4}(sC_{gd4} - g_{m4})}$$

8

⇒ 2 zeros, 2 poles

2<sup>nd</sup> order ⇒ can easily find poles & zeros, but results give little insight

Instead, note: { Feedback depends on  $sC_{gd4}$  (no Miller effect, why?)  
↳  $Z=0$  (source)  
Usually  $C_{gd4} \ll C_{gsi}, C_{bdi}$   
∴ Taking  $sC_{gd4} \approx 0$  in 8 = reasonable approximation

$$\text{Now, MGF} \Rightarrow A_v(s) = P_1 + P_2 \quad (L_1 \approx 0) = \frac{2^{\text{nd}} \text{ order poly}}{a(s) b(s)}$$
$$= g_{m1} (r_{ds2} \parallel r_{ds4}) \cdot \frac{(1 - s/z_1)(1 - s/z_2)}{(1 - s/p_1)(1 - s/p_2)}$$

$$\text{where } p_1 = \frac{-1}{(r_{ds2} \parallel r_{ds4}) c_2}, \quad p_2 = \frac{-g_{m3}}{c_1}$$

$$\text{where } c_1 = C_{gs3} + C_{bd3} + C_{gs4} + C_{bd1} + C_{gd1}$$
$$c_2 = C_{bd2} + C_{bd4} + C_{gd2}$$

5/6

Jan 29, 2008

$C_1, C_2$  have same order of mag }  $\Rightarrow p_1 = \text{dom pole}$   
 $r_{ds1} || r_{ds4} \gg 1/g_{m3}$  (typically) }  $p_2 = \text{non dom. pole}$  (next most dominant)

Observation

$\frac{1}{g_{m3}}$  = resistance to snail-signal  $\frac{1}{g_{m3}}$  at  $D_1$  in ②



$\therefore$  In ② could have found  $p_1$  and  $p_2$  by calculating  $R_i, C_i$   
 where  $R_i = \text{res to gnd. at node } i$



Then  $p_1 = \frac{-1}{\text{largest}\{R_i \cdot C_i\}}$ ,  $p_2 = \frac{-1}{\text{next largest}\{R_i \cdot C_i\}}$

Q : Coincidence ?

A : No. This method is reasonable approx in many cases (HW 2)

Slang: Because of this, people often say that the dominant pole occurs at node  $D_2$  and the non-dominant pole occurs at node  $D_1$ .

6/6.

Jan 29, 2008

# Full version of MGF

Block diagram defs.:

- 1) "Path"  $\equiv$  route through B.D. (in dir. of arrows) connecting a pair of nodes
- 2) "Path gain"  $\equiv$  product of block gains along path
- 3) "Loop"  $\equiv$  path which starts and ends at same node with no node along path encountered more than once
- 4) "Loop gain"  $\equiv$  path gain of loop
- 5) "Determinant"  $\equiv 1 - \sum$  (all loop gains)  
 $+ \sum$  (products of loop gains of all loop pairs with no common nodes)  
 $- \sum$  (triples)  
 $+ \sum$  (...)  
 ...
- 6) "Forward path"  $\equiv$  path from input to output containing no full loops

Let  $H = \frac{X_{out}}{X_{in}}$  where  $X_{in}$  = input of B.D.  
 $X_{out}$  = output of B.D.

Then  $H = \frac{1}{\Delta} \cdot \sum_{k=1}^L P_k \cdot \Delta_k$  (MGF)


where  $\Delta$  = determinant  
 $L$  = # of forward paths  
 $P_k$  =  $k^{th}$  forward path  
 $\Delta_k$  = determinant of B.D. that remains after deleting  $k^{th}$  path,  $P_k$

"cofactor" =  $\Delta$  with loops touching the  $k^{th}$  path removed.

1/6
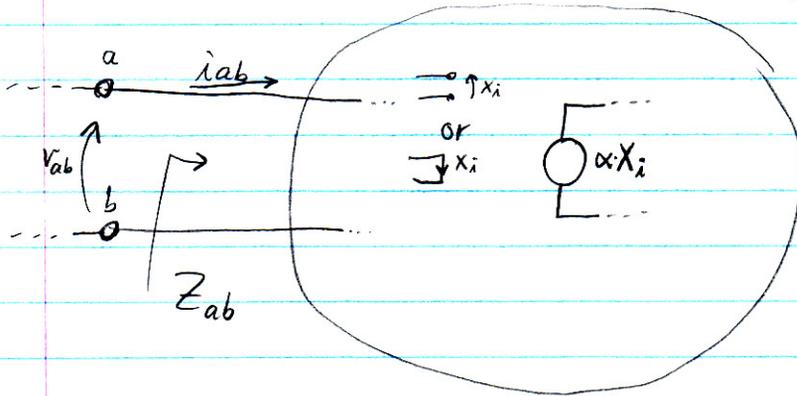
# Blackman's Impedance Relation

arbitrary SSM circuit containing  $\geq 1$  controlled sources



$X_i =$  voltage or current  
 $\alpha X_i =$  " " " "

(eg.  $X_i = V_{gs}$ ,  $\alpha = g_m$   
 $\alpha X_i =$  current)

BIR 
$$Z_{ab} = Z_{ab}^0 \cdot \frac{1 + T_{sc}}{1 + T_{oc}} \quad (1)$$

$\left( \equiv \frac{v_{ab}(s)}{i_{ab}(s)} \right)$

Nullstilt!

where  $Z_{ab}^0 \equiv$  Impedance between a and b with controlled source removed  
 $T_{sc} \equiv -\alpha \cdot \frac{X_i}{X_x}$  when  $v_{ab} = 0$  (a, b shorted) ( $\alpha = 0$ )

and  $\alpha X_i$  is replaced by an independent "test source",  $X_x$

$T_{oc} \equiv$  Same as  $T_{sc}$  except with  $i_{ab} = 0$  (a, b open circuited)


Note: if have more than one controlled sources, pick any one of them (call it the reference source).

T'ene er "loop gain"

See note of March 18, 2008

Ex 1 C.S. Amp

Recall SSM

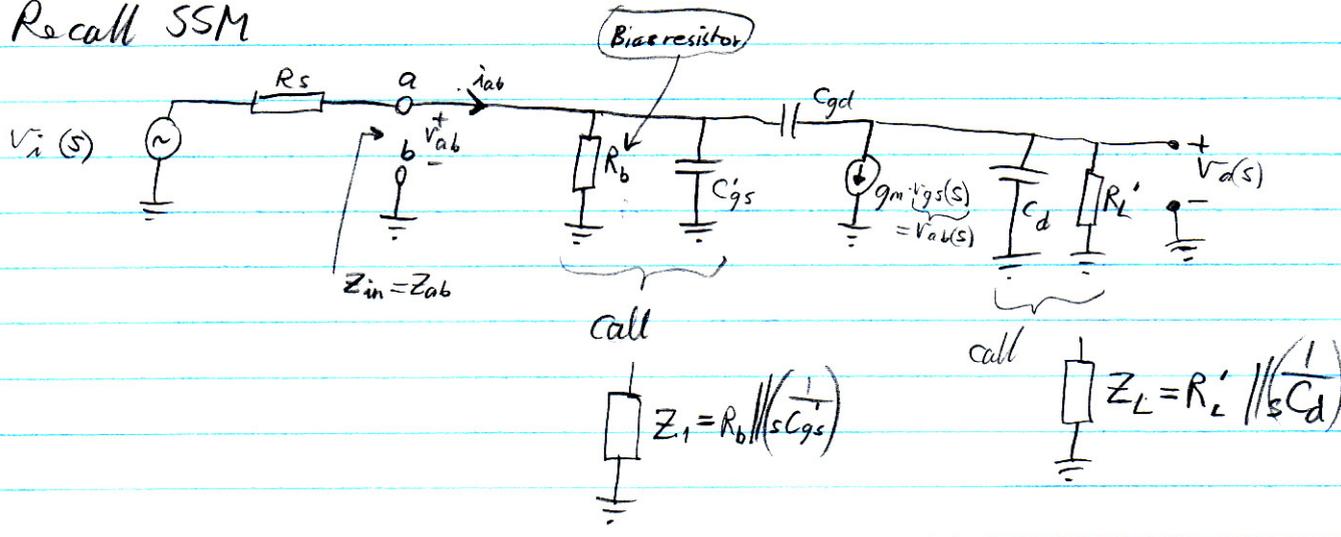

BIR:  $\alpha = g_m$ ,  $X_i = V_{ab}$ ,  $x_x = i_x$

$$Z_{ab}^o = Z_1 \parallel \left( \frac{1}{sC_{gd}} + Z_L \right) = \frac{Z_1 \cdot (1 + Z_L \cdot s \cdot C_{gd})}{1 + (Z_1 + Z_L) \cdot s \cdot C_{gd}}$$

$T_{sc} = 0$  (because  $X_i = V_{ab} = 0$ )

$$T_{oc} = -g_m \cdot \frac{1}{i_x} \left[ -i_x \left( Z_L \parallel \left( Z_1 + \frac{1}{sC_{gd}} \right) \right) \cdot \frac{Z_L}{Z_1 + \frac{1}{sC_{gd}}} \right]$$

$$= \frac{g_m Z_1 Z_L}{Z_L + Z_1 + \frac{1}{sC_{gd}}} \quad (\text{note } \rightarrow 0 \text{ as } C_{gd} \rightarrow 0)$$


$$\therefore \textcircled{1} \Rightarrow Z_{in} = Z_{ab}^o \cdot \frac{1}{1 + T_{oc}} = Z_1 \cdot \frac{1 + sC_{gd} \cdot Z_L}{1 + [Z_L + Z_1 + (1 + g_m Z_L)] \cdot s \cdot C_{gd}}$$

②

Miller effect

Observations

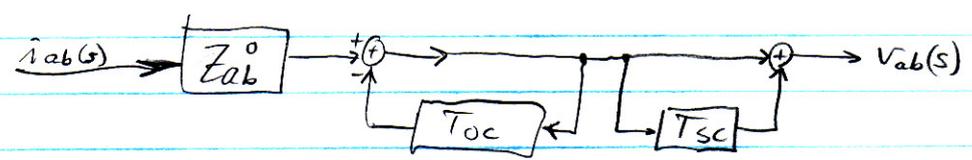
- 1)  $T_{oc}$  represents a feedback path around the reference source. Why? def  $\Rightarrow$  If output of ref. source has no connection to its controlling voltage (or current) then  $T_{oc} = 0$ . Also, MGF and ① give:



3/6

Jan 31, 2008


Or

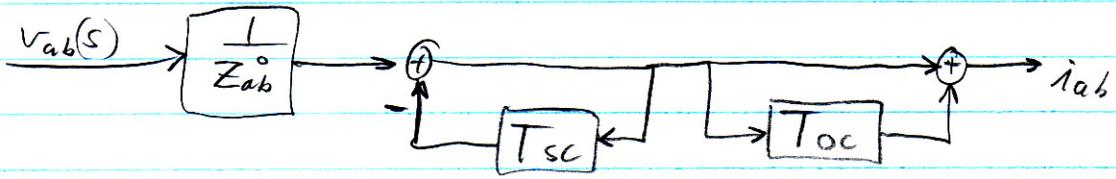

∴  $T_{sc}$  also arises from a feedback path within the circuit

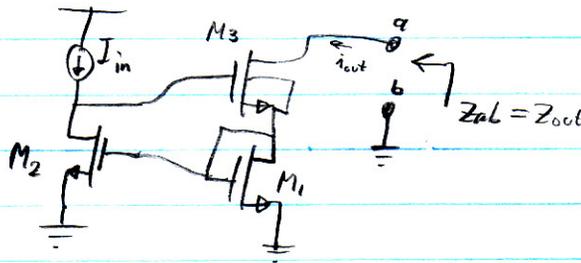
2) Feedback can either increase or decrease  $Z_{ab}$

Ex 2 Wilson current mirror (low freq analysis)



Low freq. SSM (Using  $\square \approx \square \parallel \frac{1}{g_{m1}}$ )

(Set  $i_{in} = 0$  to find  $Z_{out}$ )

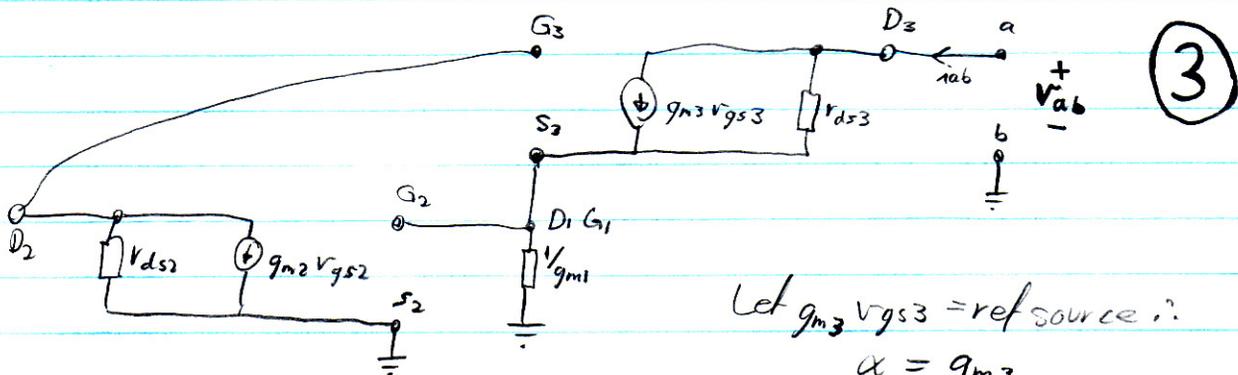

Let  $g_{m3} v_{gs3} = \text{ref source } \therefore$

$$\alpha = g_{m3}$$

$$X_i = v_{gs3}$$

Inspection of ③  $\Rightarrow Z_{ab}^o = r_{ds3} + \frac{1}{g_{m1}} \approx r_{ds3}$

4.16

Jan 31, 2008

T<sub>oc</sub> :  $i_{ab} = 0 \Rightarrow v_{gs2} = 0 \Rightarrow v_{gs3} = 0 \Rightarrow x_i = 0 \therefore T_{oc} = 0$

T<sub>sc</sub> : with  $g_{m3} v_{gs3}$  replaced by  $i_x$  and  $v_{ab} = 0$  have

$$\left. \begin{aligned} v_{gs2} &= i_x \left( r_{ds3} \parallel \left( \frac{1}{g_{m1}} \right) \right) \approx \frac{i_x}{g_{m1}} \\ \text{KVL} \Rightarrow v_{gs2} + v_{gs3} &= -g_{m2} v_{gs2} r_{ds2} \end{aligned} \right\} \Rightarrow v_{gs3} = -\frac{i_x}{g_{m1}} (1 + g_{m2} r_{ds2})$$


$$\therefore T_{sc} = \frac{g_{m3}}{g_{m1}} (g_{m2} r_{ds2} + 1) = g_{m3} r_{ds2} + 1$$

(for  $M_1 = M_2 = M_3$ )

$\therefore \textcircled{1} \Rightarrow Z_{ab} = r_{ds3} (2 + g_{m2} r_{ds2}) \therefore$  Feedback increased  $Z_{ab}$

Proof of BIR:

Linearity  $\Rightarrow$  can write

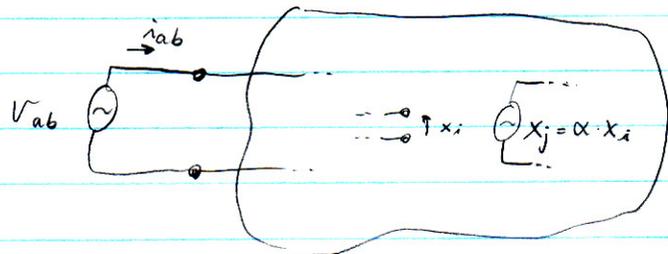

SSM circuit as before (all indep. sources set to zero)

$$\left. \begin{aligned} v_{ab} &= A \cdot i_{ab} + B \cdot X_j \\ X_i &= C \cdot i_{ab} + D \cdot X_j \end{aligned} \right\} \textcircled{4} \text{ (two-port representation)}$$

$A(s), B(s), C(s), D(s) \equiv$  transfer functions

Solving  $\textcircled{4}$  for  $Z_{ab} = \frac{v_{ab}}{i_{ab}}$  gives  $Z_{ab} = A \cdot \frac{1 - \frac{\alpha(AD-BC)}{A}}{1 - \alpha D}$   $\textcircled{5}$

$\textcircled{4} \Rightarrow A = \left. \frac{v_{ab}}{i_{ab}} \right|_{X_j=0} = \text{def of } Z_{ab}^0$   $\textcircled{6}$

Now suppose  $v_{ab} = 0$  and  $X_j = X_x$  (indep. of  $x_i$ )

Then  $\textcircled{4} \Rightarrow i_{ab} = -\frac{B}{A} X_x$   
 $X_i = C \cdot i_{ab} + D \cdot X_x$

$$\Rightarrow -\alpha \frac{X_i}{X_x} = -\frac{\alpha(AD-BC)}{A} \textcircled{7}$$

$\equiv T_{sc}$

5/6

Jan 31, 2008


Now suppose  $i_{ab} = 0$  and  $x_j = x_x$  (indep. of  $x_i$ )  
Then ④ similarly  $\Rightarrow T_{oc} = -\alpha D$  ⑧

$\therefore$  ⑤~⑧  $\Rightarrow Z_{ab} = Z_{ab}^o \cdot \frac{1+T_{sc}}{1+T_{oc}}$   $\square$

$\square$

Asymptotic Gain Relation

⑨

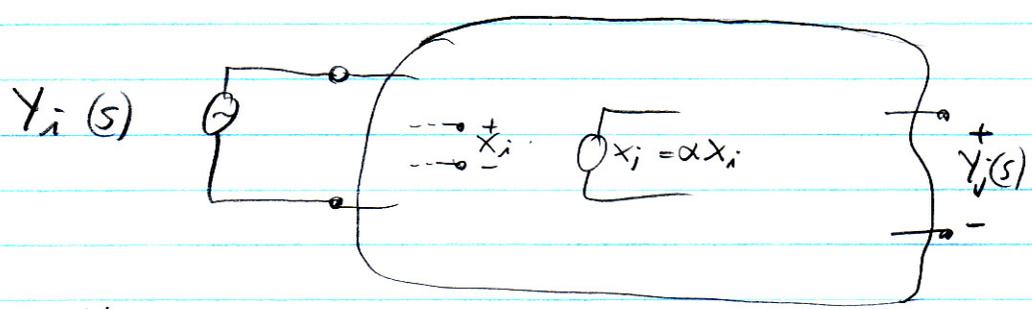

arbitrary SSM circuit with at least 1 controlled source

$x_i \neq Y_i$  required

any controlled source in circuit  $\equiv$  "ref. source"

$\left. \begin{matrix} x_i, x_j \\ Y_i, Y_j \end{matrix} \right\}$  voltages or currents

AGR:  $A(s) = A_\infty \cdot \frac{T}{1+T} + A_0 \cdot \frac{1}{1+T}$  ⑩  
 $\left( = \frac{Y_j(s)}{Y_i(s)} \right)$

where  $T \equiv -\alpha \cdot \frac{x_i}{x_x}$  where  $Y_i = 0$  and  $x_j$  replaced by an independent "test source",  $x_x$   
"loop gain"

$A_\infty(s) \equiv \frac{Y_j(s)}{Y_i(s)} \Big|_{\alpha \rightarrow \infty} \equiv$  "asymptotic gain"


$A_0(s) \equiv \frac{Y_j(s)}{Y_i(s)} \Big|_{\alpha=0} \equiv$  "direct transmission term"

6/6

Jan 31, 2008

Observations

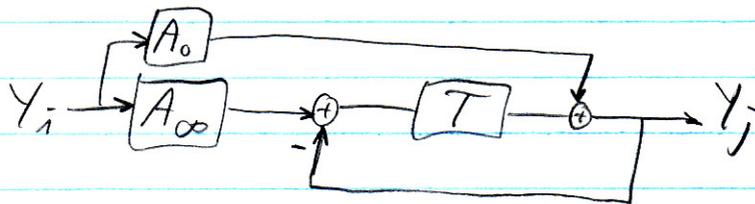MGF of (10)  $\Rightarrow$  can redraw (9) as



$\Rightarrow$  large  $T \Leftrightarrow$  feedback dominates behavior  $\Rightarrow A(s) \cong A_\infty(s)$

$A_0(s)$  arises from forward path through feedback network

"Reference source" in BIR & AGF:

See note of March 18, 2008

1/6


Avg.: 68 } Mid-term  
Med.: 70 }

### Feedback

Let  $x_i(s)$  = input signal (V or I)

$x_o(s)$  = output ——— " ———

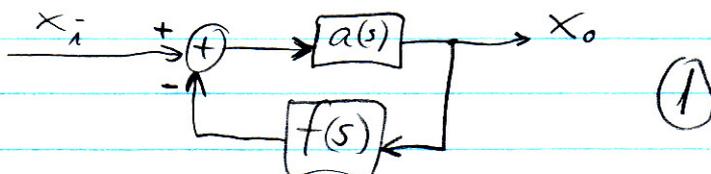
Then a circuit incorporates feedback if its B.D. can be reduced to:



MGF + ①  $\Rightarrow$

$$A(s) = \frac{a(s)}{1 + a(s)f(s)} \quad \text{②} \quad \text{where } A(s) \equiv \frac{x_o(s)}{x_i(s)}$$

### Ex 1 "Passive feedback"

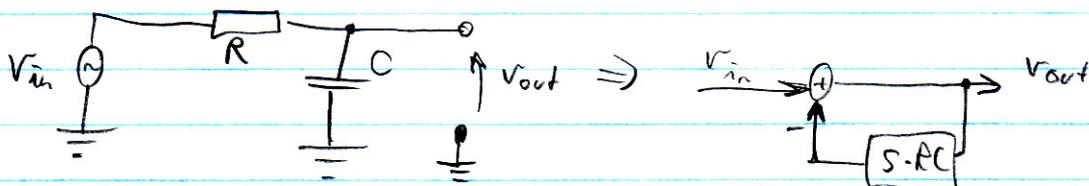


$$\therefore a(s) = 1$$

$$f(s) = sRC$$

(more generally, poles  $\Rightarrow$  feedback)


$$\frac{v_{out}}{v_{in}} = \frac{\frac{1}{sC}}{\frac{1}{sC} + R} = \frac{1}{1 + sRC} \Rightarrow v_{out} = v_{in} - v_{out} \cdot s \cdot RC$$

Ex 2 "Parasitic feedback"

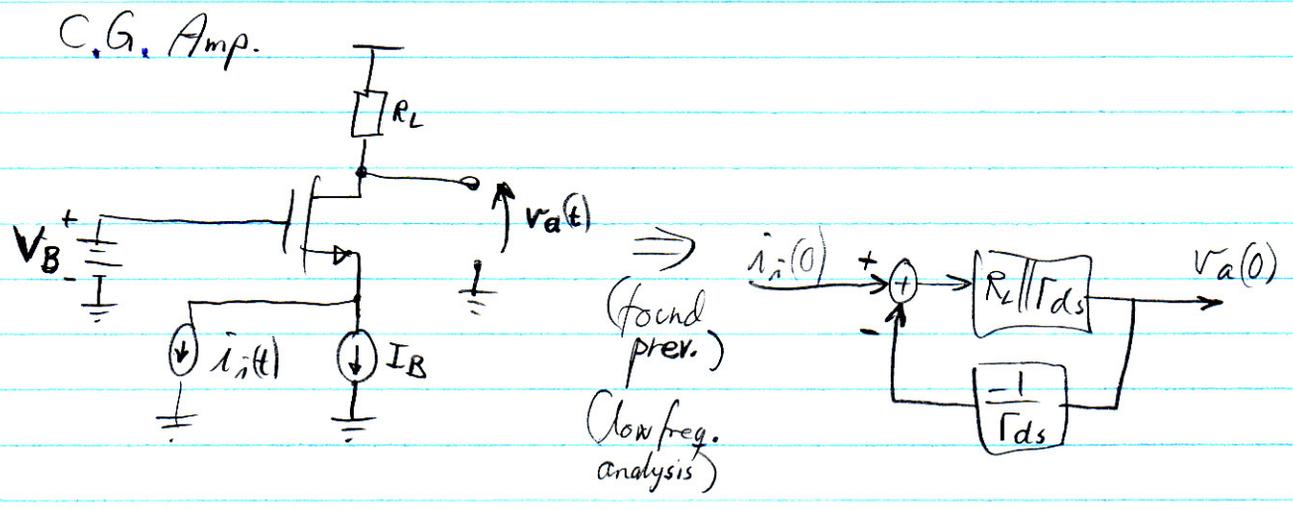


Note: In Ex1 feedback reduces the magnitude of  $X_o \equiv$  "neg. feedback"  
 In Ex2  $\sim$  increases  $\sim$   $\equiv$  "pos. feedback"

Ex 3 "Intentional active feedback"

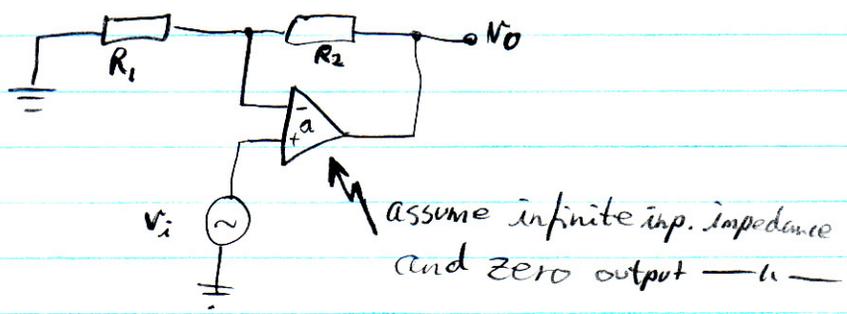
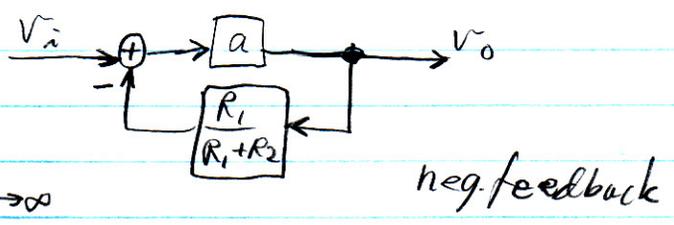
$$v_o = a \left[ v_i - \frac{R_1}{R_1 + R_2} v_o \right]$$



$$A = \frac{a}{1 + a \left( \frac{R_1}{R_1 + R_2} \right)} \rightarrow 1 + \frac{R_2}{R_1} \text{ as } a \rightarrow \infty$$

$\therefore$  large  $a \Rightarrow A$  depends only of the ratio of  $R$ 's

Easy in IC's

accurate in IC's

(3)


3/6

Feb. 12, 2008

Intentional active feedback  $\Rightarrow$  feedback around high gain amp  
 $\Rightarrow$  many benefits (e.g. ③)

Negative Intentional Active Feedback

Def.: In the following feedback system

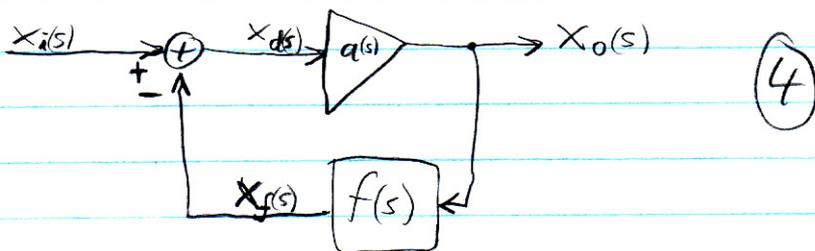

$a(s) \equiv$  "open loop gain",  $f(s) \equiv$  "feedback factor"

$T(s) \equiv a(s) \cdot f(s) \equiv$  "loop gain",  $A(s) \equiv$  "closed loop gain"  
(recall  $A(s) = \frac{a(s)}{1 + a(s) \cdot f(s)}$ )

Let  $A_{ideal} = \lim_{a \rightarrow \infty} A = \frac{1}{f}$  (e.g.  $A_{ideal} = 1 + \frac{R_2}{R_1}$  in Ex 3)

Asymptotic gain-relation: jan. 31

$A = A_{ideal} \cdot \frac{T}{1+T}$

$A = \frac{1}{f} \left( 1 - \frac{1}{1+a \cdot f} \right) = \frac{1}{f} \cdot \frac{af}{1+af} = \frac{a}{1+af}$

$\therefore$  ②  $\Rightarrow A = A_{ideal} \left( 1 - \frac{1}{1+T} \right)$  fractional deviation of A from  $A_{ideal}$

Also, MGF & ④  $\Rightarrow$

$X_d = \frac{1}{1+T} \cdot X_i \rightarrow 0$  as  $T \rightarrow \infty$  ( $a \rightarrow \infty$ )

$X_f = \frac{1}{1+1/T} \cdot X_i \rightarrow X_i$  as  $T \rightarrow \infty$  ( $a \rightarrow \infty$ )

$\therefore X_f$  "tracks"  $X_i$  with "error signal"  $X_d$  ( $d =$  difference)

- Benefits:
- (i) gain desensitivity
  - (ii) non-linear distortion reduction
  - (iii) in-loop noise suppression
  - (iv) broadbanding
  - (v) input/output impedance adjustment

- (Potential) Drawbacks
- (i)  $A < a$
  - (ii) excessive phase shift can cause instability

$$\left(\frac{U}{V}\right)' = \frac{U'V - UV'}{V^2}$$

(i) Gain desensitivity

$$\textcircled{2} \Rightarrow \frac{dA}{da} = \frac{1}{(1+af)^2} \Rightarrow \frac{\Delta A}{\Delta a} \approx \frac{1}{(1+af)^2} \quad \text{small } \Delta a$$

$\rightarrow = \frac{A}{a} \cdot \frac{1}{1+af}$

$$\therefore \frac{\Delta A}{A} \approx \left(\frac{1}{1+T}\right) \cdot \frac{\Delta a}{a} \Rightarrow \text{large variation in } a \Rightarrow \text{small } \frac{\Delta A}{A}$$

$\Rightarrow A$  is "stable" wRT variations in  $a$

$$\textcircled{2} \Rightarrow \frac{dA}{df} = -A^2$$

$$\therefore \frac{\Delta A}{\Delta f} \approx -A \cdot \frac{1}{f} \cdot \frac{T}{1+T}$$

$$\therefore \frac{\Delta A}{A} \approx -\left(\frac{T}{1+T}\right) \frac{\Delta f}{f} \Rightarrow A \text{ is not "stable" wRT variations}$$


$\approx 1$  for  $|T| \gg 1$

$\Rightarrow$  want high gain amplifier (not nec. well defined) and precise feedback factor.

$\frac{\Delta A}{A} = \frac{-T}{1+T} \cdot \frac{\Delta f}{f}$	$\frac{\Delta A}{A} = \frac{1}{1+T} \cdot \frac{\Delta a}{a}$
--	---

5/6

Feb 12, 2008

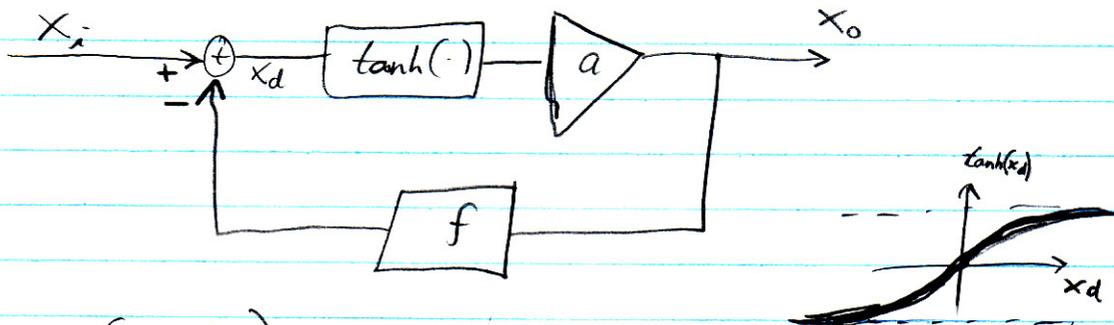(ii) Non-linear distortion reductionEx 4

$$x_o = a \cdot \tanh(x_i - f \cdot x_o)$$

$$\therefore \tanh^{-1}\left(\frac{x_o}{a}\right) = x_i - f \cdot x_o$$

$$\therefore \frac{x_o}{a} + \frac{x_o^3}{3a^3} + \frac{x_o^5}{5a^5} + \dots = x_i - f \cdot x_o$$

$$\therefore x_o + \frac{x_o^3}{3a^2} + \frac{x_o^5}{5a^4} + \dots = a(x_i - f \cdot x_o)$$

$\rightarrow 0$  as  $a \rightarrow \infty$

$$\therefore x_o \approx A \cdot x_i \text{ for large } a \text{ and } x_o \rightarrow \underbrace{\frac{1}{f}} \cdot x_i \text{ as } a \rightarrow \infty$$


no distortion

- Heuristics:
- 1) Follows from gain desensitivity  
(distortion prior to  $a \Leftrightarrow$  input dependent gain variation)
  - 2) Large  $a \Rightarrow$  small  $x_d \Rightarrow$  small portion of non-linear curve is traversed  $\Rightarrow \approx$  linear

6./6

Feb. 12, 2008

(iii) In-loop noise suppression

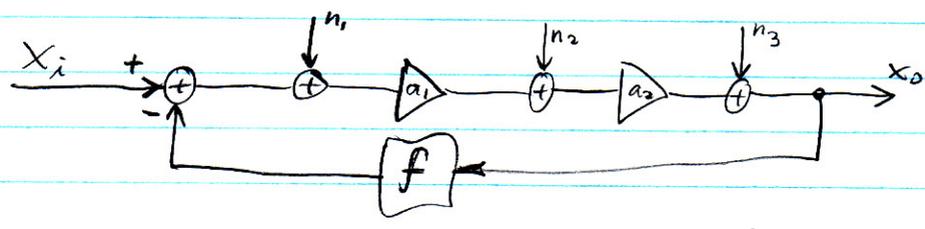

Open loop gain:  $a = a_1 a_2$


MGF  $\Rightarrow X_o = \frac{a}{1+af} \left( X_i + \frac{n_1}{a} + \frac{n_2}{a_1} + \frac{n_3}{a_1 a_2} \right)$

Annotations:  $\frac{n_1}{a}$  is circled and labeled "not suppressed";  $\frac{n_2}{a_1}$  is circled and labeled "Somewhat Suppressed";  $\frac{n_3}{a_1 a_2}$  is circled and labeled "most suppressed".

(iv) Broadbanding

Ex 5 suppose  $a \approx \frac{a_0}{1-j\omega/\omega_{p0}}$  (dom. pole approx.)

$F \approx$  indep. of  $\omega$

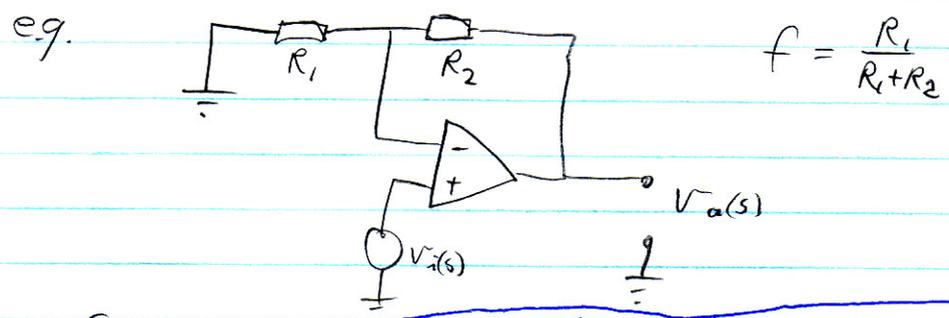


Then (2)  $\Rightarrow A = \frac{a}{1+af} = \frac{1}{f} \cdot \frac{af}{1+af} = \frac{1}{f} \cdot \frac{1}{1 + \frac{1}{f} \cdot \frac{1}{a}} = A_{ideal} \cdot \frac{1}{1 + 1/f}$

$A(j\omega) = \left(1 + \frac{R_2}{R_1}\right) \frac{1}{1 + \left(1 + \frac{R_2}{R_1}\right) (1-j\omega/\omega_{p0})/a_0}$

algebra  $\Rightarrow A(j\omega) = \frac{A_0}{1-j\omega/\omega_{pA}}$


where  $A_0 = \left(1 + \frac{R_2}{R_1}\right) \frac{1}{1 + \left(1 + \frac{R_2}{R_1}\right)/a_0}$  (5)

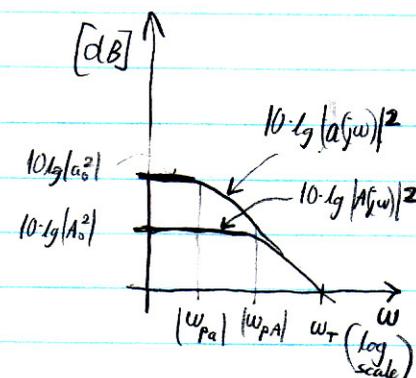and  $\omega_{pA} = \omega_{p0} \left(1 + a_0 \cdot \frac{R_1}{R_1 + R_2}\right)$  (6)



Negative intentional active feedback (cont. from pp. 3-6 last time)

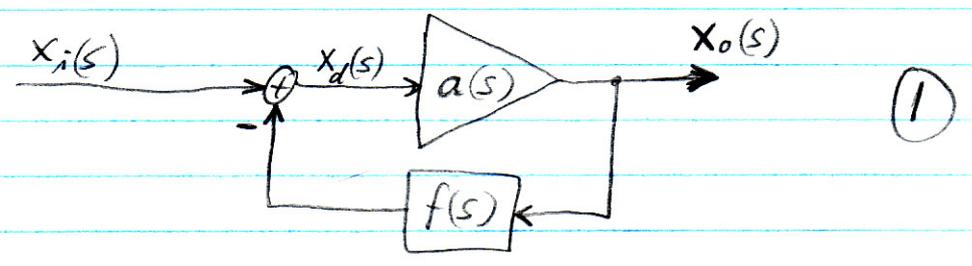Recall: Can always write the block diagram of a circuit with feedback as:



$a(s) \equiv$  "open loop gain"  
 $f(s) \equiv$  "feedback factor"  
 $T(s) \equiv a(s) \cdot f(s) \equiv$  loop gain

← (i M.G.F.:  $T = a \cdot f$  unlike definisjoner!)

$A(s) = \frac{x_o(s)}{x_i(s)} \equiv$  "closed loop gain"

M.G.F  $\Rightarrow A(s) = \frac{a(s)}{1 + a(s) \cdot f(s)}$  (2)

Broadbanding (cont.)

Suppose:  $a(j\omega) = \underbrace{a_0}_{\text{DC-gain}} \cdot \frac{1}{1 - j\omega/\omega_{pa}}$  (3)

↳ dominant pole approx.

$f(j\omega) = \text{const.}$

(2), (3)  $\Rightarrow A(j\omega) = A_0 \cdot \frac{1}{1 - j\omega/\omega_{pa}}$  where

$A_0 = \frac{a_0}{1 + a_0 \cdot f}$  (DC closed loop gain)

&  $\omega_{pa} = (1 + a_0 \cdot f) \cdot \omega_{pa}$

(4)

2/6

Feb. 14, 2008

$|A_o \cdot \omega_{pa}| \equiv$  "closed loop gain bandwidth product",  $GBW_{\text{closed loop}}$

$|a_o \cdot \omega_{pa}| \equiv$  "open loop gain bandwidth product",  $GBW_{\text{open loop}}$

④  $\Rightarrow A_o \cdot \omega_{pa} = a_o \cdot \omega_{pa}$

$\therefore GBW_{\text{open loop}} = GBW_{\text{closed loop}}$  in this case.

$\therefore$  Increasing  $f$  (between 0 and 1) decreases  $A_o$ , but increases the 3dB BW.

"Unity Gain Frequency"

$\equiv \omega_t$  such that  $a(j\omega_t) = 1$ ,  $\omega_t \in \mathbb{R}$


$\therefore$  ③  $\Rightarrow \left| a_o \cdot \frac{1}{1 - j\omega_t/\omega_{pa}} \right| = 1$

$\Rightarrow (a_o^2 - 1) \cdot \omega_{pa}^2 = \omega_t^2$

$\Rightarrow \omega_t \approx a_o \cdot |\omega_{pa}|$  ( $a_o \gg 1$ )

$\therefore GBW = \omega_t$  in this case (not always in other cases)

Ex 1 (from last time)

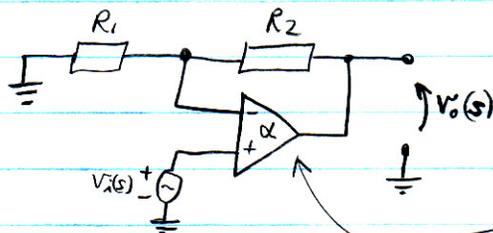


Assume  $Z_{in} = \infty$   
 $Z_{out} = 0$

$\Rightarrow$  ① if  $a = \alpha$ ,  $f = \frac{R_1}{R_1 + R_2}$

3/6

Feb 14, 2008

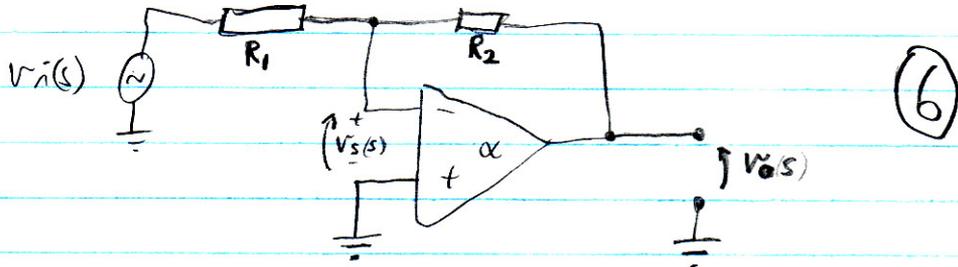Ex2 (Same except different input location)




$$v_o(s) = \alpha(s) \cdot [-v_s(s)]$$

$$\therefore v_s(s) = v_i(s) - R_1 \cdot \left[ \frac{v_i(s) - v_o(s)}{R_1 + R_2} \right]$$

$$\therefore -v_s(s) = -v_i(s) \left[ 1 - \frac{R_1}{R_1 + R_2} \right] - v_o(s) \cdot \left[ \frac{R_1}{R_1 + R_2} \right]$$

$$\rightarrow = \frac{R_2}{R_1 + R_2}$$

$\therefore$  BD of (6) is:

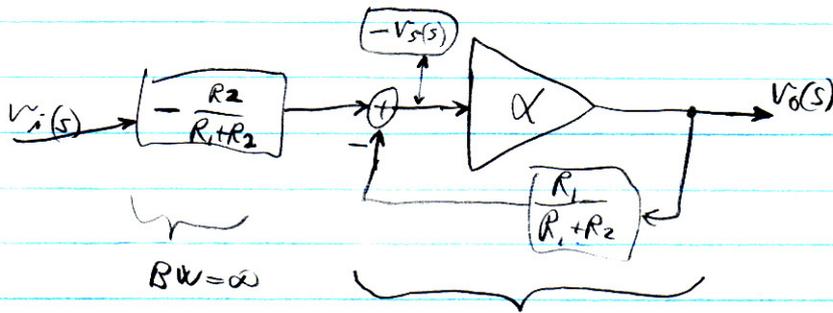

BW =  $\infty$

$$\equiv (1) \text{ with } a = \alpha \text{ \& } f = \frac{R_1}{R_1 + R_2}$$

(Same as Ex. 1.)


$\Rightarrow$  BW = same as Ex 1

But GBW of (6) less than that of Ex 1 by  $\frac{R_2}{R_1 + R_2}$

$$\text{Also, } \underset{\text{closed loop}}{\text{GBW}} = \frac{R_2}{R_2 + R_1} \cdot \omega_t = \frac{R_2}{R_1 + R_2} \cdot \underbrace{a_0}_{\omega_{pa}}$$

GBW<sub>open loop</sub>


Feb 14, 2008

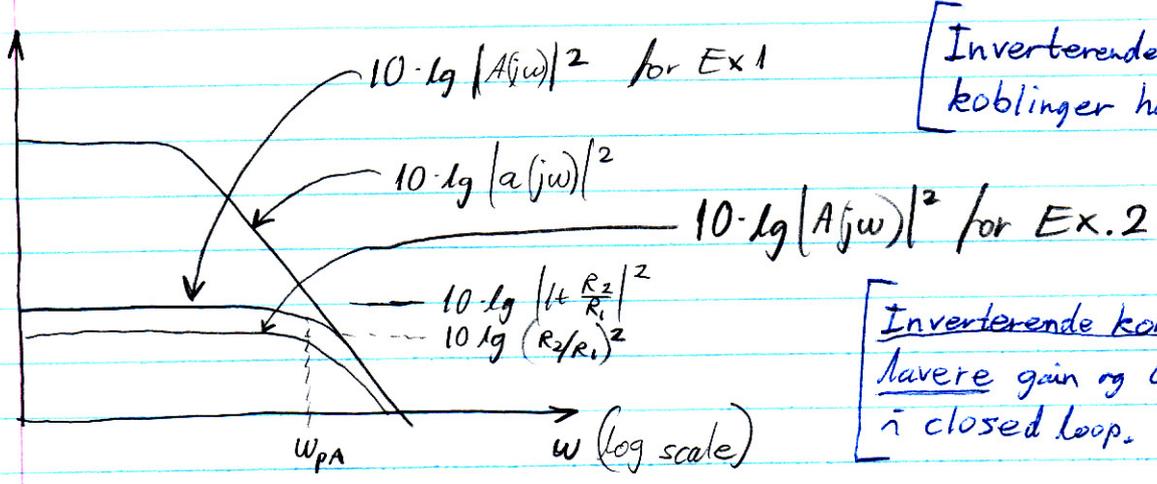


Inverterende og ikke-inv. koblinger har samme B.W.

Inverterende kobling gir lavere gain og GBW produkt i closed loop.

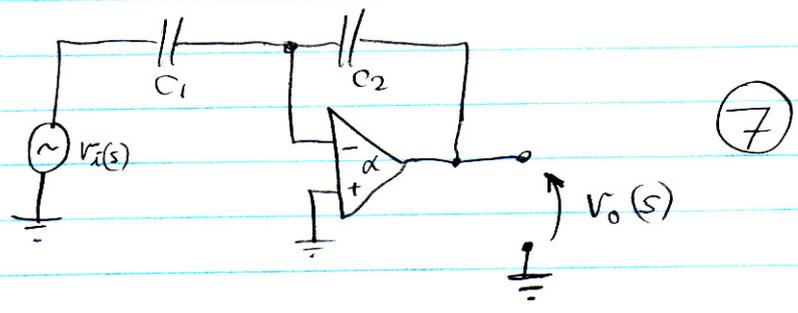Ex 3 Same as Ex2 with R's replaced by C's (important later in switched cap. circuits)



Exercise show BD of ⑦ is

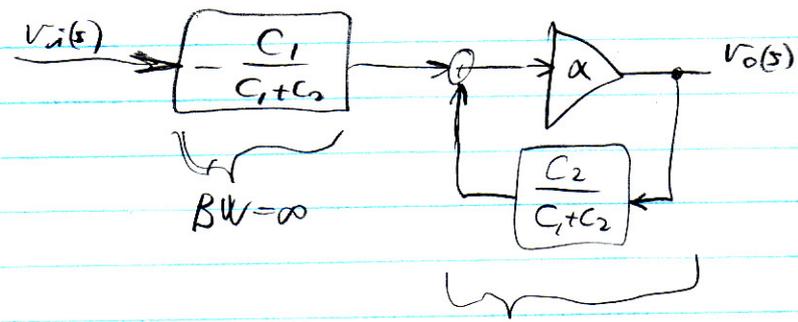


≡ ① with  $a = \alpha$   
 $f = \frac{C_2}{C_1 + C_2} \Rightarrow f = \text{const} (\in \mathbb{R})$

∴ (4) ⇒  $BW = \left(1 + a_0 \frac{C_2}{C_2 + C_1}\right) \cdot |w_{pa}|$   
 Also  $GBW_{closed\ loop} = \frac{C_1}{C_1 + C_2} \cdot w_t = \frac{C_1}{C_1 + C_2} \cdot a_0 \cdot |w_{pa}|$

(V) Impedance transformation


Ex. 4 Wilson current mirror

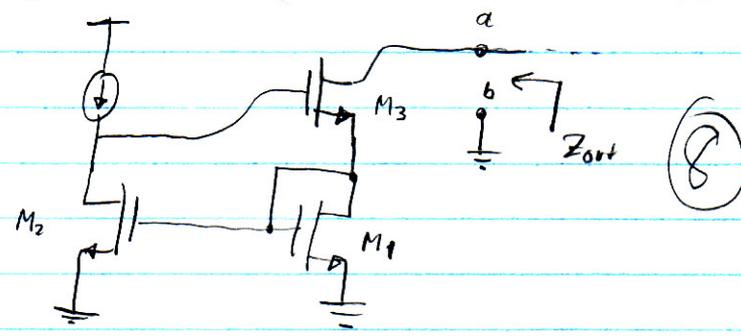

previously found:

$Z_{out} \approx r_{ds3} \cdot g_{m2} \cdot r_{ds2}$   
 (low freq. analysis, neglecting body effect)

Now consider

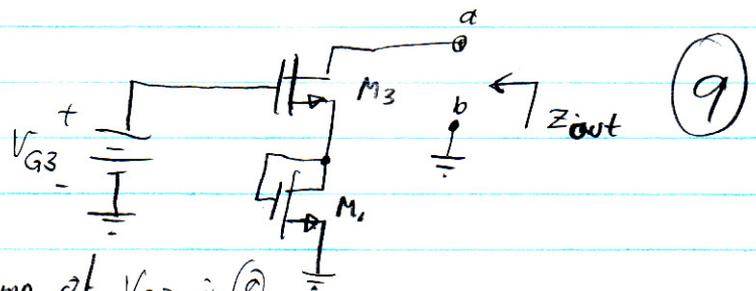

Where  $V_{G3} = DC\ comp.\ of\ V_{G3}\ in\ (8)$   
 Can show:  $Z_{out}\ of\ (9) \approx r_{ds3} (2 + \frac{1}{g_{m1}} \cdot r_{ds3})$   
 $\approx 2 \cdot r_{ds3}$

Note: (9) is equiv. to (8) with feedback disabled


∴ feedback increases  $Z_{out}$  by  $(\frac{1}{2} g_{m2} \cdot r_{ds2})$  factor

6/6

Feb. 14, 2008


Heuristics:

(8)  $\equiv$

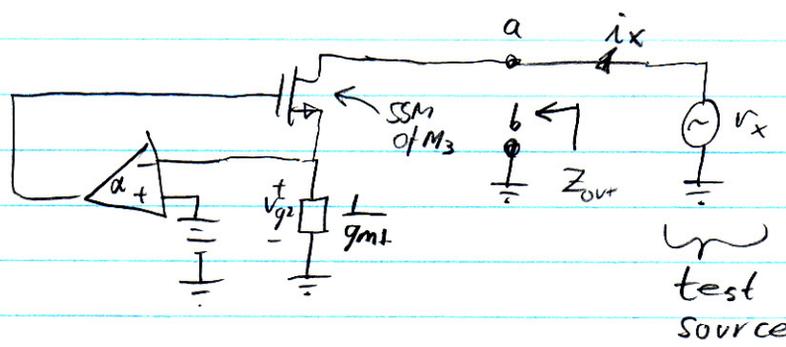


If  $v_x$  increases,  $i_x$  increases  $\Rightarrow v_{g2}$  increases  
 $\Rightarrow v_{g3}$  decreases  
 $\Rightarrow$  feedback acts to reduce  $i_x$

Ex 5 Voltage source

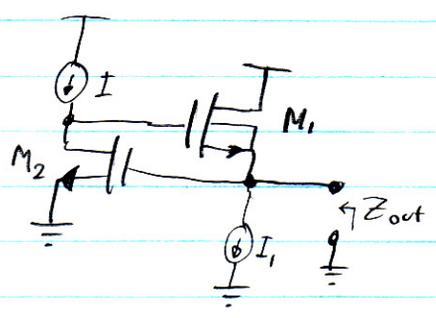

(10)

Low freq SSM:

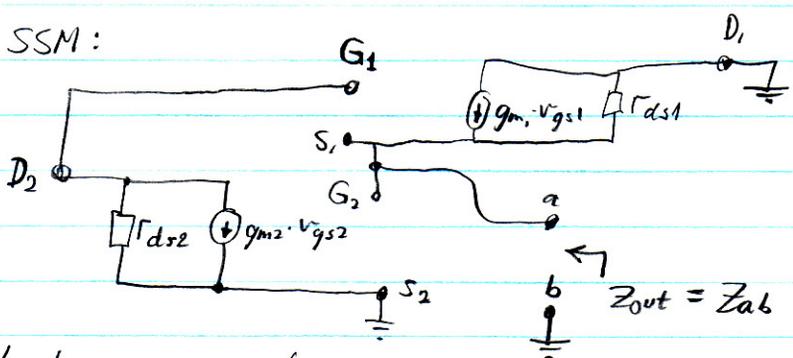

(11)

BIR: Let  $g_{m1} \cdot v_{g1} \equiv \text{ref. source}$   
 $\therefore v_{gs1} = X_i, \alpha = g_{m1}, Z_{ab}^0 = r_{ds1}$

Exercise: Show  $T_{sc} = 0, T_{oc} = g_{m1} \cdot g_{m2} \cdot r_{ds1} \cdot r_{ds2}$   
 $\therefore Z_{ab} = r_{ds1} \cdot \frac{1}{1 + g_{m1} g_{m2} \cdot r_{ds1} \cdot r_{ds2}} \approx \frac{1}{g_{m1} g_{m2} r_{ds2}} = \text{small!}$

Feedback reduced output imp. by a factor of  $g_{m2} \cdot r_{ds2}$

Stability

Let A(s) = (a0 + a1\*s + a2\*s^2 + ... + am\*s^m) / (b0 + b1\*s + b2\*s^2 + ... + bn\*s^n) (1)

If A(0) != 0 or inf, can write (1) as


A(s) = A0 \* (1 + a1\*s + ... + am\*s^m) / (1 + b1\*s + b2\*s^2 + ... + bn\*s^n) (2)

(other choices of T(s) are possible if we allow a(s) has poles)

...then:

A(s) = a(s) / (1 + a(s)\*f(s)) where a(s)\*f(s) = T(s) and a(s) = A0(1 + a1\*s + ... + am\*s^m)

(2) can be impl. as:

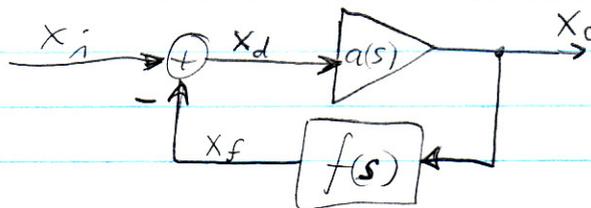

Def: A system is stable if (and only if) it satisfies the following property:

For each bounded input signal, Xi(t), the output signal, Xo(t), must also be bounded

(X(t) is bounded means exists B in R st. |X(t)| < B for all t)

Stability is equivalent to bounded input, bounded output, stability

BIBO

Such that

April 18, 2007

Bounded input: R(s) = AR(s) / BR(s)



... hvor BR(s) sine røtter har negativ realdel eller, om de er på den vertikale akse, multiplisitet maks 1 (ellers får vi terms med rampe-form)

ECE 171A

=> Stabilt sys. må ha neg. realdel på polene for å garantere bounded output.

2/4

Feb. 19, 2008

Claim 1 Let  $h(t)$  be the impulse response of an LTI system and let  $H(s)$  be its transfer function. Then the system is stable iff either of the following hold:

iff  $\equiv$   
"if and only if"

- i) All poles of  $H(s)$  are in the LHP (not including imag. axis) (ie. if  $s_0$  is a pole then  $\text{Re}\{s_0\} < 0$ )
- ii)  $\int_{-\infty}^{\infty} h(t) dt < \infty$

proof Exercise (review material)

Claim 2 If an LTI has a transfer function given by (2), then it is stable iff

$$T(s_0) = -1 \Rightarrow \text{Re}\{s_0\} < 0$$

proof = Exercise.

Def. "Nyquist plot"  $\equiv$  plot of  $\text{Im}\{T(j\omega)\}$  vs.  $\text{Re}\{T(j\omega)\}$  as  $\omega$  increases from  $-\infty$  to  $\infty$

Nyquist Criterion:



Provided there are no RHP pole-zero cancellations in  $T(s) = a(s) \cdot f(s)$  an LTI system is stable iff the net no. of CCW encirclements of the point  $(-1, 0)$  by the Nyquist plot equals the no. of RHP poles in  $T(s)$

$\therefore$  Nyquist crit.  $\Rightarrow$  stability test  $\leftrightarrow$  {not so useful these days (because of computers)}  
will soon see: Nyquist crit.  $\Rightarrow$  insight  $\Rightarrow$  concepts of phase & gain margin } very useful


3/4

Feb. 19, 2008

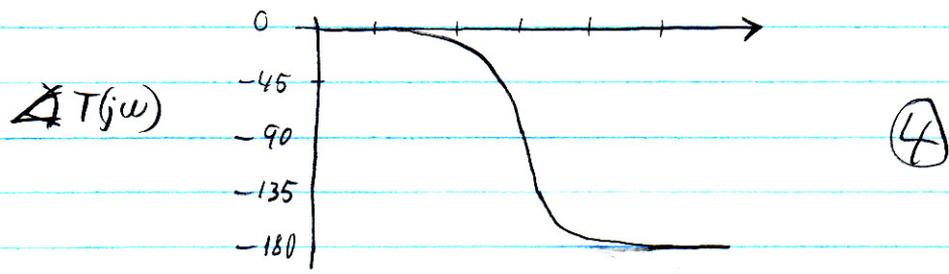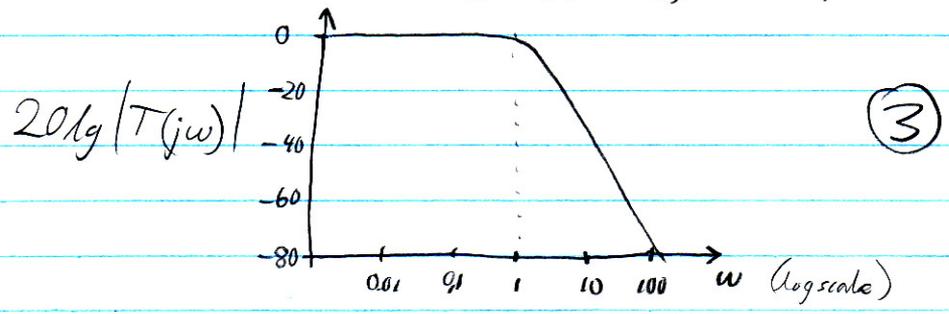Ex 1 Suppose  $T(s) = \frac{1}{(1+s)(1+s/2)}$  poles: -1, -2



③, ④ ⇒ Nyq. Plot

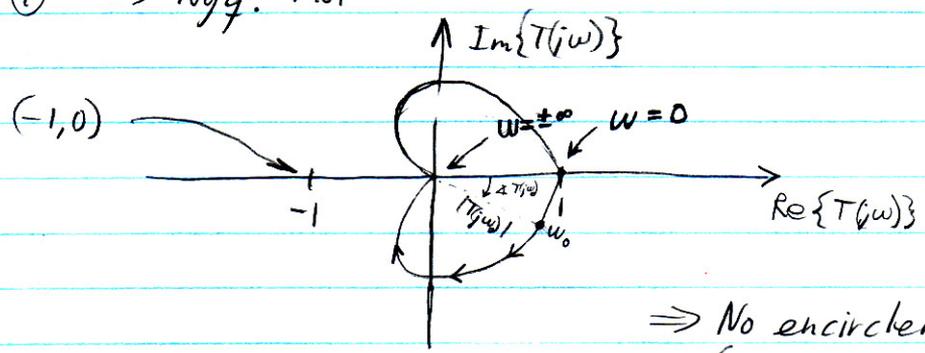

⇒ No encirclements of (-1, 0)  
(T(s) has no RHP poles by inspection)

Nyq. crit ⇒ system with t.f.  $A(s) = \frac{a(s)}{1+T(s)}$  is stable (provided there are no pole-zero cancellations in  $a(s)/f(s)$ ) (why?)




4/4

Feb. 19, 2008

Ex 2 Suppose  $a(s) = \frac{a_0}{(1-s/p_1)(1-s/p_2)(1-s/p_3)}$  and  $f = \text{const.}$

$$\therefore T(j\omega) = f \cdot a(j\omega)$$

For  $|p_1| \approx 10 \cdot |p_2| \approx 100 |p_3|$  and  $\text{Re}\{p_i\} < 0, i=1,2,3$

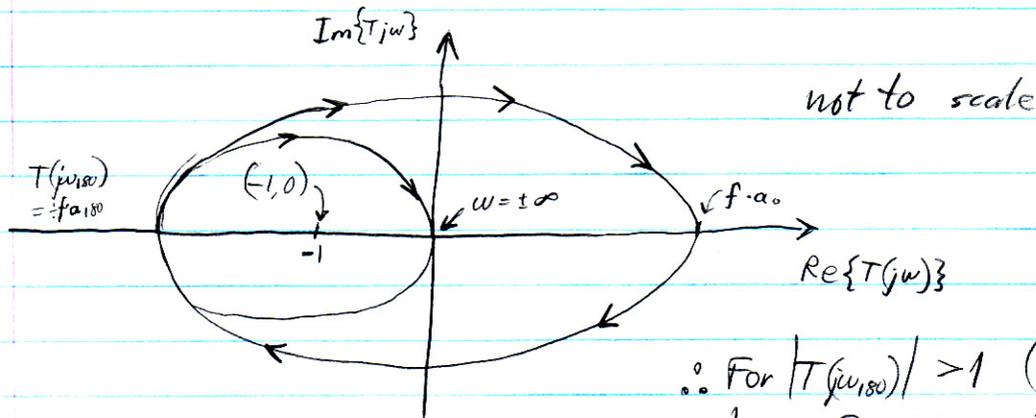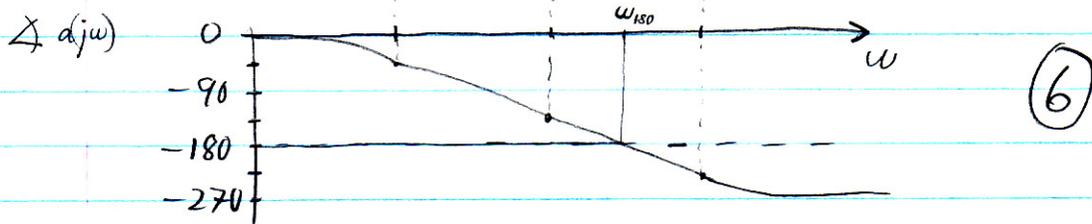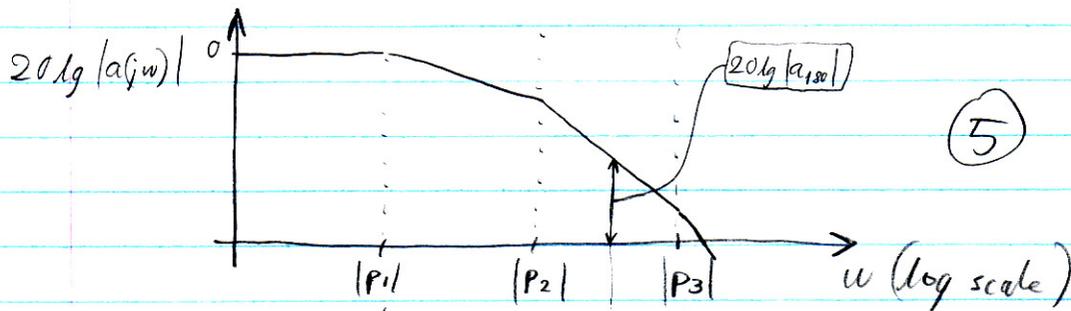


$\therefore$  For  $|T(j\omega_{180})| > 1$  (the case shown) have 2 c.w. encirclements, but  $T(s)$  has no RHP poles

$\therefore$  Nyquist crit  $\Rightarrow$  unstable if  $|T(j\omega_{180})| > 1$   
 $\Rightarrow$  stable if  $|T(j\omega_{180})| < 1$

Nyquist Criterion (cont.)

Let  $A(s) = \frac{a(s)}{1 + a(s)f(s)}$

$T(s) = a(s)f(s)$

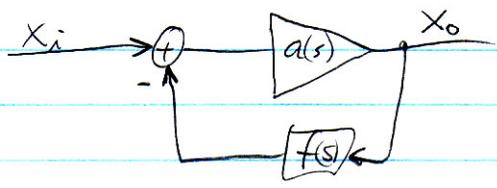


Assume: No zero of  $f(s)$  is a pole of  $a(s)$   
Then  $T(s_0) = -1 \iff s_0$  is a pole of  $A(s)$

Ex. 1 Suppose  $T(j\omega_1) = -1$  for some  $\omega_1 \in \mathbb{R}$   
 $\implies A(s)$  has pole on imag. axis  $\implies$  oscillation  
 $\implies$  unstable


s.t. =  
"such that"

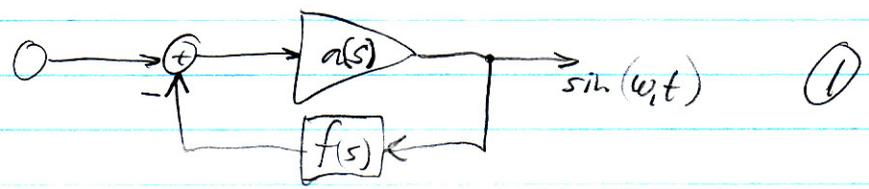$\therefore$  can choose initial cond. s.t.



occurs.

This happens because (1) is equiv. to

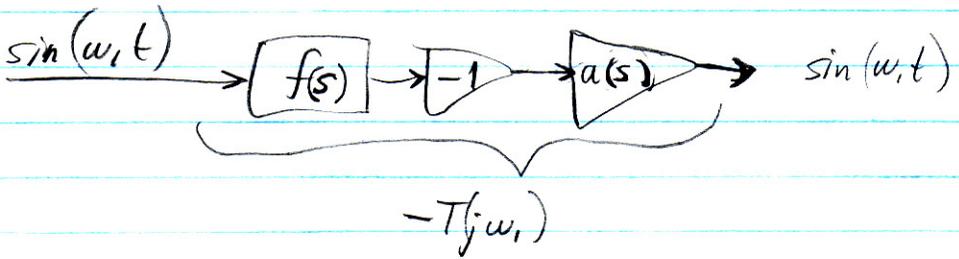

$T(j\omega_1) = -1 \implies |T(j\omega_1)| = 1$   
and  
 $\angle T(j\omega_1) = \pi$

Ex 2 Suppose  $T(s_0) = -1$  for  $s_0 = \sigma_0 + j\omega$ ,  $\sigma_0 \geq 0$   
 $\Rightarrow$  have ① with  $\sin(\omega t)$  replaced by  $\underbrace{e^{\sigma_0 t}}_{L \rightarrow \infty \text{ as } t \rightarrow \infty} \cdot e^{j\omega t}$   
 $\Rightarrow$  0 input  $\Rightarrow$  unbounded output

Ex 3 Suppose  $A(s)$  is stable, but for some  $\omega_1 \in \mathbb{R}$ ,  
 slang

$|T(j\omega_1)| = 1 - |\epsilon|$  where  $|\epsilon| = \text{small } \#$   
 and  $\angle T(j\omega_1) = \pi$

Then have ringing for any input step  
 e.g:  $x_i = \text{step}$       $x_o = \text{ringing}$

In many systems, ringing is undesirable because it slows the settling time.

$\Rightarrow$  We need to design with "gain margin" s.t.  $|T(j\omega)| \neq 1$   
 when  $\angle T(j\omega) = \pi$  with sufficient "margin" to minimize ringing.

Nyg. crit. = method of evaluating "marginal stability"  
 using simulated or calculated freq. response plots

Recall Nyq. Plot  $\equiv$  Plot of  $\text{Im}\{T(j\omega)\}$  vs.  $\text{Re}\{T(j\omega)\}$  as  $\omega$   
 increases from  $-\infty$  to  $\infty$

Nyg. Crit  $\equiv$  An LTI system is stable iff the net  
 number of CCW encirclements of  $(-1, 0)$   
 by the Nyq. plot equals the number of  
 RHP poles of  $T(s)$ .

3/5


Feb. 21, 2008

E.G.

The Nyquist crit. is based on The Encirclement Property (E.P).


E.P.: Let  $R(s)$  be any rational fn. The plot of  $R(s)$  along a closed CW path,  $C$ , in the complex  $s$ -plane encircles the point  $s=0$  in a clockwise direction a net no. of times equal to the no. of zeros  $\div$  no. of poles within the contour.

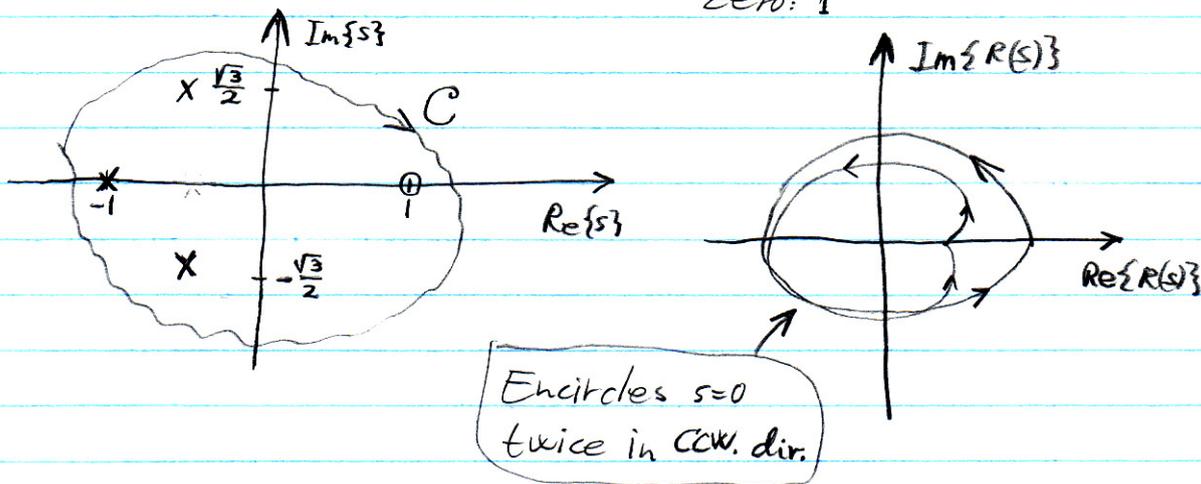Ex. 4 Suppose  $R(s) = \frac{s-1}{(s+1)(s^2+s+1)}$  poles:  $-1, -\frac{1}{2} \pm \frac{\sqrt{3}}{2}j$   
zero: 1



Why does this work?

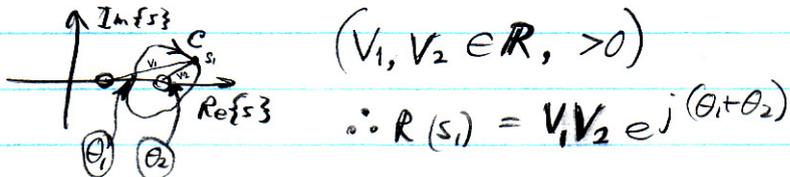Ex. 5 Suppose  $R(s)$  has only 2 (RHP) zeros and no poles



As  $C$  is traversed:  $\left\{ \begin{array}{l} \text{net change in } \theta_1 \text{ is } 0 \\ \text{net change in } \theta_2 \text{ is } -2\pi \end{array} \right.$

$\therefore \angle R(s) = \theta_1 + \theta_2$

$\therefore$  As  $C$  is traversed, the net change in  $\angle R(s)$  is  $-2\pi$   
 $\Rightarrow R(s)|_{s \in C}$  circles origin once (in cw dir.)  
( $s=0$ )

Feb. 21, 2008

E.G.

Proof of Nyq. crit.


Restrictions of proof:

- 1) Rational  $T(s)$
- 2)  $|T(j\omega)| < \infty \quad \forall \omega \in \mathbb{R}$
- 3)  $T(s)$  has  $(\# \text{poles}) \geq (\# \text{of zeros})$

(But Nyq. crit also applies without restrictions 1) & 3) and can be modified to handle poles on the imag axis.)

Consider contour  $C$  as follows:

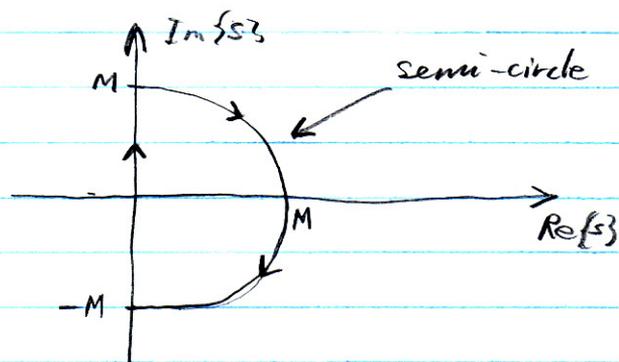As  $M \rightarrow \infty$ ,  $C$  contains all RHP poles of  $A(s)$



$$1), 3) \Rightarrow T(s) = \frac{c_0 + c_1 s + \dots + c_{N_1} s^{N_1}}{d_0 + d_1 s + \dots + d_{N_2} s^{N_2}}$$


Where  $N_1 \leq N_2$

$$\therefore \lim_{|s| \rightarrow \infty} T(s) = \begin{cases} \frac{c_{N_1}}{d_{N_1}} & \text{if } N_1 = N_2 \\ 0 & \text{if } N_1 < N_2 \end{cases} = \text{const} \in \mathbb{R}$$

$\Rightarrow$  The plot of  $T(s)$  along the semi-circular part of  $C$  approaches a single point on real axis as  $M \rightarrow \infty$

$\Rightarrow$  Nyq. plot is equiv. to plot of  $T(s)$  along  $C$  as  $M \rightarrow \infty$

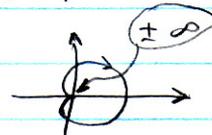e.g., recall: Nyq. plot of  $T(s) = \frac{1}{(1+s)(1+s/2)}$  is



$\Rightarrow$  Can apply encirclement property to Nyq. plot

Let  $R(s) = 1 + T(s)$ . Then plot of  $R(s)$  along  $C$  encircles the origin exactly as many times as that of  $T(s)$  encircles  $(-1, 0)$ .

$\therefore$  E.P.  $\Rightarrow$  net no. of cw. encirclements of  $(-1, 0)$   
 $=$  # of zeros of  $(1+T(s))$  minus # of poles of  $1+T(s)$  inside  $C$ .

5/5

Feb. 21, 2008 E.G.

But:

- zeros of  $1+T(s) \equiv$  poles of  $A(s)$
- poles of  $1+T(s) \equiv$  poles of  $T(s)$
- inside  $C =$  all RHP as  $M \rightarrow \infty$

$\Rightarrow$  Nyq. crit.

□


Important special case of Nyquist criterion:

Suppose  $\nexists T(0) = 0$  and  $T(s)$  has no RHP poles

If  $\nexists |T(j\omega)| = 1$  for only one pos. value,  $\omega = \omega_\pi$ ,

Then  $A(s)$  is stable iff  $|T(j\omega_\pi)| < 1$

eg. picture =

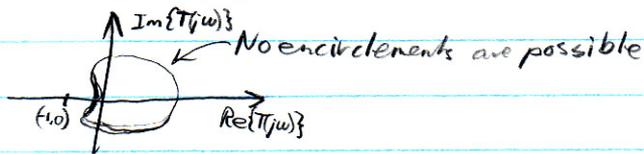

Note:

In general,  $|T(j\omega_\pi)| > 1 \Rightarrow$  instability (!)

1/7


ECE 264A

Feb. 26, 2008

E.G.

OH:  
1~2<sup>30</sup> this  
Friday (2/29)

### Gain & Phase Margin

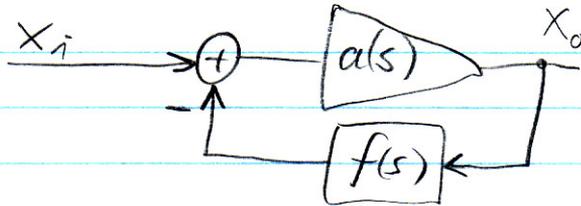

$$A(s) = \frac{a(s)}{1 + \frac{a(s) \cdot f(s)}{T(s)}}$$

Assume no pole of  $a(s)$  is a zero of  $f(s)$ .

Nyg. crit  $\Rightarrow$  2 special cases:

i) Suppose  $\nabla T(0) = 0$ ,  $T(s)$  has no RHP poles and  $|\nabla T(j\omega)| = \pi$  has no more than one positive solution,  $\omega = \omega_\pi$  } ①  
 Then  $A(s)$  is stable iff  $|T(j\omega_\pi)| < 1$

ii) Suppose  $\nabla T(0) = 0$ ,  $|T(0)| > 1$ ,  $T(s)$  has no RHP poles, and  $|T(j\omega)| = 1$  has no more than one positive solution,  $\omega = \omega_u$  } ②  
 Then  $A(s)$  is stable iff  $-\pi < \nabla T(j\omega_u) < \pi$


i)  $\Rightarrow$  Basis of "Gain margin" (GM) definition (soon)  
 ii)  $\Rightarrow$  Basis of "Phase margin" (PM) definition (soon)

2/7

Feb 26, 2008

E.G.
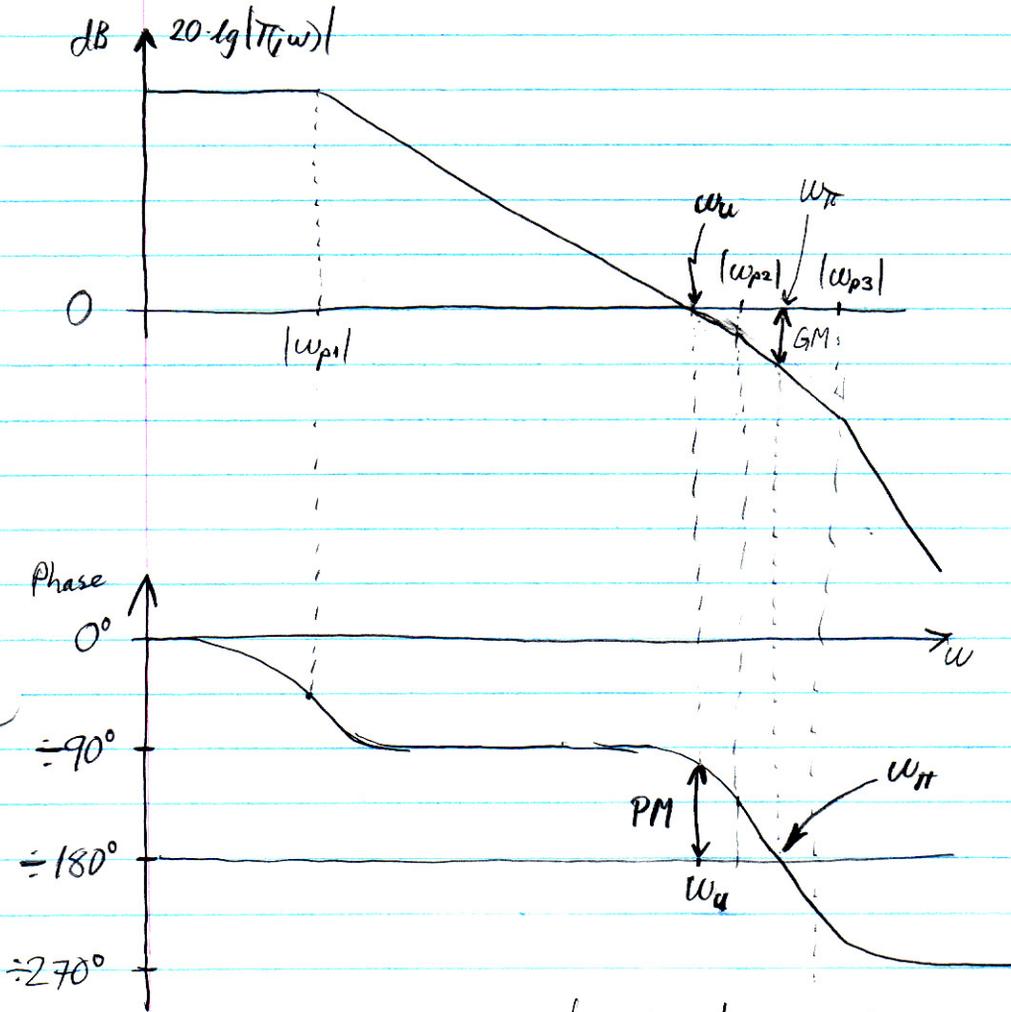
# Def. of PM & GM (via 3-pole T(s) example)



ie.  $GM \equiv 20 \lg \left| \frac{1}{T(j\omega_u)} \right|$  (pos. as shown)

$PM \equiv 180^\circ - |\angle T(j\omega_u)|$  (pos. as shown)

3/7


Feb. 26, 2008 E.G.

∴ ①,  $GM > 0 \Leftrightarrow$  stable (closed loop)


②,  $PM > 0 \Leftrightarrow$  stable (closed loop)

Also, larger  $GM$  ( $PM$ )  $\Leftrightarrow$  better marginal stability  
(i.e. step response has less ringing; can tolerate larger component errors without instab.)

Consider:

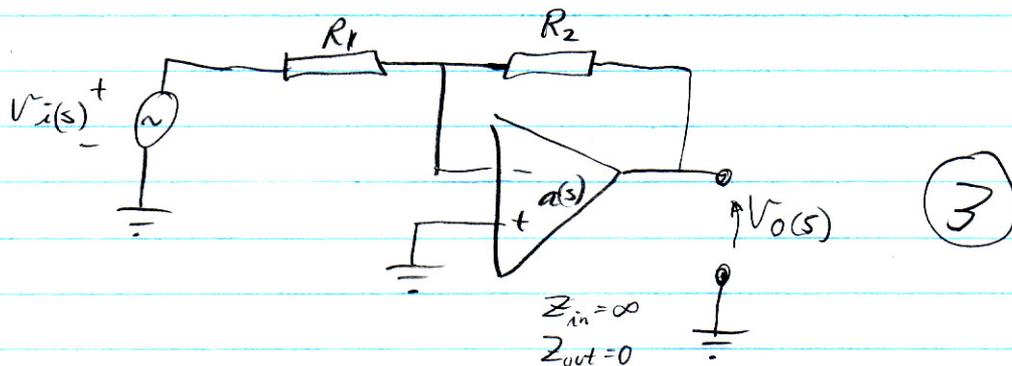

Previously found:

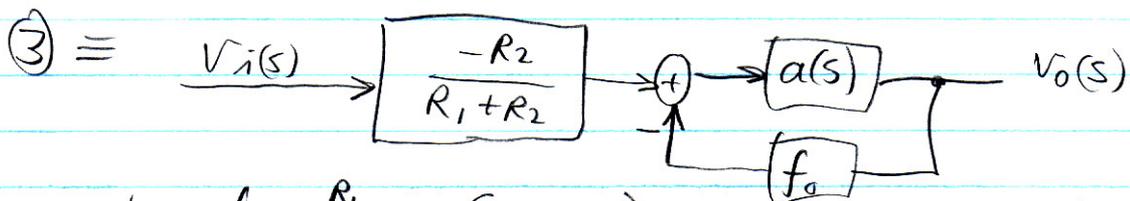


where  $f_0 = \frac{R_1}{R_1 + R_2}$  ( $0 < f_0 < 1$ )

4/7

Feb 26, 2008 E.G.

Ex 1 (3) with  $a(s) = \frac{a_0}{1-s/\omega_{pa}}$ ,  $\omega_{pa} < 0$  ( $\in \mathbb{R}$ )  
 $a_0 > 0$  ( $\in \mathbb{R}$ )
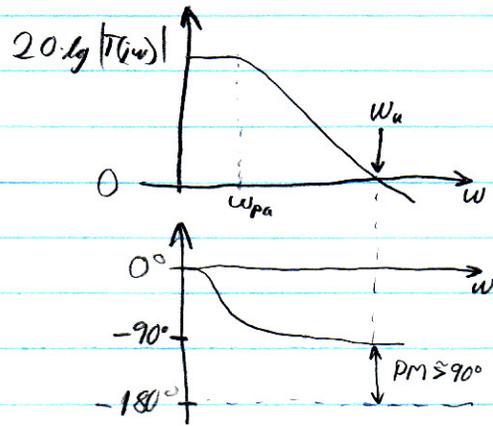
$$\therefore T(j\omega) = \frac{a_0 \cdot f_0}{1-j\omega/\omega_{pa}}$$



Depending on  $a_0 f_0$

$$90^\circ < PM < 180^\circ$$


$$\text{e.g. } \lim_{a_0 f_0 \rightarrow 1} PM = 180^\circ$$

$$\lim_{a_0 f_0 \rightarrow \infty} PM = 90^\circ$$

Feb. 14


Recall:  $A(s) \equiv \frac{V_o(s)}{V_i(s)} = A_0 \cdot \frac{1}{1-s/\omega_{pa}}$  where  $A_0 \in \mathbb{R}$   
 $\omega_{pa} = (1+a_0 f_0) \cdot \omega_{pa}$

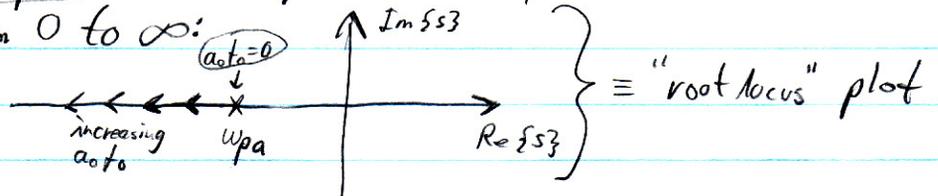Plot of  $\omega_{pa}$  position in  $s$ -plane as  $a_0 f_0$  increases from 0 to  $\infty$ :



$\therefore$  as expected, it's stable for any choice of  $a_0 f_0 > 0$

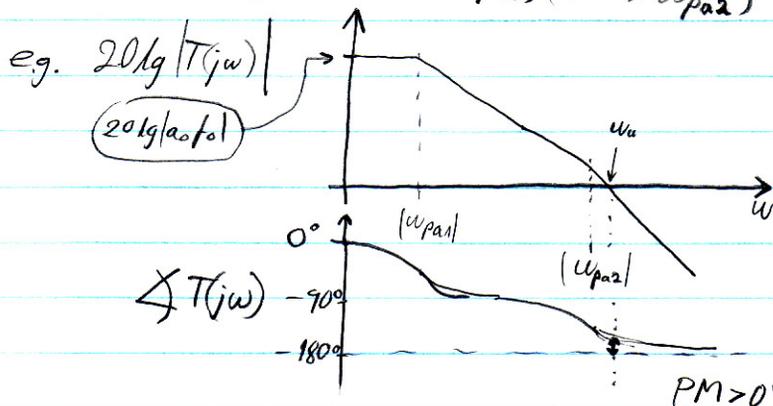Ex 2 (3) with  $a(s) = \frac{a_0}{(1-s/\omega_{pa1})(1-s/\omega_{pa2})}$ ,  $\omega_{pa1} < 0$  ( $\in \mathbb{R}$ )  $i=1,2$   
 $a_0 > 0$  ( $\in \mathbb{R}$ )




$\Rightarrow 0^\circ < PM < 180^\circ$

$\Rightarrow$  always stable  
(at least barely)

5/7

Feb. 26, 2008 E.G.

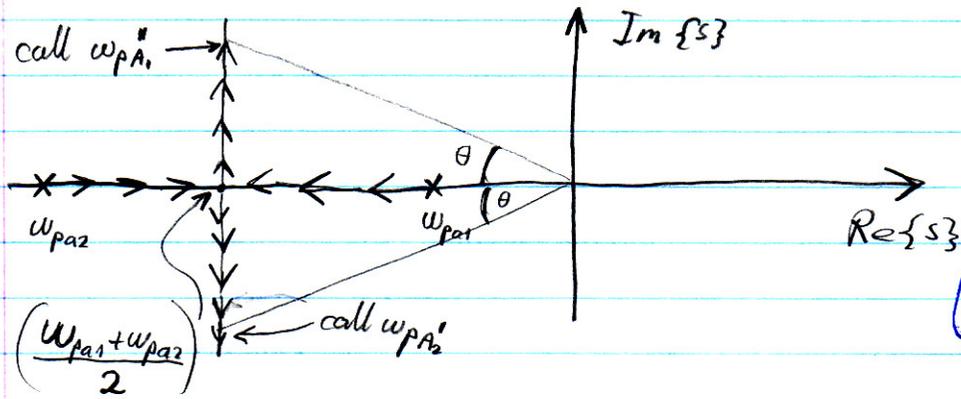Root Locus plot (verify) (pos. of  $\omega_{PA_i}$ )



$$\frac{a(s)}{1+f \cdot a(s)} = \frac{a_0 \cdot \omega_{pa1} \cdot \omega_{pa2}}{s^2 - (\omega_{pa1} + \omega_{pa2}) \cdot s + (1+a_0 \cdot f) \cdot \omega_{pa1} \omega_{pa2}}$$

Recall  $\theta = \cos^{-1} \zeta$  where  $\zeta$  = damping ratio

$\therefore \zeta = \cos \theta$ , so

$\zeta \rightarrow 0$  as  $\theta \rightarrow 90^\circ$


(i.e. as  $a_0 \cdot f \rightarrow \infty$ )

(i.e. as  $PM \rightarrow 0$ )

$\therefore$  Smaller PM  $\Rightarrow$  more ringing.

Ex. 3 ③ with  $a(s) = \frac{a_0}{(1-s/\omega_{pa1})(1-s/\omega_{pa2})(1-s/\omega_{pa3})}$

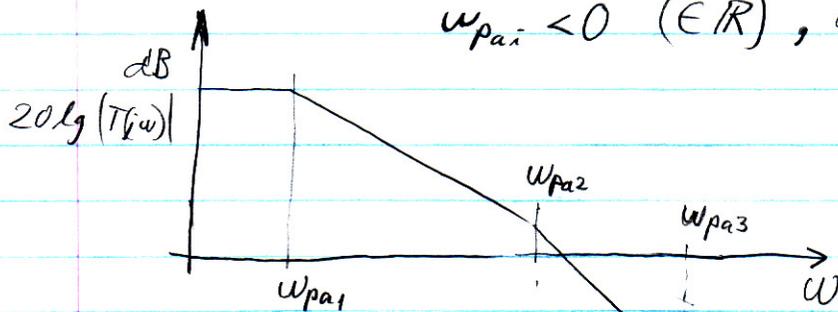$\omega_{pa_i} < 0 (\in \mathbb{R}), a_0 > 0 (\in \mathbb{R})$




$\Rightarrow -90^\circ < PM < 180^\circ$   
 $\Rightarrow$  can be unstable

6/7

Feb. 26, 2008 E.G.

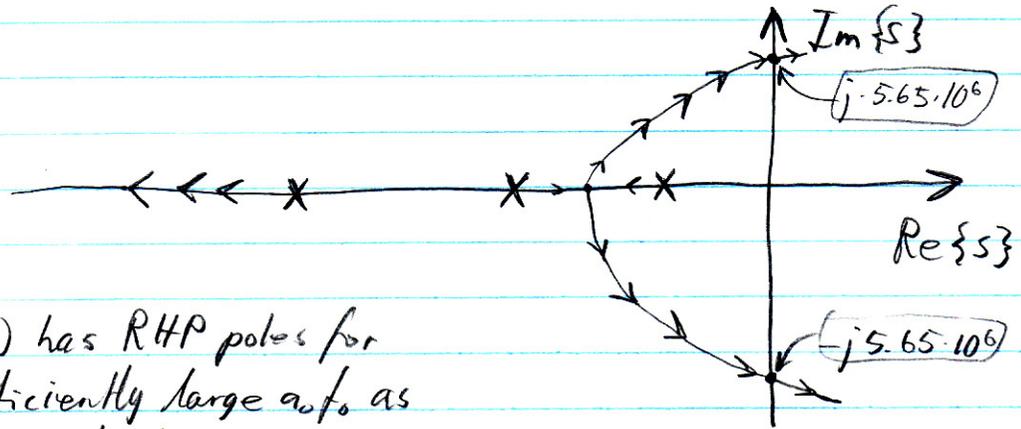
e.g. Suppose  $\omega_{p1} = -10^6 \frac{\text{rad}}{\text{sec}}$ ,  $\omega_{p2} = -2 \cdot 10^6 \frac{\text{rad}}{\text{sec}}$ ,  $\omega_{p3} = -10^7 \frac{\text{rad}}{\text{sec}}$   
Then the root locus plot is as follows:




$\therefore A(s)$  has RHP poles for sufficiently large  $a_0$  as expected.

Using SPICE to estimate  $T(j\omega)$

Ex4 Consider (3) with

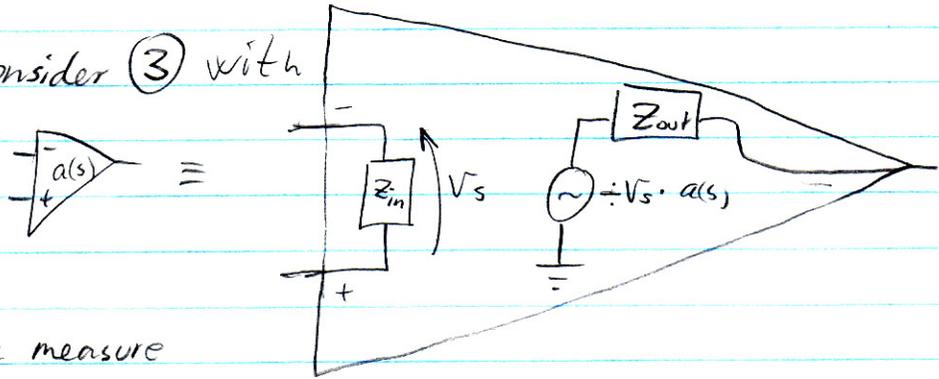

Suppose we measure  $T(j\omega)$  using:

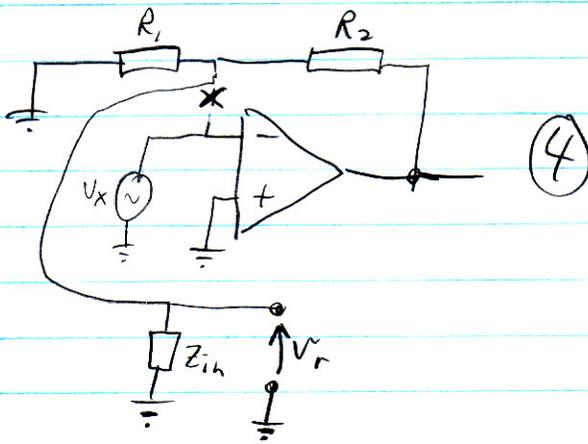

have:

- 1) Broken feedback loop
- 2) Applied test source after break
- 3) Loaded node prior to break as if it were not broken

7/7

Feb. 26, 2008 E.G.

First suppose  $Z_{in} = \infty$ ,  $Z_{out} = 0$

$$\text{Inspection} \Rightarrow \frac{v_r}{v_x} = -a(s) \cdot \frac{R_1}{R_1 + R_2} = -a(s) \cdot f_0 = -T(s)$$

$$\therefore T(s) = -\frac{v_r(s)}{v_x(s)}$$

$\therefore$  can use this approach to "measure"  $T(j\omega)$   
Often works, but must be careful in general.

Suppose  $Z_{in} \neq \infty$ ,  $Z_{out} \neq 0$

$$\text{AGR} \Rightarrow A(s) = A_0 \frac{T}{1+T} + A_0 \frac{1}{1+T}$$

Before  $A_0 = 0$  because  $Z_{out} = 0$

Now,  $A_0 \neq 0$

We still get  $T(j\omega)$  using (4) but analysis will miss poles contributed by  $A_0(s)$

$$N_{CCW, (0,0)}^{(1+T)} = Z_{(1+T)} - P_{(1+T)} =$$

$$= P_{cl.l.} - P_T = N_{CCW, (-1,0)}^T$$


$$N_{CCW, (-1,0)}^T = P_T - P_{cl.l.}$$

RHP poles & RHP

Zeros in general

(map from  $s$  to  
either  $T(s)$  or  
to  $(1+T(s))$ .)

SEC:

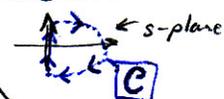

For stability,  $P_{cl.l.} = 0$

$$\Rightarrow N_{CCW, (-1,0)}^T = P_T$$


$$N_{CCW, (-1,0)}^T = \text{"\# RHP poles, open loop"} \div \text{"\# RHP poles, closed loop"}$$

1/5

ECE 264A Feb. 28, 2008 E.G.

Using SPICE to estimate  $T(j\omega)$

Ex 1

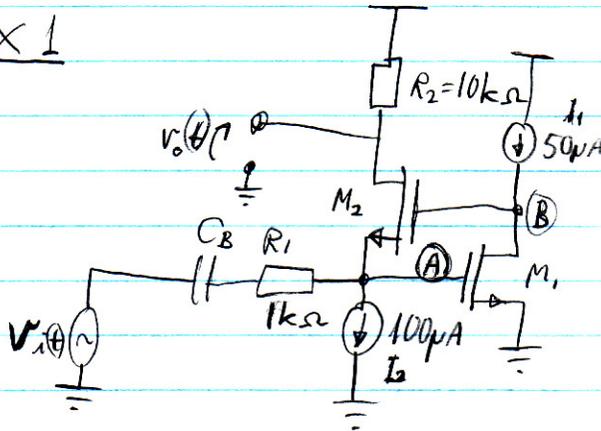

(1)

$$M_1: \frac{W}{L} = 15 \mu\text{m}/1 \mu\text{m}$$

$$M_2: \frac{W}{L} = 20 \mu\text{m}/1 \mu\text{m}$$

$C_B$  = large DC-blocking cap (assume  $C_B \approx \infty$ )

Observations

(i) A is a low impedance node:

- inside the loop bandwidth  $\Rightarrow$  A = almost virtual ground (HW)
- even with feedback disabled, impedance of A  $\approx 1k\Omega \parallel \left(\frac{1}{g_{m2}}\right)$

(ii) Similar reasoning  $\Rightarrow$  driving point resistance between nodes A and B is relatively small ( $\approx 1/g_{m1}$ )

(ii)  $\Rightarrow$  Reasonable to neglect  $C_{gd1}$ ,  $C_{gs2}$  (2)

Apply A.G.R. with  $g_{m1} \cdot v_{gs1} \equiv$  ref. source

$$\therefore A(s) = A_\infty(s) \cdot \frac{T(s)}{1+T(s)} + A_0(s) \cdot \frac{1}{1+T(s)}$$

$\rightarrow$  gain of C.G. amplifier formed by  $M_2$  (but with high impedance gate connection)

$$\frac{1}{g_{m2}} \approx 1k\Omega, \text{ so } A_0(0) \approx 5$$

The point is:  $T(s)$  does not give the whole stability "picture" because  $A_0(s)$  might have marginal stability.


2/5

Feb. 28, 2008

E.G.

- Good approach
- 1) Measure  $T(s)$  to estimate the degree of stab.
  - 2) If simulations show more ringing than expected, consider  $A_o(s)$

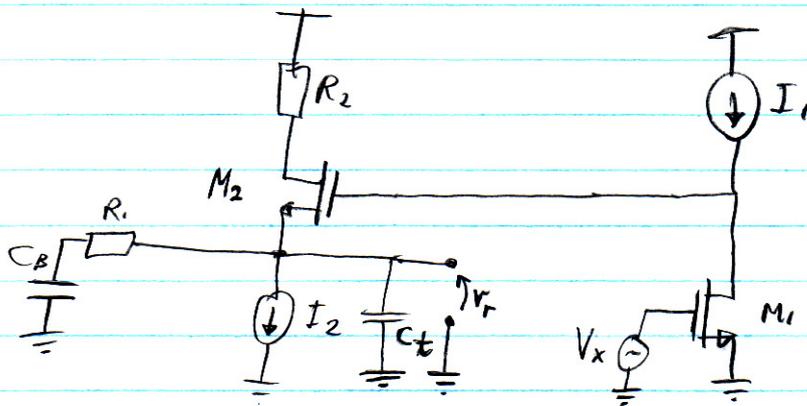②  $\Rightarrow$  Can "measure"  $T(j\omega)$  using:



③

where  
 $C_t \equiv C_{gst}$  (termination impedance)  
 DC-value of  $V_x$   
 $=$  DC-value of node (A) in ①

$\Rightarrow$

have "broken" feedback loop and applied test signal

$$\textcircled{3} \Rightarrow T(j\omega) = -\frac{v_r(j\omega)}{v_x(j\omega)}$$

$\rightarrow$  (same  $T(j\omega)$  as in A.G.R. if ② holds - verify)

$\Rightarrow$

simple test to find PM, GM, or Nyquist plot  
 simulations  $\Rightarrow$  PM  $\approx 90^\circ$


In general, this always works, but must:

- 1) Bias input node following break point as in the closed loop circuit.
- 2) Must terminate the node (prior to breakpoint) as in the closed loop circuit.

HW 6  $\Rightarrow$  Method of avoiding need to terminate output node.

Theory behind breaking feedback loops

Ex

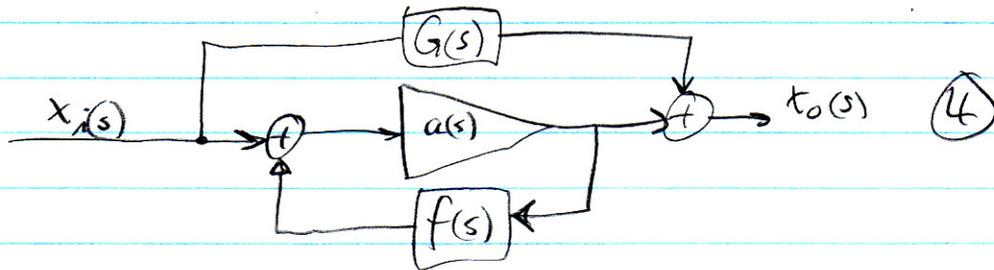

$$H(s) \equiv \frac{x_o(s)}{x_i(s)} = \frac{a(s)}{1 + a(s)f(s)} + G(s)$$

call A(s)

Both  $G(s)$  and  $A(s)$  } • have poles (in general)  
 } • affect stability

In circuits, often } •  $A(s) \Rightarrow$  desired behavior (dominant)  
 } •  $G(s) \Rightarrow$  parasitic signal-path (non-dominant)

$\therefore$  Feedback loop in (4)  $\Rightarrow A(s)$

Knowing  $A(s) \not\Rightarrow$  insight into how  $a(s)$  or  $f(s)$  can be modified to improve performance.

But

Knowing  $T(j\omega) \Rightarrow$  " ———— || ———— ...  
 ... ———— || ———— "

(via Nyq. crit., etc..)

Can "break" any point of feedback loop in (4) and "measure"  $T(j\omega)$  via simulation.


The problem: Usually have a circuit, not a B.D., to analyze. Previously have used A.G.R. for specific circuits to justify measuring  $T(j\omega)$  directly from circuit. (i.e. without first conv. to a B.D.)

Does this work in general?

4/5

Feb. 28, 2008 E.G.

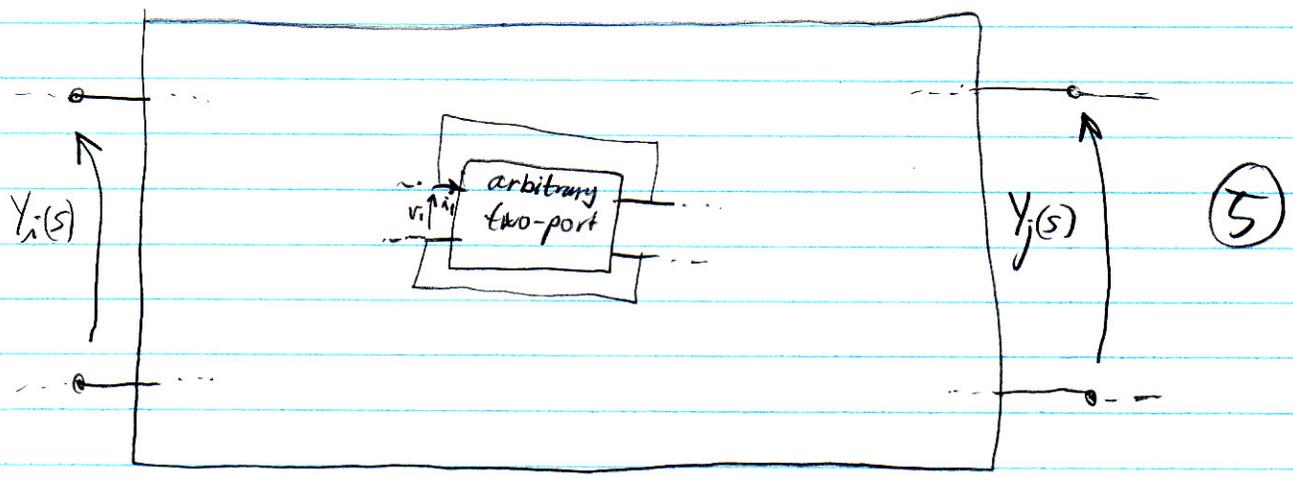Arbitrary LTI circuit containing a feedback loop




$Y$  is voltage, but could be current!

Let  $H(s) = \frac{Y_j(s)}{Y_i(s)}$

Note: Can draw (5) s.t.  $Y_i(s) = \text{current}$  and/or  $Y_j(s) = \text{current}$

Can redraw (5) as:

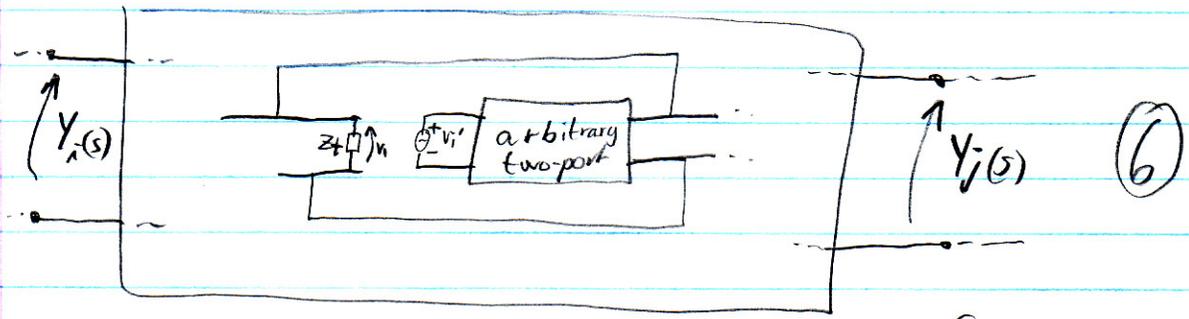

where  $v_i' = \alpha \cdot v_i$ , with  $\alpha \equiv 1$ ,  $Z_f \equiv \frac{v_i(s)}{i_i(s)}$  (input imp. of two-port depends on loading of  $Y_i(s)$  &  $Y_j(s)$  ports)



1/4

Note: For the version of the Nyquist Plot and Criterion presented previously, must have at least as many poles as zeros.

(More zeros <sup>(than poles)</sup>  $\Rightarrow$  inf. B.W. !)

Compensation

The problem: Given an amplifier and feedback network, how do we adjust or add components to achieve a desired stability margin?


Most often  $T(s)$  satisfies:

- (i)  $|T(0)| < \pi$  (neg. feedback at DC)
- (ii)  $T(s)$  has no RHP (incl.  $j\omega$  axis) poles
- (iii)  $|T(j\omega)| = 1$  has one pos. solution,  $\omega = \omega_u$

①  $\Rightarrow$  PM, GM valid indicators of stab. margin.

Ex 1:  $T(s) = T_0 \cdot \frac{1}{(1-s/\omega_{p1})(1-s/\omega_{p2})(1-s/\omega_{p3})}$  ②

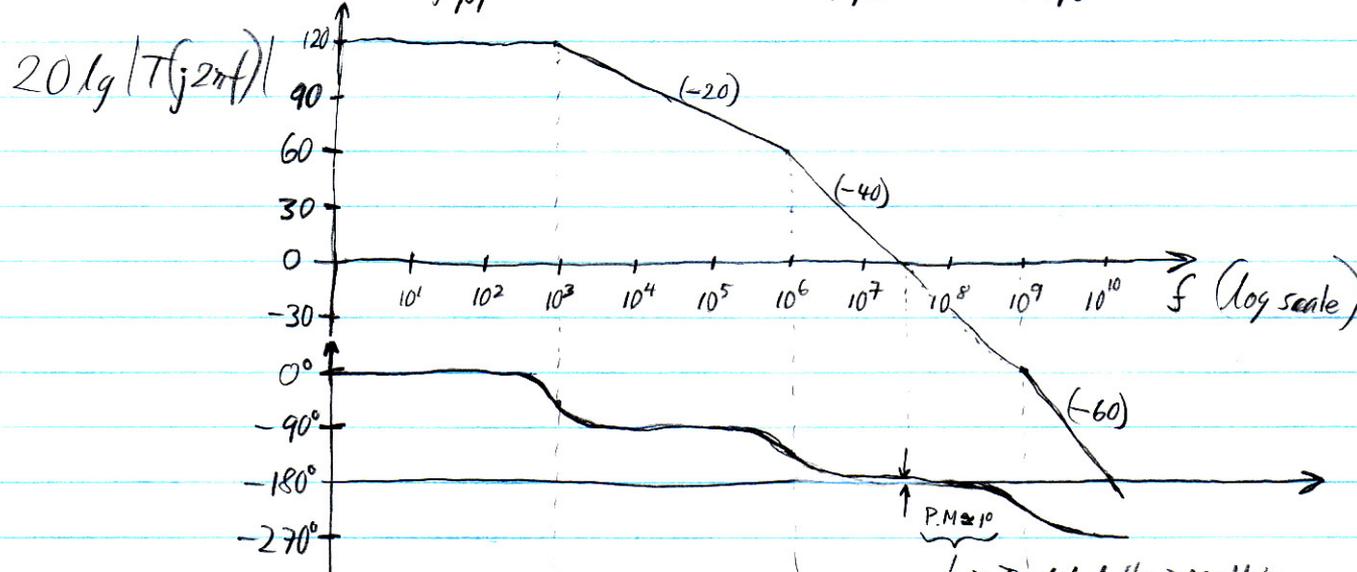with  $T_0 = 10^6$ ,  $f_{p1} = \frac{\omega_{p1}}{2\pi} = 10^3 \text{ Hz}$ ,  $f_{p2} = 10^6 \text{ Hz}$ ,  $f_{p3} = 10^9 \text{ Hz}$



Testet dette i Matlab: Fikk 0.004°

2/4

March 04, 2008

E.G.

### Observations

- i) Both  $\angle T(j\omega)$  and  $|T(j\omega)|$  decrease monotonically
- ii)  $PM \approx 45^\circ$  requires  $|f_{p2}| > f_u$

$\therefore$  Only 3 ways (compensation methods) to increase P.M.  
given  $T(s)$  has the form of (2)

- 1) Reduce  $T_0 \Rightarrow \omega_u$  decreases, but  $\angle T(j\omega)$  unchanged  
 $\Rightarrow$  P.M. increases

But: Trades C.L. accuracy for P.M.

(feedback benefits requires large  $T_0$ )

- 2) Reduce  $|f_{p1}|$

$\Rightarrow \omega_u$  decreases, but  $\angle T(j\omega)$  almost

unchanged for  $\approx 4 \cdot |f_{p1}|$  (2 octaves = 0.6 decades)

$\Rightarrow$  P.M. increases

But: Trades C.L. BW for P.M.

- 3) Increase  $|f_{p2}|$

$\Rightarrow \omega_u$  increases until  $|f_{p2}| > f_u$ , then remains unchanged  
but  $\angle T(j\omega_u)$  increases

$\Rightarrow$  P.M. increases (up to  $90^\circ$ )

But: Usually not possible without simultaneously  
reducing  $|f_{p1}|$ .

Jargon:

1)  $\equiv$  "gain compensation"

2)  $\equiv$  "dom. pole compensation"

2)+3)  $\equiv$  "pole splitting compensation" or "miller compensation"


See (3/5)  
Jan. 17

Ex 2 Suppose we can add LHP zero to  $T(s)$  given by ②

e.g. let  $T'(s) = T(s) \cdot (1 - s/w_{z1})$

same as in Ex 1.

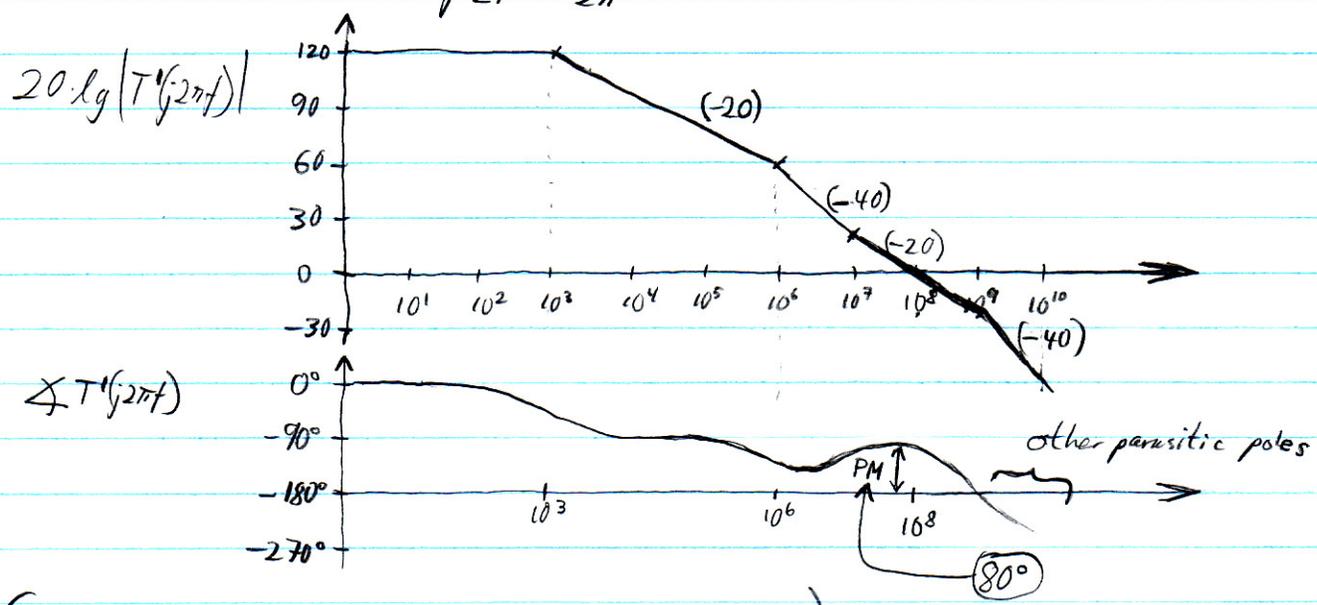with  $f_{z1} = \frac{w_{z1}}{2\pi} = -10^7 \text{ Hz}$



(zero approx at  $1.2 \cdot w_u \leftarrow$  rule of thumb)

Observations


- i) LHP zero added pos. phase shift without significantly changing  $f_u$  ( $f_u$  gikk fra  $10^{7.5}$  til  $10^8$  Hz)
  - $\Rightarrow$  Increased PM (fra  $\sim 0^\circ$  til  $80^\circ$ )
  - $\Rightarrow$  Adding LHP zero  $\equiv$  compensation strategy

ii) A RHP zero would have decreased PM  $\rightarrow$  to  $-89.4^\circ \Rightarrow$  unstable! called "lead compensation"

Lead compensation is used in 2-stage CMOS op-amps (soon).


$\rightarrow$  Vil nesten ikke endre  $w_u$  men likevel påvirke fasen til en viss grad. Denne tommelfinger-regelen er ikke brukt her. (Her er  $|z| < w_u$ .)

Ex3 Gain compensation

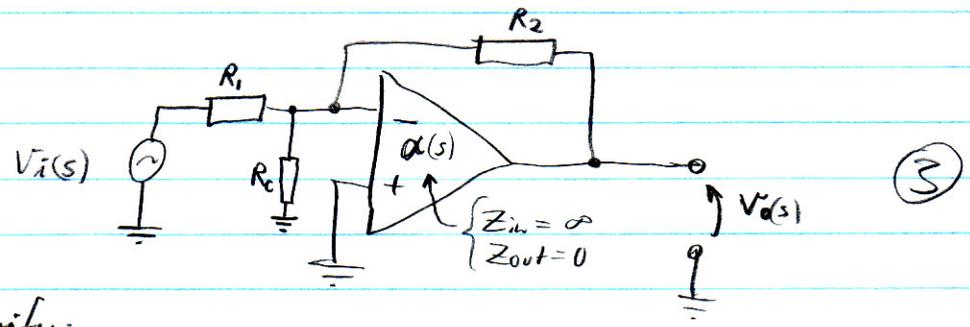

Can verify:

③ ⇒

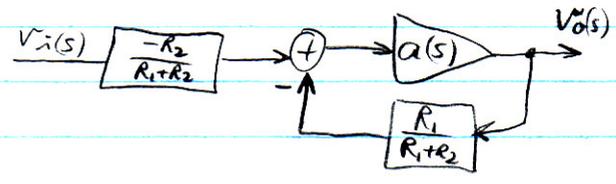

Where

$$a(s) = \frac{R_1 // R_2 // R_c}{R_1 // R_2} \cdot \alpha(s)$$

e.g. Suppose  $\alpha(s)$  = 3-pole, no-zero transfer fcn.

⇒  $T(s)$  given by ②

⇒ decreasing  $R_c$  ⇒ smaller  $T_0$  but same  $\angle T(j\omega)$  as before

e.g. suppose with  $R_c = \infty$ ,  $T(s)$  = same as Ex 1

Then  $PM \approx 4^\circ$  (very poor relative stability)


{ Jeg fikk 0.004° PM i Matlab... }

e.g. suppose  $R_1 = R_2$  and  $R_c = \frac{R_1}{1000}$

Then  $PM \approx 35^\circ$

But went from  $T_0 = 120dB$  to  $T_0 = 66dB$

Ex4 Dom. pole compensation in CMFB

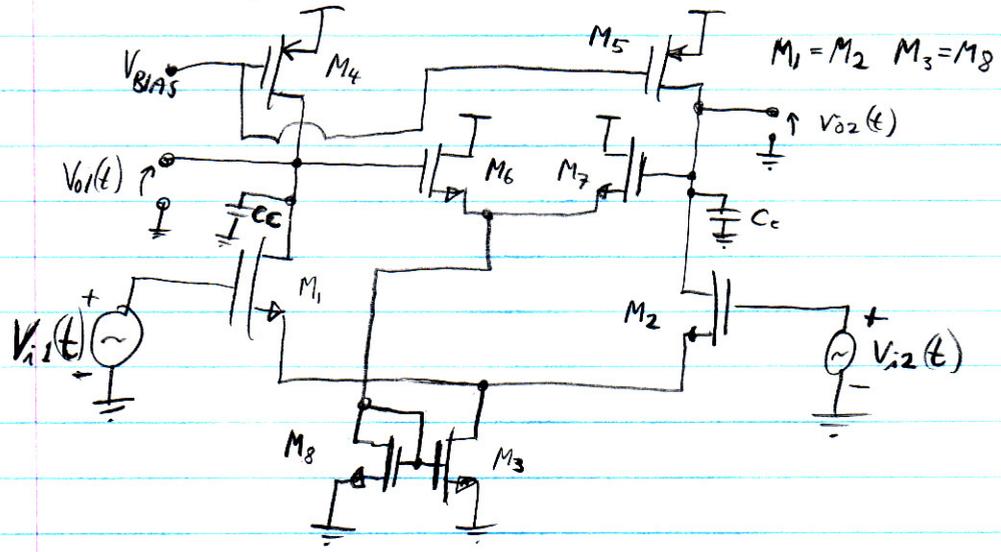

$M_1 = M_2$   $M_3 = M_8$

$M_4 = M_5$

$M_6 = M_7$

Exercise:  
Consider how  $C_c$  implements dom. pole compensation!

1/5


ECE 264A

March 06, 2008 E.G.

Ex 4 from last time

(recall diff pair with CMFB diagram)

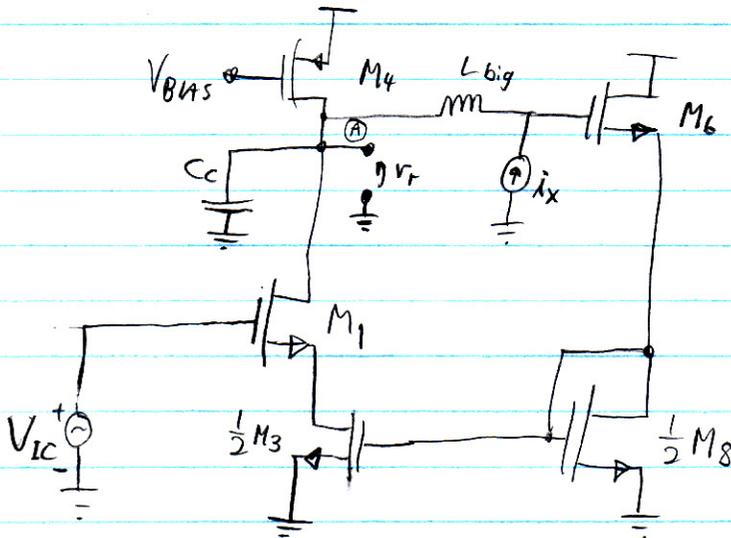CM  $\frac{1}{2}$ -circuit &  $T(s)$  measurement config



( $L_{big} \Rightarrow$  zero-freq voltages at two terminals of  $L_{big}$  are same, but  $L_{big}$  blocks non-zero frequency components)

valid if  $C_{gs6} \ll C_c$

Note: trans impedance from node (A) to all other nodes is small \*  
 $\Rightarrow \approx \frac{1}{C_c \cdot R_A} =$  pole of  $T(s)$  ( $C_c$  has little effect on other poles of  $T(s)$ )

where  $R_A =$  small-sig. res. from node (A) to small-sig ground

$\Rightarrow$  (A) = dom. pole node


$\Rightarrow$  can reduce  $(f_{p1})$  (only) by increasing  $C_c$

Strøm injisert innle (A) vil i liten grad påvirke spenningene på andre noder i kretsen.  $\frac{V_{andre}}{I_{\text{in}}}$  = liten =  $Z_{trans}$ .

2/5

March 06, 2008 E.G.

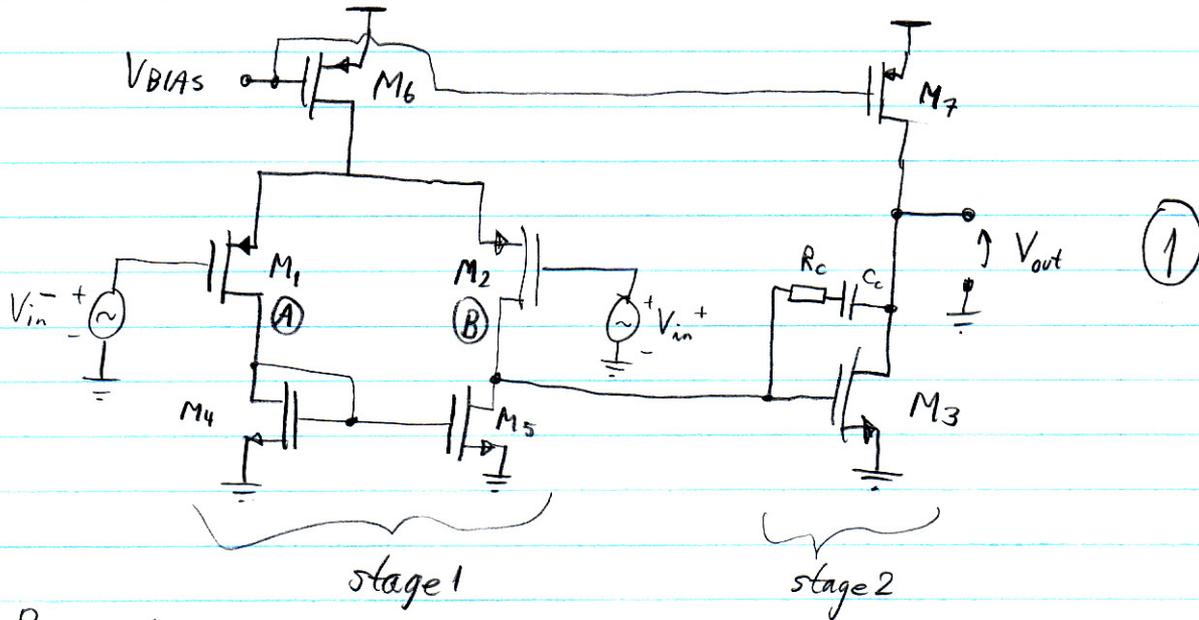Ex Two-stage op-amp with lead compensation



Remarks:

1) Typ. designed s.t. pole assoc. with (A)

$$\text{i.e. } p_A = \frac{-g_{m4}}{C_A} \leftarrow \text{cap from (A) to small-sig. ground}$$

is s.t.  $|p_A| \gg \omega_u \leftarrow \text{unity-gain freq.}$

2) A source-follower buffer stage is sometimes added to (1)

3) Could replace pMOSs by nMOSs and vice versa, but pMOSs have better  $1/f$  noise performance so (1) as shown has better  $1/f$  noise (why?).

First consider with  $R_c = 0$

Using prev. results and Remark 1):

① has 2 significant poles,  $p_1$  &  $p_2$  and 1 significant zero,  $z_1$  given by:

$$p_1 \cong -\frac{1}{g_{m3} R_1 R_2 C_c} \quad \text{② where } \begin{aligned} R_1 &\equiv r_{ds2} \parallel r_{ds5} \\ R_2 &\equiv r_{ds3} \parallel r_{ds7} \end{aligned}$$

and  $C_c \gg C_{gs}$  is assumed

$$p_2 \cong -\frac{g_{m3} C_c}{C_{d3} C_{gs3} + C_c (C_{d3} + C_{gs3})} \quad \text{③}$$

Where  $C_{d3}$  = total cap. from output to ground from  $M_3, M_7$ , and any load.

$$\cong -\frac{g_{m3}}{C_{d3}} \quad \text{(often)}$$

$$z_1 \cong \frac{g_{m3}}{C_c} \quad \text{④}$$

- $p_1$  = dom. pole (sets open loop BW)
- $p_2$  = non-dom pole (with  $p_1$  sets open-loop phase shift at unity gain freq.)
- $z_1$  = RHP-zero (adds neg. phase shift - just like a LHP pole)

eg.  $g_{m3} = 1 \cdot 10^{-3} \Omega^{-1}$ ,  $R_1 = R_2 = 100k\Omega$ ,  $A_{v01} = 70$  } ⑤

$\downarrow$   
DC-gain of stage 1

$$C_{d3} = C_{gs3} = 350fF, C_c = 1pF$$

$$\text{②} - \text{⑤} \Rightarrow \begin{aligned} p_1 &= -100 \cdot 10^3 \frac{\text{rad}}{\text{sec}} && (-16k\text{Hz}) \\ p_2 &= -1.2 \cdot 10^9 \frac{\text{rad}}{\text{sec}} && (-191\text{MHz}) \\ z_1 &= 10^9 \frac{\text{rad}}{\text{sec}} && (159\text{MHz}) \end{aligned}$$

$$A_{v02} (\equiv \text{DC-gain of stage 2}) = -g_{m3} \cdot R_2 = -100$$

$$\therefore A_v(s) \cong 7000 \cdot \frac{(1 - s/10^9)}{(1 + s/10^5)(1 + s/1.2 \cdot 10^9)}$$

$$\therefore \omega_u \cong 7.1 \cdot 10^8 \frac{\text{rad}}{\text{sec}} \quad (113\text{MHz}) \quad \text{(verify)}$$

4/5

March 06, 2008 E.G.

$$\begin{aligned} \angle A_v(j\omega_u) &= \tan^{-1}\left(-\frac{7.1 \cdot 10^8}{10^9}\right) - \tan^{-1}\left(\frac{7.1 \cdot 10^8}{10^5}\right) - \tan^{-1}\left(\frac{7.1 \cdot 10^8}{1.2 \cdot 10^9}\right) \\ &\cong \underbrace{-35.4^\circ}_{\text{zero}} - \underbrace{90^\circ}_{\text{dom. pole}} - \underbrace{30.6^\circ}_{\text{non-dom. pole}} = -156^\circ \end{aligned}$$

If  $f(s) = 1$ , then  $T(s) = A_v(s)$  so

$$\text{P.M.} = 180^\circ - 156^\circ = \underline{24^\circ} \text{ (low P.M.)}$$

- Note:
- 1) Increasing  $C_c$  reduces neg. phase shift from  $p_2$  at  $\omega_u$  but increases  $\angle z_1$  at  $\omega_u$  (because  $\omega_u$  decreases but so does  $z_1$ )
  - 2) Situation is actually worse than calculated because of pole at  $\textcircled{A}$

Heuristics: As  $\omega$  increases, feed fwd. path through  $C_c$  begins to dominate the gain path through  $M_3$ . Gain path through  $M_3$  has negative polarity, but feed-fwd. path through  $C_c$  has phase  $\rightarrow 0$  as  $\omega \rightarrow \infty \Rightarrow$  As  $\omega \rightarrow \infty$ , have pos. feedback

Now consider with  $R_c > 0$

Can show,  $R_c \neq 0 \Rightarrow$  have  $z_1 \cong \frac{1}{C_c(\frac{1}{g_{m3}} - R_c)}$  ⑥  
 have a 3<sup>rd</sup> pole,  $p_3$

Usually:

- 1)  $|p_3| \gg |p_1|, |p_2|, |z_1|$ , so can ignore  $p_3$
  - 2)  $p_1, p_2$  are hardly affected by  $R_c$
- ⑦

⑥  $\Rightarrow R_c > \frac{1}{g_{m3}} \Rightarrow z_1$  "moves" to LHP  
 $\Rightarrow z_1$  contributes pos phase shift

Fact: ⑦ breaks down for very large  $R_c$ .

5/5

March 06, 2008 E.G.

Typical rule of thumb: Choose  $R_c$  s.t.  $|z_1| \cong 1.2 \cdot \omega_u$  (8)

$$(6), (8) \Rightarrow 1.2 \cdot \omega_u \cong \left| \frac{1}{C_c(\frac{1}{g_{m3}} - R_c)} \right|$$

$$R_c = \frac{1}{g_{m3}} + \frac{1}{1.2 \cdot \omega_u \cdot C_c} \quad (9) \quad (\text{for } R_c > \frac{1}{g_{m3}})$$

e.g. (using (5)) (9)  $\Rightarrow R_c = 2.17 \text{ k}\Omega$

$$\text{Now } \angle A_v(j\omega) = \tan^{-1}\left(\frac{\omega_u}{1.2 \cdot \omega_u}\right) - 90^\circ - 30.6^\circ \cong -80.8^\circ$$

$\therefore$  new P.M. for  $f(s) = 1$ : P.M.  $\cong 99.2^\circ$

$\Rightarrow$  Can afford to reduce  $C_c$  ( $\Rightarrow$  increases BW) to reduce P.M. (typ. want P.M.  $> 65^\circ$ )

Closed loop system:

- critically damped if P.M. =  $76^\circ$
- gain peaking if P.M.  $< 66^\circ$



2/4

March 11, 2008 E.G.

4)  $p_1 \Rightarrow$  3dB BW and introduces  $-90^\circ$  phase at  $\omega_u$   
 $p_2, z_1 \Rightarrow$  PM (i.e. P.M. varies with  $p_2, z_1$ ; not with  $p_1$ )  
 assumes  $|p_2|, |z_1| \approx 10 \cdot |p_1|$

General:  
 Zero is placed near  $\omega_u$

5)  $R_c$  chosen s.t.  $z_1$  in LHP  $\Rightarrow$  introduces pos. phase shift at  $\omega_u$

Jargon: PM of an open-loop op-amp  $\equiv 180^\circ + \angle A_v(j\omega_u)$   
 why? When connected as voltage follower, i.e.  $f=1$ , (hardest non-attenuating config to compensate) loop gain  $\equiv T(j\omega) \equiv A_v(j\omega)$

Usually, ① designed s.t.  $|p_2|, |z_1| > \omega_u$   
 same order of mag.!

$$\begin{aligned} \therefore \textcircled{3} \Rightarrow |A_v(j\omega_u)| &\approx \left| g_{m1} g_{m3} R_1 R_2 \frac{1}{1 - j\omega_u/p_1} \right| \\ &\approx g_{m1} g_{m3} R_1 R_2 \cdot \left| \frac{p_1}{j\omega_u} \right| \end{aligned}$$

$$\therefore \textcircled{4} \Rightarrow \approx \left| \frac{g_{m1}}{C_c \cdot j \cdot \omega_u} \right|$$


$$\therefore |A_v(j\omega_u)| = 1 \Rightarrow \omega_u \approx \frac{g_{m1}}{C_c} \quad \textcircled{7}$$

$$\text{P.M.} = 180^\circ - \tan^{-1} \frac{\omega_u}{z_1} + \tan^{-1} \frac{\omega_u}{p_2} - \underbrace{90^\circ}_{\text{contrib. by } p_1} \quad \textcircled{8}$$

Problem: How to maintain constant P.M. across temp./process/supply voltage variations?

(5) - (8)  $\Rightarrow$  P.M. depends on  $g_{m1}, g_{m3}, C_{d3}, C_{gs3}, C_c, R_c$   
 These parameters vary and don't track each other

A Solution: Replace stage 2 of (1) by:

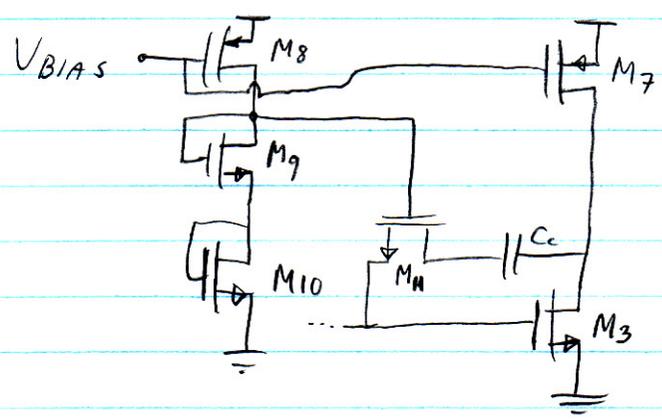

with  $\frac{W_7/L_7}{W_3/L_3} = \frac{W_8/L_8}{W_{10}/L_{10}}$  (10)

(9)

$M_{11}$  biased by  $M_8 - M_{10} \cong R_c$   
 No DC-current  $\Rightarrow M_{11}$  in triode  
 $\Rightarrow R_c \cong \frac{1}{\mu_n C_{ox} \left(\frac{W_{11}}{L_{11}}\right) (V_{GS_{11}} - V_{T_n})}$   
 call  $V_{eff_{11}}$

$g_{m3} = \mu_n C_{ox} \left(\frac{W_3}{L_3}\right) \cdot V_{eff3}$   
 $\therefore R_c g_{m3} = \frac{\left(\frac{W_3}{L_3}\right) V_{eff3}}{\left(\frac{W_{11}}{L_{11}}\right) V_{eff_{11}}}$  (11)

$\therefore (6) \Rightarrow Z_1 = \frac{g_{m3}}{C_c \cdot \left[1 - \left[\frac{\left(\frac{W_3}{L_3}\right) V_{eff3}}{\left(\frac{W_{11}}{L_{11}}\right) V_{eff_{11}}}\right]}\right]}$  (12)

(7), (12)  $\Rightarrow \frac{W_u}{Z_1} = \frac{g_{m1}}{g_{m3}} \cdot \left[1 - \left[\frac{\left(\frac{W_3}{L_3}\right) V_{eff3}}{\left(\frac{W_{11}}{L_{11}}\right) V_{eff_{11}}}\right]\right]$

(5), (7)  $\Rightarrow \left|\frac{W_u}{p_2}\right| = \frac{g_{m1}}{g_{m3}} \cdot \frac{C_{d3} + C_{gs3}}{C_c}$

$\mu_n \cdot C_{ox} \approx K'$

$\frac{g_{m1}}{g_{m3}} = \frac{\sqrt{2 \cdot \mu_p \cdot C_{ox} \cdot \left(\frac{W_1}{L_1}\right) \cdot I_{D1}}}{\sqrt{2 \mu_n \cdot C_{ox} \left(\frac{W_3}{L_3}\right) I_{D3}}}$

Facts:

- 1)  $\mu_p/\mu_n \cong \text{const.}$  for a given process
  - 2)  $I_{D1}/I_{D3} \cong \text{const.}$  because derived from a common bias network
- $\Rightarrow \frac{g_{m1}}{g_{m3}} \cong \text{const.}$

3)  $\frac{C_{d3} + C_{gs3}}{C_c} \neq \text{const.}$ , but does not vary much over process & temp. because dominated by oxide capacitor

4/4

March 11, 2008 E.G.

$\therefore P.M. \approx \text{const. provided } V_{\text{eff}3}/V_{\text{eff}11} \approx \text{const.}$

$$\textcircled{10} \Rightarrow \begin{aligned} V_{\text{eff}10} &= V_{\text{eff}3} \\ V_{\text{eff}9} &= V_{\text{eff}11} \end{aligned}$$

$$\therefore \frac{V_{\text{eff}3}}{V_{\text{eff}11}} = \frac{V_{\text{eff}10}}{V_{\text{eff}9}} = \frac{\sqrt{\frac{2 \cdot I_{D10}}{M_n \cdot C_{ox} (W_{10}/L_{10})}}}{\sqrt{\frac{2 \cdot I_{D9}}{M_n \cdot C_{ox} (W_9/L_9)}}} = \sqrt{\frac{W_{10}/L_{10}}{W_9/L_9}} = \left\{ \begin{array}{l} \text{ratio of} \\ \text{like quantities} \end{array} \right.$$

$\therefore P.M. \approx \text{indep. of process \& temperature}$

The "reference source" in Blackman's Impedance Relation (BIR) and the Asymptotic Gain Formula (AGF):

The values of the variables in BIR ( $Z_{ab}^o, T_{sc}, T_{oc}$ ) or in AGF ( $A_\infty, A_o, T$ ) depend on which reference source we use.

Of course, the resulting impedance ( $Z_{ab}$ ) or gain ( $A$ ) is the same, independent of our choice of reference source.

BIR & AGF was covered on Jan. 31 in class.