

$$1 N_p = 20 \lg(e) \text{ dB} \\ \approx 8.7 \text{ dB}$$



rad
m

Np
m

$$\Gamma(l) = \Gamma_{\text{load}} \cdot e^{-2j\beta l} \cdot e^{-2\alpha l}$$

$$\beta = \frac{2\pi}{\lambda}$$

$$\beta \cdot l = 2\pi \cdot \frac{l}{\lambda} \quad \text{el. length}$$

$$\begin{aligned} \frac{1}{2} \text{ runde: } \frac{1}{4}\lambda &\Rightarrow \beta l = \pi/2 \\ 1 \text{ runde: } \frac{1}{2}\lambda &\Rightarrow \beta l = \pi \end{aligned}$$

$$v_p = \frac{c}{\sqrt{\epsilon_r}} \quad \lambda = \frac{\lambda_0}{\sqrt{\epsilon_r}}$$

Lengde på kablet i radianer. På Smith-diagrammet bliv det dobbelt så langt

$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{Z_L - 1}{Z_L + 1}$$

$$Z_L = Z_0 \cdot \frac{1 + \Gamma}{1 - \Gamma}$$

$$Z_{in} = \frac{Z_L + jZ_0 \cdot \tan \beta l}{Z_0 + jZ_L \cdot \tan \beta l} \cdot Z_0$$

$$Z_{in} = \frac{Z_L + Z_0 \cdot \tanh(j\beta l)}{Z_0 + Z_L \cdot \tanh(j\beta l)} \cdot Z_0$$

$$\gamma = \alpha + j\beta$$

$$\tanh(x) = \frac{e^x - e^{-x}}{e^x + e^{-x}} = \frac{e^{2x} - 1}{e^{2x} + 1} = -j \cdot \tan(jx)$$

$$SWR = \frac{1 + |\Gamma|}{1 - |\Gamma|}$$

$$|\Gamma| = \frac{SWR - 1}{SWR + 1}$$

$$SWR = \frac{1 + \sqrt{\frac{P_{ref}}{P_{ind}}}}{1 - \sqrt{\frac{P_{ref}}{P_{ind}}}}$$

el. length
0-90°


$$\text{CogL: } l < \frac{\lambda}{4}$$

$$Z_{in} = jZ_0 \tan(\beta l) = j\omega L$$

$$L = \frac{Z_0 \tan(\beta l)}{\omega}$$

$$Z_{in} = -j \cdot Z_0 / \tan(\beta l) = \frac{-j}{\omega C}$$
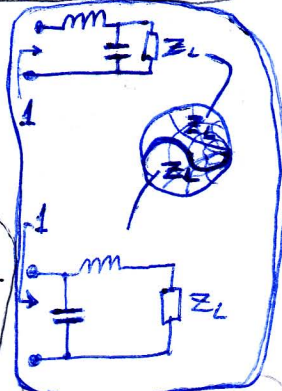
$$C = \frac{\tan(\beta l)}{\omega \cdot Z_0}$$




$$I_{m1} = \sqrt{R_e - R_e^2}$$

$$I_{m2} = \frac{I_{m1}}{R_e}$$

$$\begin{aligned} V &= V_0^+ e^{\alpha l} e^{j\beta l} (1 + \Gamma e^{-2\alpha l} e^{-j2\beta l}) \\ &= V_0^+ e^{\alpha l} e^{j\beta l} [1 + \Gamma e^{-2\alpha l} e^{-j2\beta l}] \end{aligned}$$

$$V = V_0^+ e^{j\gamma l} + V_0^- e^{-j\gamma l}$$


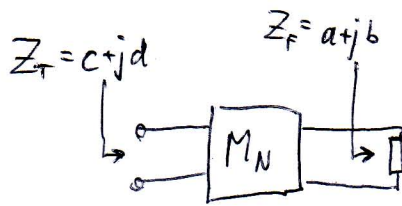
$$I = I_0^+ e^{j\gamma l} + I_0^- e^{-j\gamma l}$$



$$a > c$$

$$b^2 > (c - a) \cdot a$$

$$ac < c^2 + d^2 \Leftrightarrow ac < |Z_T|^2$$

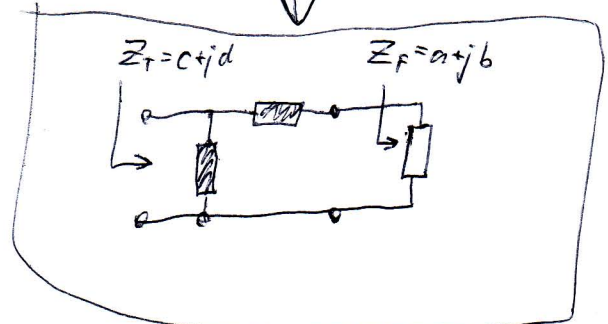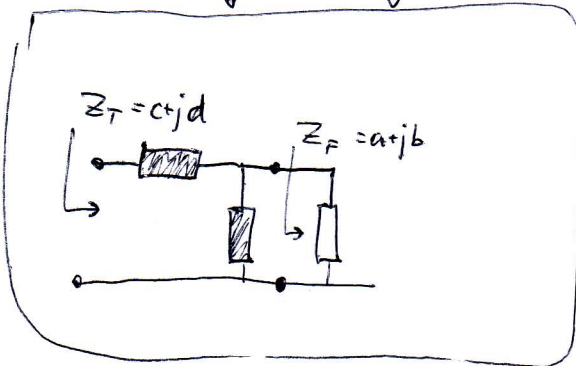

Normalize to $c = \text{Re}\{Z_T\} \Omega$

Normalize to
 $\text{Re}\{Y_T\} = \text{Re}\left\{\frac{1}{Z_T}\right\} \text{ adm}$
 or $\frac{1}{\text{Re}\left\{\frac{1}{Z_T}\right\}} = c + \frac{d^2}{c} \Omega$

- Z_F is outside A
- Y_F outside B
- add parallel susceptance (circle A)
- Change $Y \rightarrow Z$
- add series reactance
- done.

- Z_F is outside B (real part < 1)
- Add series reactance (circle A)
- Change $Z \rightarrow Y$
- Add parallel ~~add~~ susceptance to reach $Y_T = \frac{1}{Z_T}$.
- done

63
64

$$L = \frac{Z_0 \tan(\beta l)}{j\omega} \approx \frac{Z_0 \beta l}{j\omega}$$

$$C = \frac{\tan(\beta l)}{j\omega Z_0} \approx \frac{\beta l}{j\omega Z_0}$$

$\frac{\beta l < \frac{\pi}{6}}{1 < \frac{\lambda}{12}}$


$\beta = \frac{2\pi}{\lambda}$

$$\begin{bmatrix} b_1 \\ b_2 \\ b_3 \end{bmatrix} = \begin{bmatrix} S_{11} & S_{12} & S_{13} \\ S_{21} & S_{22} & S_{23} \\ S_{31} & S_{32} & S_{33} \end{bmatrix} \begin{bmatrix} a_1 \\ a_2 \\ a_3 \end{bmatrix}$$

$$V_n = \sqrt{Z} \cdot (a_n + b_n)$$

$$\left(\begin{array}{c} \text{ref.} \\ \left[\frac{V}{\sqrt{Z}} \right] \\ = \left[\frac{V}{\sqrt{Z}} \right] \end{array} \right) = \left(\begin{array}{c} \left[\frac{P_1}{P_2} \right] \\ \text{(no dimension)} \end{array} \right) \cdot \left(\begin{array}{c} \text{Incident} \\ \left[\frac{V}{\sqrt{Z}} \right] \end{array} \right)$$

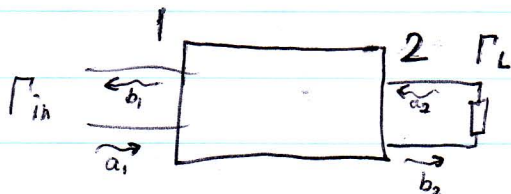$S_{nn} = \Gamma_{\text{in}}$ for den n-te porten
 $1 + S_{nn} = T$ og fortæller
 hvor stor andel af spændingen
 som går videre, uden hensyn
 til impedans.
 a, b og S ind beregnes også ut i pa porten
 sin impedans!



$$\Gamma_{\text{in}} = \frac{b_1}{a_1} = S_{11} + \frac{S_{21} \Gamma_L S_{12}}{1 - S_{22} \Gamma_L}$$

$$S = \begin{bmatrix} a & d & g \\ b & e & h \\ c & f & i \end{bmatrix}$$

Tapsfri, lineær, resiprok

$$|d|^2 + |e|^2 + |f|^2 = 1 \quad (\text{alle kolonner})$$

$$ga^* + hb^* + ic^* = 0 \quad (\text{mult. af to kolonner})$$


$$a_1 = \frac{V_{01}^+}{\sqrt{Z_{01}}}$$

$$b_1 = \frac{V_{01}^-}{\sqrt{Z_{01}}}$$

$$\left[\frac{V}{\sqrt{Z}} \right] = \left[\frac{V}{\sqrt{Z}} \right]$$

Couplers

3-port

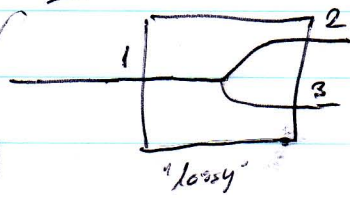

There are
no matched,
lossless
3-port
couplers!

$$|S_{11}|^2 = \text{reflection loss}$$

$$|S_{21}|^2 = \text{insertion loss}$$

$$|S_{31}|^2 = \text{coupled power}$$


T-junction

$$S = \begin{bmatrix} -1/3 & 2/3 & 2/3 \\ 2/3 & -1/3 & -2/3 \\ 2/3 & 2/3 & -1/3 \end{bmatrix}$$

lossless


Res. T
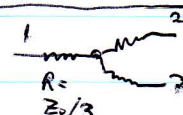
$$S = \begin{bmatrix} 0 & 1/2 & 1/2 \\ 1/2 & 0 & 1/2 \\ 1/2 & 1/2 & 0 \end{bmatrix}$$



50% ave eff $\rightarrow$ noise

matched

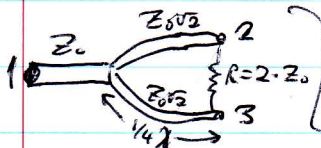

Wilkinson

$$S = \frac{-j}{\sqrt{2}} \cdot \begin{bmatrix} 0 & 1 & 1 \\ 1 & 0 & 0 \\ 1 & 0 & 0 \end{bmatrix}$$


Combiner:

$$b_1 = \frac{1}{\sqrt{2}} \cdot (a_2 + a_3)$$

$$P_{\text{out}} = \frac{1}{2} \cdot (P_2 + P_3)^2$$

(Unequal power div: pg. 74)

4-port

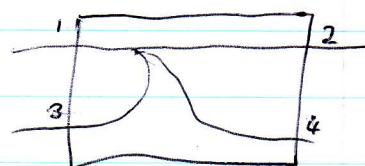

$$|S_{11}|^2 = \text{Ref. loss } (0)$$


$$|S_{21}|^2 = \text{Insertion loss } (0.5, 0.9, 0.99)$$

$$|S_{31}|^2 = \text{Isolation } (0 = -\infty \text{ dB})$$

$$|S_{41}|^2 = \text{Coupled power } \begin{pmatrix} 0.5 \\ 3\text{dB} \end{pmatrix} \begin{pmatrix} 0.1 \\ 10\text{dB} \end{pmatrix} \begin{pmatrix} 0.01 \\ 20\text{dB} \end{pmatrix}$$

Branch-line (90°)

(Applications: pg. 81)

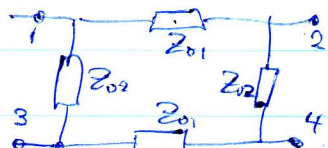

$$Z_{01} = Z_0/\sqrt{2}$$

$$Z_{02} = Z_0$$


$$\text{length} = \lambda/4$$

$$S = \frac{-1}{\sqrt{2}} \cdot \begin{bmatrix} 0 & j & 0 & 1 \\ j & 0 & 1 & 0 \\ 0 & 1 & 0 & j \\ 1 & 0 & j & 0 \end{bmatrix}$$

$$\begin{pmatrix} 2: -90^\circ \\ 4: -180^\circ \end{pmatrix} \text{ over}$$

Unequal Power division: Lecture 10 pg 78-79

Rat-race (0-180°)

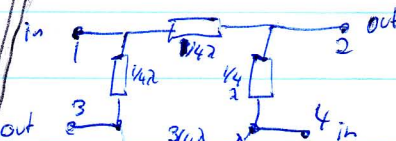

$$3\text{dB: } Z = Z_0/\sqrt{2}$$


inp a_1 : in-phase
inp a_4 : out of phase

$$S = \frac{-j}{\sqrt{2}} \cdot \begin{bmatrix} 0 & 1 & 1 & 0 \\ 1 & 0 & 0 & 1 \\ 1 & 0 & 0 & 1 \\ 0 & 1 & -1 & 0 \end{bmatrix}$$

(Not 3dB: page 79, Lecture 10)

Noise

Attenuator

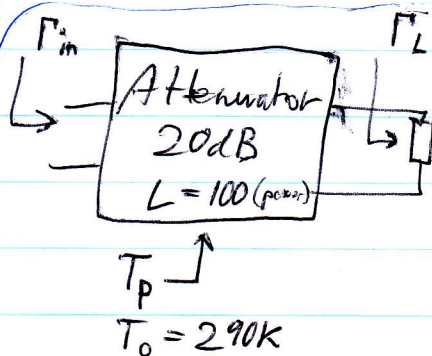

$$\Gamma_{in} = \frac{1}{L} \cdot \Gamma_L$$

$$NF_{att} = L$$

$$T_{eq} = (NF - 1) \cdot T_p = (L - 1) \cdot T_p$$

$$NF_{att} = 1 + \frac{T_{eq}}{T_0} = 1 + (L - 1) \frac{T_p}{T_0} \quad (= L \text{ n r } T_p = T_0)$$

$$\text{st y ut} = \frac{1}{L} \cdot (\text{st y vi sender inn p r inngangen}) + \frac{L-1}{L} \cdot (\text{attenuatoren sin st y})$$

$$NF = \frac{T_0 + T_{eq}}{T_0} = 1 + \frac{T_{eq}}{T_0} \approx \frac{SNR_i}{SNR_o}$$

$$T_{eq} = (NF - 1) \cdot T_0$$

$$P = kTB \quad (\cdot G \text{ for } P_{\text{noise out of ampl.}})$$

$$k = 1.38 \cdot 10^{-23} \text{ J/K}$$

$$h = 6.626 \cdot 10^{-34} \text{ Js}$$

$$V_n^2 = 4kTBR$$

$$V_n = 2\sqrt{kTR}$$

Elektromotorisk RMS-verdi!

$$\left(\frac{V}{\sqrt{Hz}} \right)$$

R mtemperatur:

$$4 \cdot 10^{-21} \frac{W}{Hz}$$

$$1k\Omega \text{ mots.: } E_{rms} = 4 \frac{nV}{\sqrt{Hz}}$$

Cascade:

$$T_{eq} = T_1 + \frac{T_2}{G_1} + \frac{T_3}{G_1 G_2} + \dots$$

$$NF_{eq} = 1 + \frac{T_{eq}}{T_0} = NF_1 + \frac{NF_2 - 1}{G_1} + \frac{NF_3 - 1}{G_1 G_2} + \dots$$

$$G_T = \frac{P_L}{P_{AVS}} = |S_{21}|^2 \cdot \frac{(1-|\Gamma_S|^2) \cdot (1-|\Gamma_L|^2)}{|1-\Gamma_S \Gamma_{in}|^2 \cdot |1-S_{22} \Gamma_L|^2} \quad \text{Transducer Gain}$$

$$P_L = \frac{1}{2} \cdot \frac{|V_2|^2}{Z_0} \cdot (1-|\Gamma_L|^2) \quad \text{til } M_L \quad P_{AVS} = \frac{(\frac{V_g}{2} \cdot \frac{1}{2})^2}{Z_0} = \frac{|V_g|^2}{8Z_0}$$

$$P_{in} = \frac{1}{2} \cdot \frac{|V_1|^2}{Z_0} \cdot (1-|\Gamma_{in}|^2) \quad \text{til transistor}$$

$$G = \frac{P_L}{P_{in}} \quad \text{"gain" (useless)}$$

$$G_A = \frac{P_{AVL}}{P_{AVS}} = \frac{P_L | \Gamma_L = \Gamma_{out}^* |}{P_{AVS}} = |S_{21}|^2 \cdot \frac{(1-|\Gamma_S|^2)}{|1-S_{11} \Gamma_S|^2 \cdot (1-|\Gamma_{out}|^2)} \quad \text{Available gain}$$

$$\text{Vanhignis: } G_A > G > G_T$$

$$\text{eller: } G > G_A > G_T$$

$$G_T = \underbrace{\frac{1-|\Gamma_S|^2}{|1-\Gamma_S \Gamma_{in}|^2}}_{G_S \text{ due to source matching}} \cdot \underbrace{|S_{21}|^2}_{\text{transistor gain @ 50\Omega in/output}} \cdot \underbrace{\frac{1-|\Gamma_L|^2}{|1-S_{22} \Gamma_L|^2}}_{\text{Gain due to load matching}}$$

$$\text{Unilateral: } s_{12} = 0 \Rightarrow G_T = G_{TV} = \frac{1-|\Gamma_S|^2}{|1-\Gamma_S \cdot s_{11}|^2} \cdot |S_{21}|^2 \cdot \frac{1-|\Gamma_L|^2}{|1-S_{22} \Gamma_L|^2}$$

For maximum unilateral gain, we need $\Gamma_S = s_{11}^*$ og $\Gamma_L = S_{22}^* \Rightarrow$

$$G_{TV(\max)} = \underbrace{\frac{1}{1-|s_{11}|^2}}_{G_S(\max)} \cdot |S_{21}|^2 \cdot \underbrace{\frac{1}{1-|S_{22}|^2}}_{G_L(\max)}$$

(16)

pg. 61

Bilateral max conjugate gainStability factor

$$\Delta = S_{11} \cdot S_{22} - S_{12} \cdot S_{21}$$

$$K = \frac{1 - |S_{11}|^2 - |S_{22}|^2 + |\Delta|^2}{2 \cdot |S_{12}| \cdot |S_{21}|}$$

$$G_T(\max) = MAG = \frac{|S_{21}|}{|S_{12}|} \cdot \begin{cases} k + \sqrt{k^2 - 1} & \text{if } |\Delta| \geq 1 \\ k - \sqrt{k^2 - 1} & \text{if } |\Delta| < 1 \end{cases} \leftarrow \begin{cases} \text{har løsning bare} \\ \text{här } k > 1 \end{cases}$$

$$\boxed{\frac{1}{(1+U)^2} < \frac{G_T}{G_{TU}} < \frac{1}{(1-U)^2}}$$

min max

$$\text{Unilateral figure of merit } U = \frac{|S_{12}| |S_{21}| \cdot |S_{11}| |S_{22}|}{(1 - |S_{11}|^2)(1 - |S_{22}|^2)}$$

$$U=0 \quad (S_{12}=0) \quad G_T = G_{TU} \quad \text{ok}$$

$$U=0.1 \sim \text{ok}$$

$$U=0.2 \quad \text{not acceptable}$$

Stability:

For hver frekvens må Γ_s (input stability) og Γ_L (output stab.) være utenfor sirkelene som er "unstable regions".

Unconditionally stable:

For alle Γ_s og $\Gamma_L \Rightarrow$ Sirkelene må aldri krysse Smith diagrammet.
 $\Rightarrow k > 1$ og $|\Delta| < 1$

Når $k < 1 \Rightarrow$ potentially unstable

$$\text{teoretisk grense: } MSG = MAG|_{k=1} = \frac{|S_{21}|}{|S_{12}|}$$

} I praksis prøver vi å føre til $G = MSG - 3\text{dB}$ for bra stabilitet.