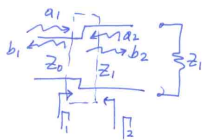


Impedance Step:

S-9



Terminate port 2 with Z_1

$$\Gamma_1 = \frac{b_1}{a_1} = S_{11} = \frac{Z_1 - Z_0}{Z_1 + Z_0}$$

Terminate port 1 with Z_0

$$\Gamma_2 = \frac{b_2}{a_2} = S_{22} = \frac{Z_0 - Z_1}{Z_0 + Z_1} = -\Gamma_1$$

Since it is lossless

$$|S_{11}|^2 + |S_{21}|^2 = 1 \Rightarrow |S_{21}| = \sqrt{1 - |\Gamma_1|^2} = |S_{12}| \text{ (reciprocity)}$$

S-Matrix

$$\begin{bmatrix} \Gamma_1 & \sqrt{1 - |\Gamma_1|^2} \\ \sqrt{1 - |\Gamma_1|^2} & -\Gamma_1 \end{bmatrix}$$

If we expand $\sqrt{1 - |\Gamma_1|^2}$, we find

$$S_{21} = S_{12} = \frac{2\sqrt{Z_0 Z_1}}{Z_0 + Z_1}$$

Let us look at it differently: Terminate Port 2 with Z_1 & calculate $V_2 (= b_2 \sqrt{Z_1})$

$$V_2 = (1 + \Gamma_1) V_1^+ = \frac{2Z_1}{Z_0 + Z_1} V_1^+ \rightarrow \text{Note: } \frac{V_2}{V_1^+} \neq S_{21}$$


$$\text{and } b_2 \sqrt{Z_1} = \frac{2Z_1}{Z_0 + Z_1} a_1 \sqrt{Z_0}$$

$$\Rightarrow S_{21} = \frac{b_2}{a_1} = \frac{2\sqrt{Z_1 Z_0}}{Z_0 + Z_1}$$

because we need to normalize to two different impedances Z_0 & Z_1 to get b_2 & a_1 .

General S-parameters 2-Port:

S-10

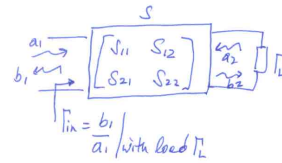


$$\begin{aligned} a_2 &= \Gamma \\ b_2 &= S_{11} a_1 + S_{12} a_2 \\ b_2 &= S_{21} a_1 + S_{22} a_2 \end{aligned}$$

$$\Rightarrow \frac{b_1}{a_1} = S_{11} + \frac{S_{21} \Gamma S_{12}}{1 - S_{22} \Gamma}$$

See explanation in class "Follow the Waves"

Shift in Terminal Planes:

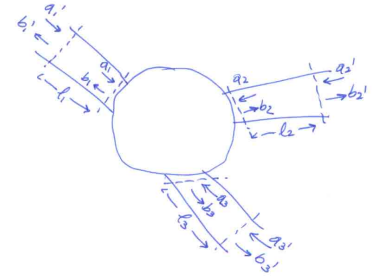

$$a_1' = a_1 e^{+j\beta l_1}$$

$$b_1' = b_1 e^{+j\beta l_1}$$

$$S_{11}' = S_{11} e^{-2j\beta l_1}$$

$$S_{mn}' = S_{mn} e^{-2j\beta l_n}$$


$$\text{Also } S_{mn}' = S_{mn} e^{-j(\beta l_m + \beta l_n)}$$

Impedance & Admittance Matrices:

S-11

$$V_1 = Z_{11} I_1 + Z_{12} I_2 + \dots + Z_{1n} I_n$$
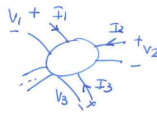
$$V_n = Z_{n1} I_1 + Z_{n2} I_2 + \dots + Z_{nn} I_n$$



$$[V] = [Z][I]$$


$$\text{also } [I] = [Y][V] \text{ & } [Z] = [Y]^{-1} \text{ (or } [Y] = [Z]^{-1})$$

$$\text{To calculate } Z_{ij} = \frac{V_i}{I_j} \Big|_{I_k=0, k \neq j}$$

- Reciprocal Network: $Z_{nm} = Z_{mn}$

- Lossless Network: $\text{Re}\{Z_{nn}\} = 0$
 $m \neq n, m, n = 1, 2, \dots, n$

Transmission Matrix:

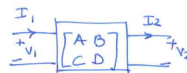

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_2 \\ I_2 \end{bmatrix}$$

$$V_1 = AV_2 + BI_2$$

$$I_1 = CV_2 + DI_2$$


$$A = \frac{V_1}{V_2} \Big|_{I_2=0} \text{ (open circuit port 2) Put voltage source at port 2 \& measure a.c. voltage } V_1$$

$$B = \frac{V_1}{I_2} \Big|_{V_2=0} \text{ (short circuit port 2) } \rightsquigarrow \dots$$

$$C = \frac{I_1}{V_2} \Big|_{I_2=0} \text{ (open circuit port 2) } \rightsquigarrow \dots$$

$$D = \frac{I_1}{I_2} \Big|_{V_2=0} \text{ (short circuit port 2)}$$

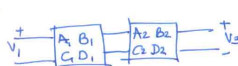The good thing about transmission matrices is that you can cascade them. The bad thing is that they can be unstable in very lossy lines. Most people do not use them & I personally do not like them (I never use them).



$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A_1 & B_1 \\ C_1 & D_1 \end{bmatrix} \begin{bmatrix} A_2 & B_2 \\ C_2 & D_2 \end{bmatrix} \begin{bmatrix} V_2 \\ I_2 \end{bmatrix}$$

EECS 411:

Conversion between Two-Port Network Parameters


S-12

TABLE 5.2 Conversions Between Two-Port Network Parameters

	S	Z	Y	ABCD
S_{11}	S_{11}	$\frac{(Z_{11} - Z_0)(Z_{22} + Z_0) - Z_{12}Z_{21}}{\Delta Z}$	$\frac{(Y_0 - Y_{11})(Y_0 + Y_{11}) + Y_{12}Y_{21}}{\Delta Y}$	$\frac{A + B/Z_0 - CZ_0 - D}{A + B/Z_0 + CZ_0 + D}$
S_{12}	S_{12}	$\frac{2Z_{12}Z_0}{\Delta Z}$	$\frac{-2Y_{12}Y_0}{\Delta Y}$	$\frac{2(AD - BC)}{A + B/Z_0 + CZ_0 + D}$
S_{21}	S_{21}	$\frac{2Z_{21}Z_0}{\Delta Z}$	$\frac{-2Y_{21}Y_0}{\Delta Y}$	$\frac{2}{A + B/Z_0 + CZ_0 + D}$
S_{22}	S_{22}	$\frac{(Z_{11} + Z_0)(Z_{22} - Z_0) - Z_{12}Z_{21}}{\Delta Z}$	$\frac{(Y_0 + Y_{11})(Y_0 - Y_{21}) + Y_{12}Y_{21}}{\Delta Y}$	$\frac{-A + B/Z_0 - CZ_0 + D}{A + B/Z_0 + CZ_0 + D}$
Z_{11}	$Z_{11} = \frac{1 + S_{11}(1 - S_{22}) + S_{12}S_{21}}{(1 - S_{11})(1 - S_{22}) - S_{12}S_{21}}$	Z_{11}	$\frac{Y_{22}}{ Y }$	$\frac{A}{C}$
Z_{12}	$Z_{12} = \frac{Z_0(1 - S_{11})(1 - S_{22}) - S_{12}S_{21}}{2S_{21}}$	Z_{12}	$\frac{-Y_{12}}{ Y }$	$\frac{AD - BC}{C}$
Z_{21}	$Z_{21} = \frac{Z_0(1 - S_{11})(1 - S_{22}) - S_{12}S_{21}}{2S_{21}}$	Z_{21}	$\frac{-Y_{21}}{ Y }$	$\frac{1}{C}$
Z_{22}	$Z_{22} = \frac{Z_0(1 - S_{11})(1 - S_{22}) - S_{12}S_{21}}{(1 - S_{11})(1 - S_{22}) - S_{12}S_{21}}$	Z_{22}	$\frac{Y_{11}}{ Y }$	$\frac{D}{C}$
Y_{11}	$Y_{11} = \frac{1 + S_{11}(1 - S_{22}) + S_{12}S_{21}}{(1 - S_{11})(1 - S_{22}) - S_{12}S_{21}}$	$\frac{Z_{22}}{ Z }$	Y_{11}	$\frac{D}{B}$
Y_{12}	$Y_{12} = \frac{-2S_{21}}{(1 + S_{11})(1 + S_{22}) - S_{12}S_{21}}$	$\frac{-Z_{12}}{ Z }$	Y_{12}	$\frac{BC - AD}{B}$
Y_{21}	$Y_{21} = \frac{-2S_{21}}{(1 + S_{11})(1 + S_{22}) - S_{12}S_{21}}$	$\frac{-Z_{21}}{ Z }$	Y_{21}	$\frac{-1}{B}$
Y_{22}	$Y_{22} = \frac{1 + S_{11}(1 - S_{22}) + S_{12}S_{21}}{(1 - S_{11})(1 - S_{22}) - S_{12}S_{21}}$	$\frac{Z_{11}}{ Z }$	Y_{22}	$\frac{A}{B}$
A	$\frac{(1 + S_{11})(1 - S_{22}) + S_{12}S_{21}}{2S_{21}}$	$\frac{Z_{11}}{Z_0}$	$\frac{-Y_{22}}{Y_0}$	A
B	$\frac{Z_0(1 + S_{11})(1 - S_{22}) - S_{12}S_{21}}{2S_{21}}$	$\frac{ Z }{Z_0}$	$\frac{-1}{Y_0}$	B
C	$\frac{1 - S_{11}(1 - S_{22}) - S_{12}S_{21}}{2S_{21}}$	$\frac{1}{Z_0}$	$\frac{-Y_{12}}{Y_0}$	C
D	$\frac{(1 - S_{11})(1 + S_{22}) - S_{12}S_{21}}{2S_{21}}$	$\frac{Z_{22}}{Z_0}$	$\frac{Y_{11}}{Y_0}$	D


$$|Z| = Z_{11}Z_{22} - Z_{12}Z_{21}; |Y| = Y_{11}Y_{22} - Y_{12}Y_{21}; \Delta Y = (Y_{11} + Y_0)(Y_{22} + Y_0) - Y_{12}Y_{21}; \Delta Z = (Z_{11} + Z_0)(Z_{22} + Z_0) - Z_{12}Z_{21}; Y_0 = 1/Z_0$$

ABCD Matrix

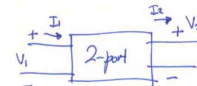

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_2 \\ I_2 \end{bmatrix}$$

ZoY matrices:

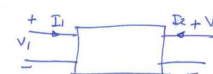

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$